



# Energy Conversion I

[alexis.martin@ensea.fr](mailto:alexis.martin@ensea.fr)  
Desk D216





## Layout

- Non isolated choppers
- Switch mode power supplies
- Power components
- **Sinusoidal absorption**

**Introduction**

**Boost**

**Flyback**

**Example of  
converter**

Introduction


# Introduction

Boost

Flyback
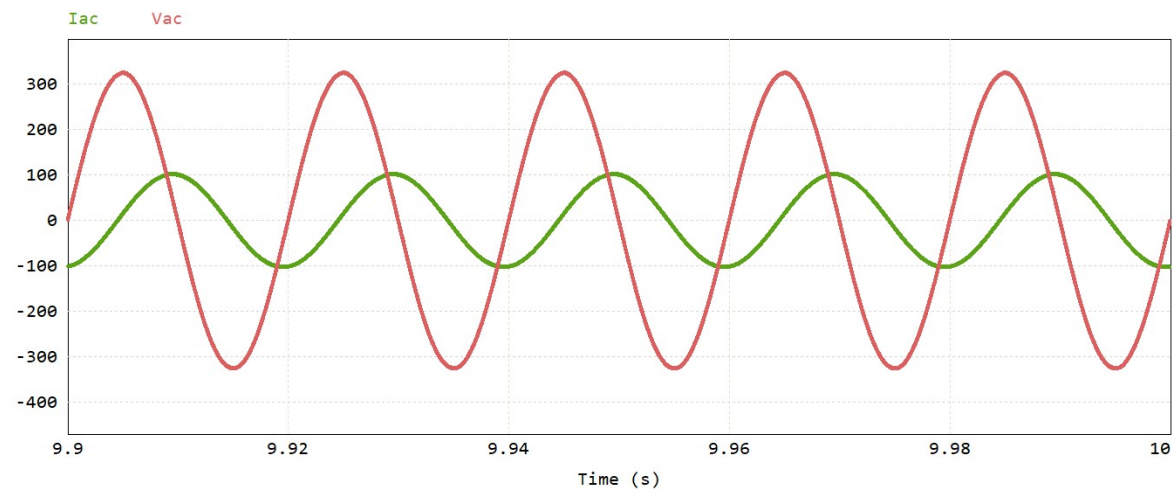
## Reminder: Power in AC

$$V_{RMS} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$



- Real power:  $P = \langle p(t) \rangle = \langle v(t) \cdot i(t) \rangle = V_{RMS} \cdot I_{RMS} \cdot \cos(\varphi_1)$
- Reactive power:  $Q = V_{RMS} \cdot I_{RMS} \cdot \sin(\varphi_1)$
- Apparent power:  $S = V_{RMS} \cdot I_{RMS}$
- Power factor:  $pf = \frac{P}{S}$
- Total harmonic distortion:  $THD = \frac{\sqrt{\sum_{n=2}^{\infty} I_{n\ RMS}^2}}{I_{1\ RMS}}$



# Introduction

Boost


Flyback

Example of  
converter

Reminder: Diode rectifier

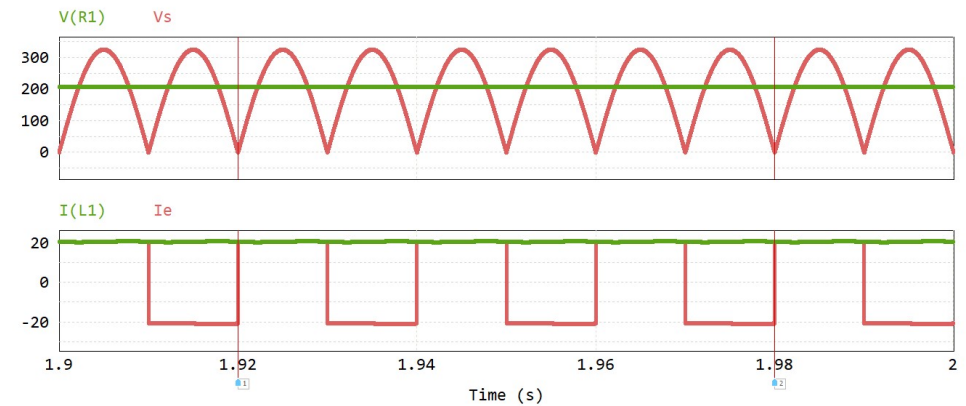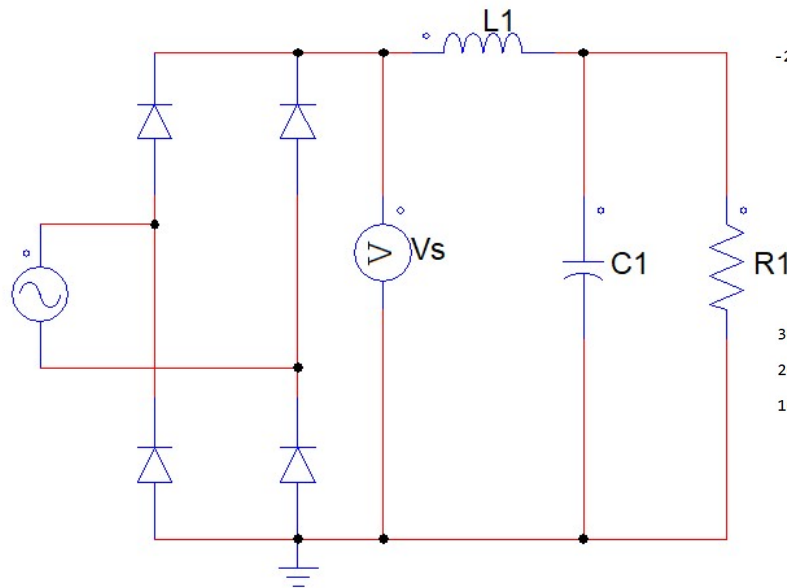
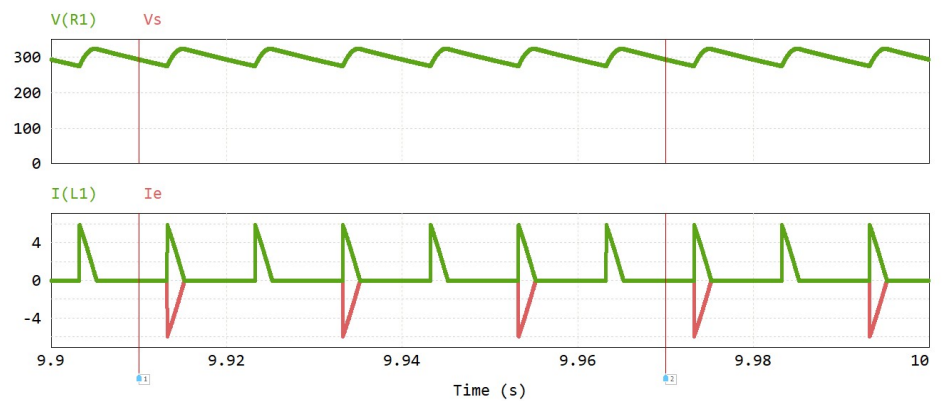
$$L = 10H \rightarrow pf = 0,9 \quad THD = 0,48$$



$$L = 10nH \rightarrow pf = 0,5 \quad THD = 1,5$$

# Introduction

Boost

Flyback

Example of  
converter

European standard: 61000-3-2

Limits for harmonics currents emission (class C  $\approx$  lightning)

Tableau 2 – Limites pour les appareils de classe C

Rang harmonique  n	Courant harmonique maximal exprimé en pourcentage du courant fondamental d'entrée des luminaires %
2	2
3	30 $\sigma$
5	10
7	7
9	5
11 $\delta n \leq 39$ (harmoniques impairs seulement)	3
* $\sigma$ est le facteur de puissance du circuit	






# Introduction

Boost

Flyback

Example of  
converter

European standard: 61000-3-2

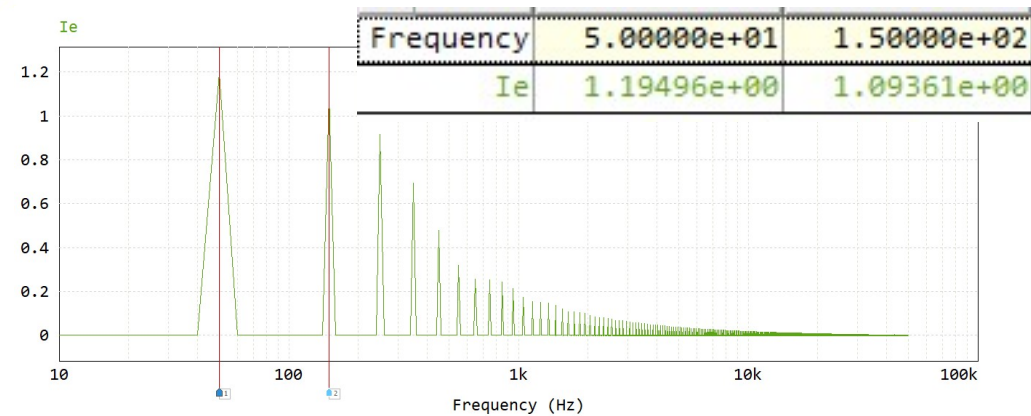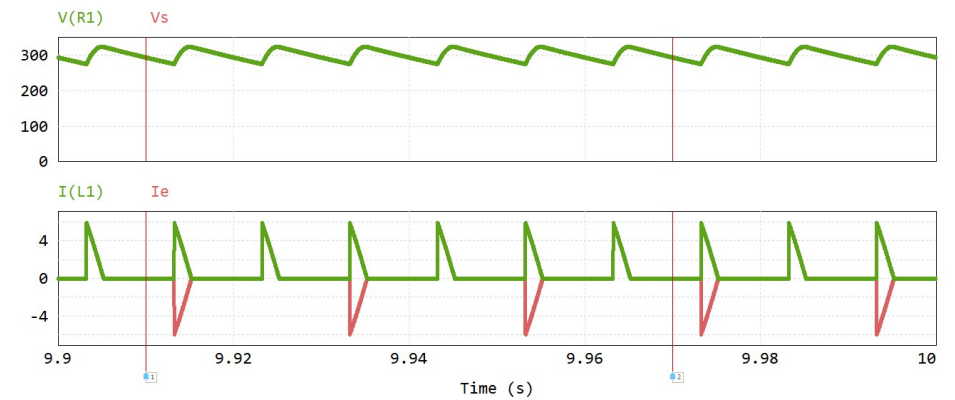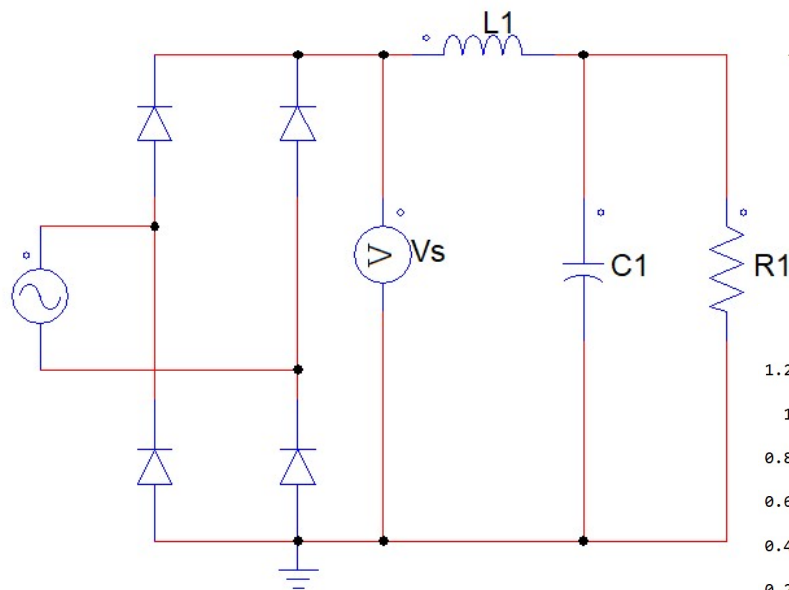


# Introduction

Boost

Flyback

Example of  
converter

Power factor correction

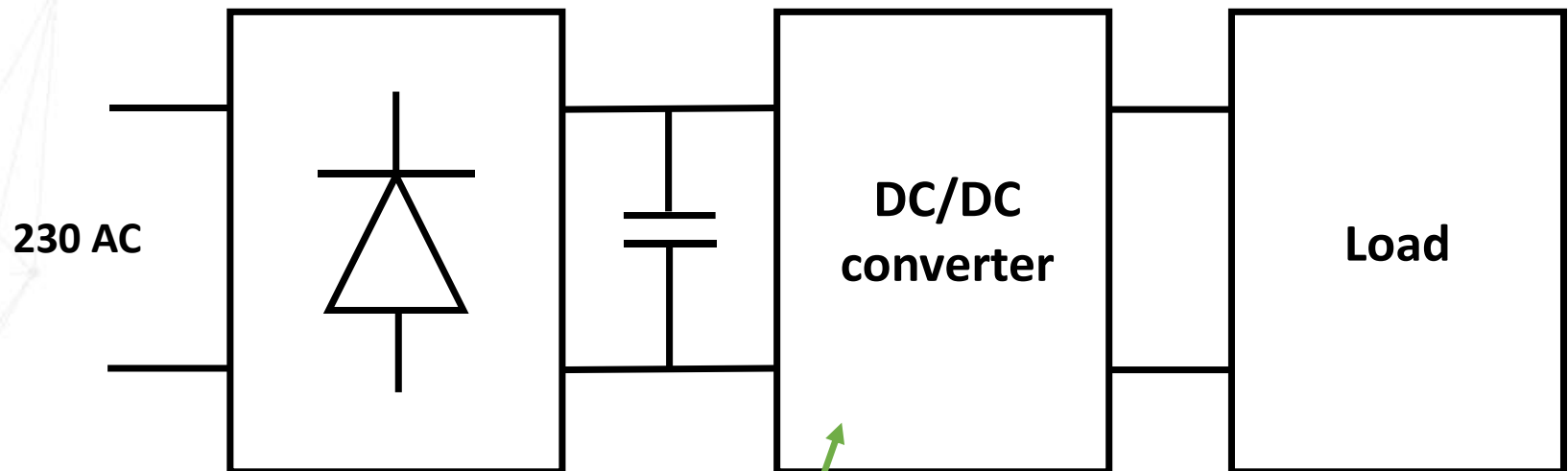

Used to absorb  
sinus current  
(before rectifier)



Introduction

**Boost**

Flyback

Example of  
converter

Boost for PFC

# Introduction


## Boost Structure

PWM control  
Hysteresis control

## Flyback

## Example of converter

### Structure

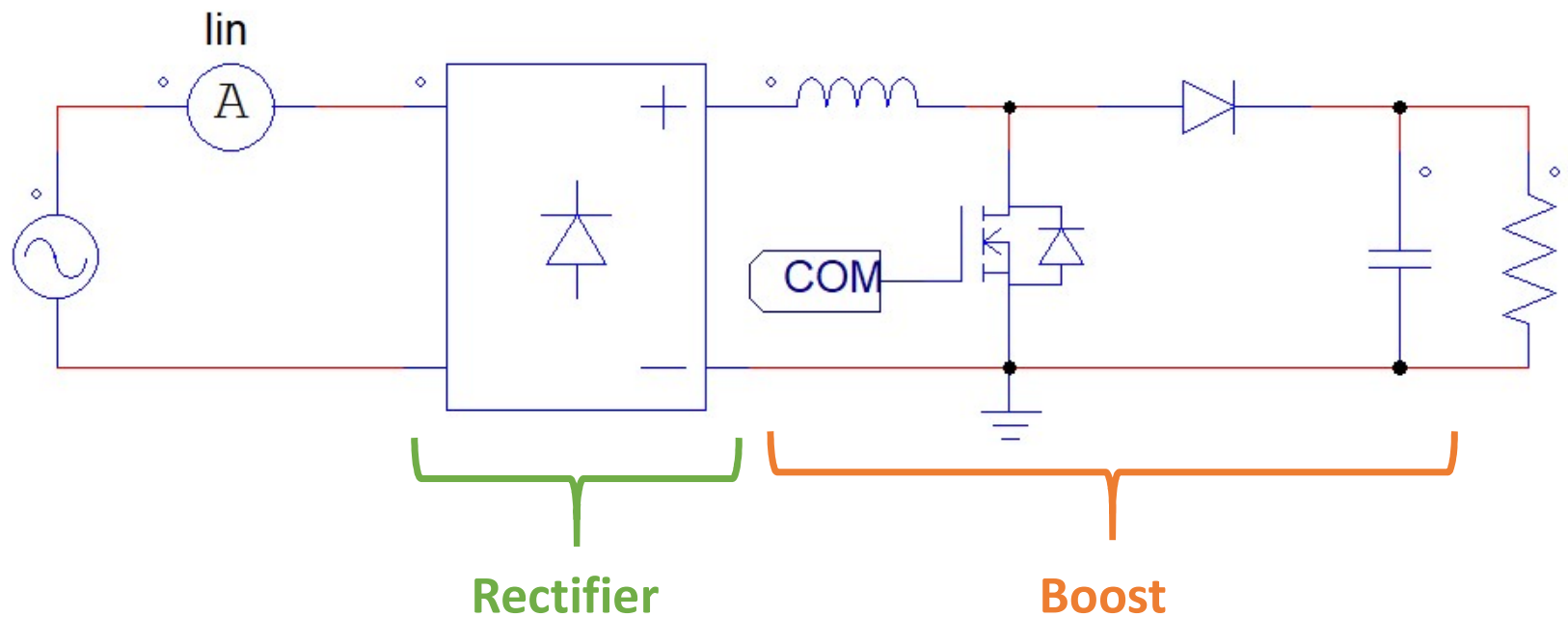

## Introduction


### Boost Structure

PWM control  
Hysteresis control

### Flyback

### Example of converter

## Structure

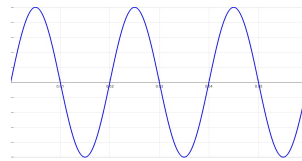


$$v_r = V\sqrt{2}\sin(\theta)$$

$$\theta = 2\pi f_{BF}t$$
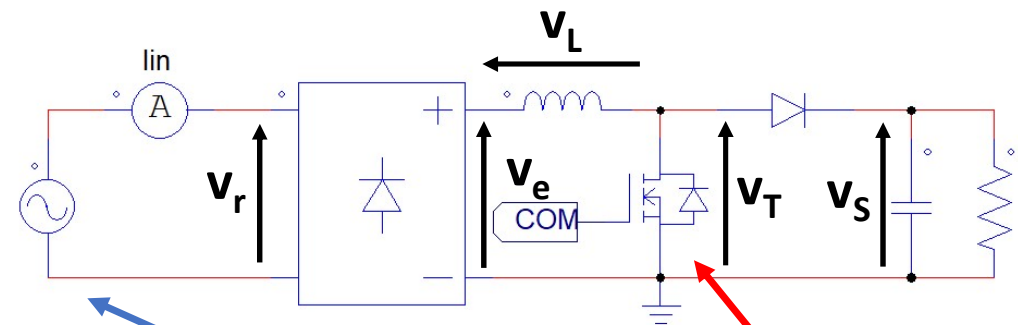
### Goal:

$$I_{in} = I \cdot \sqrt{2}\sin(\theta)$$



- 2 frequencies:  $f_{LF}$  (50Hz for grid) and  $f_{HF}$  (few 10 kHz for switching)

$$v_e = |v_r| \text{ and } v_e = (1 - \alpha)v_s \quad \rightarrow \quad V_S > v_{r \max}$$

- Two control strategies :
  - Fixed switching frequency -> PWM
  - Free switching frequency -> hysteresis control

## Introduction

### Boost

Structure


PWM control

Hysteresis control



### Flyback

### Example of converter

#### PWM control

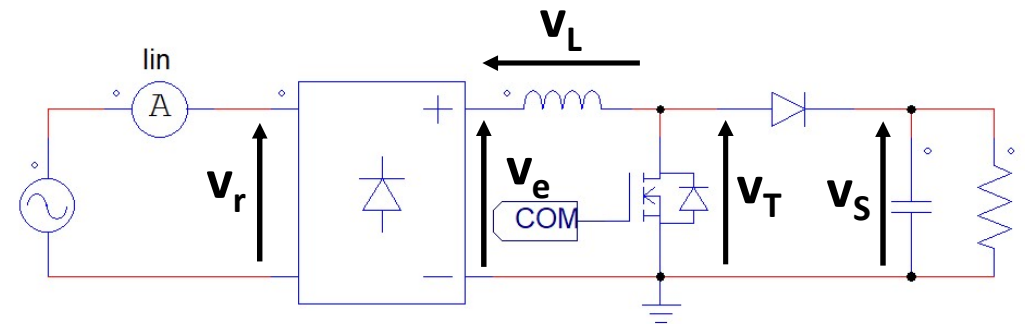

- With PWM control, the switching frequency is fixed, the duty cycle is used to control the current
- For low frequency, the boost is a continuous voltage amplifier controlled with the duty cycle  $\alpha$
- Continuous conduction of diodes in the rectifier:  
$$v_e = |v_r| = V\sqrt{2} \cdot |\sin(\theta)|$$

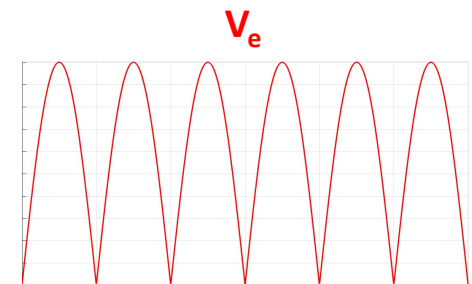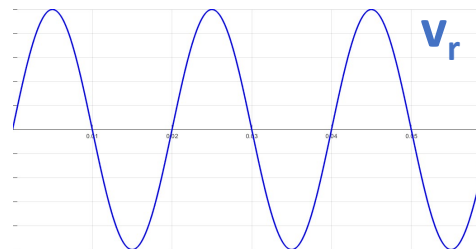

## Introduction

### Boost

Structure


PWM control

Hysteresis control

### Flyback

### Example of converter

#### PWM control

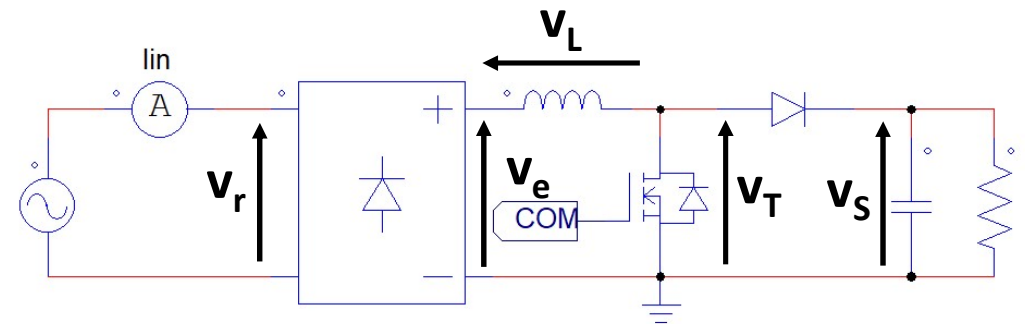

- $v_L = v_e - v_T = V\sqrt{2} \cdot |\sin(\theta)| - (1 - \alpha)V_S = L \frac{di_L}{dt}$
- We want  $I_{in} = I \cdot \sqrt{2} \sin(\theta)$ 
  - $i_L = I \cdot \sqrt{2} \cdot |\sin(\theta)|$
- For  $0 < \theta < \pi$ :
  - $1 - \alpha = \frac{V\sqrt{2}}{V_S} \cdot \sin(\theta) - \frac{L \cdot 2\pi f_{LF} \cdot I\sqrt{2}}{V_S} \cos(\theta)$
  - $\alpha = 1 - \frac{V\sqrt{2}}{V_S} \cdot \left( \sin(\theta) - \frac{2\pi L f_{LF} \cdot P}{V^2} \cos(\theta) \right)$

# Introduction

## Boost

Structure


PWM control

Hysteresis control

## Flyback


Example of converter

PWM control

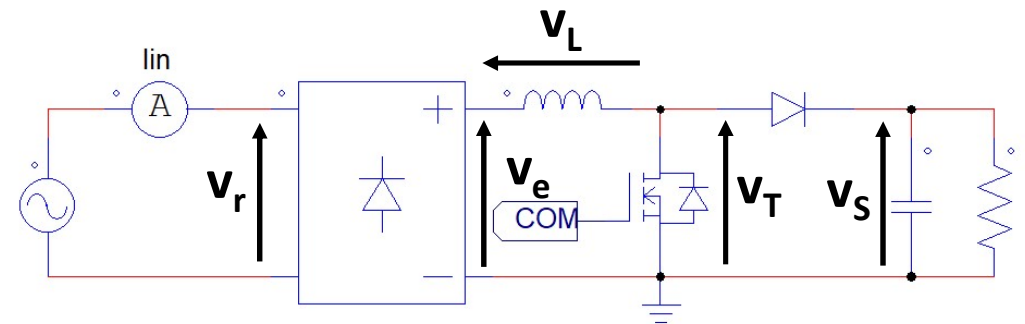

$$\alpha = 1 - \frac{V\sqrt{2}}{V_S} \cdot \left( \sin(\theta) - \frac{2\pi L f_{LF} P}{V^2} \cos(\theta) \right)$$

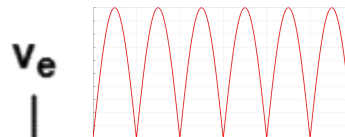Input rectified voltage (for synchronization)



Amplitude of the desired current

Measured output voltage

Measured current

Voltage regulator

Regulator

$i^*$

$v_s$

$i_L$

$v^*$

Desired output voltage

# Introduction

**Boost**  
Structure  
**PWM control**  
Hysteresis control

Flyback

Example of  
converter

PWM control

Input rectified  
voltage (for  
synchronization)

Amplitude of  
the desired  
current

Measured  
output voltage

Measured  
current



Voltage  
regulator

Regulator

Desired output  
voltage

**Condition:** voltage control « slow » (few Hz) to ensure sinusoidal current

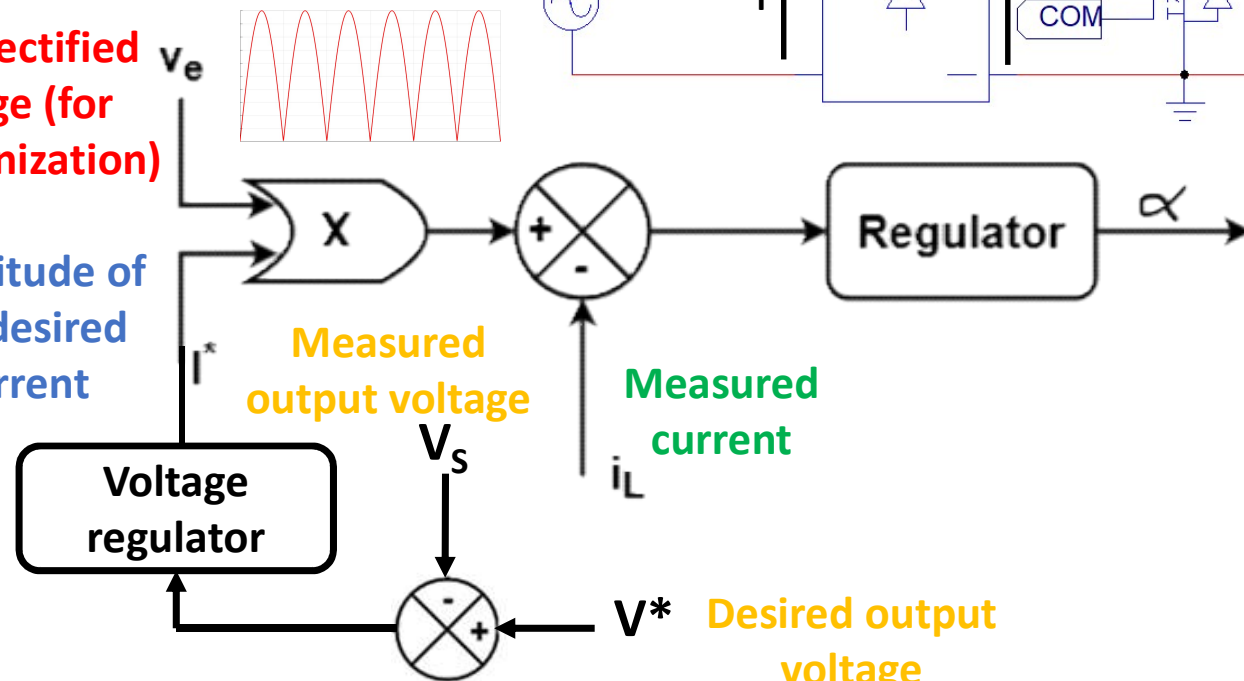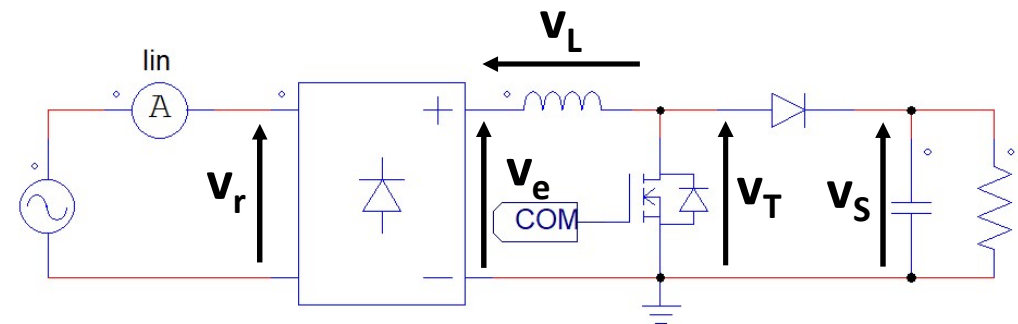Filter the output voltage for measurement (sample at  $2f_{BF}$ , band-stop filter, high output capacitor)





# Introduction

## Boost

Structure


PWM control

Hysteresis control

## Flyback

## Example of converter

### PWM control: components sizing

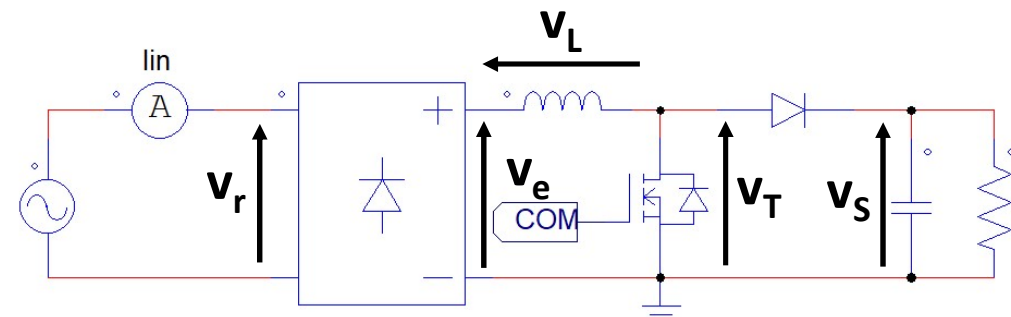

- Semi-conductors

$$\langle i_D \rangle = \frac{P}{V_S} \quad \langle i_T \rangle = \langle i_L \rangle - \langle i_D \rangle = \frac{P}{V_S} \left( \frac{4}{\pi} \frac{V_S}{V\sqrt{2}} - 1 \right)$$

$$I_{T \text{ RMS}} = \frac{P}{V} \sqrt{1 - \frac{8.V\sqrt{2}}{3\pi V_S}} I_{D \text{ RMS}} = \frac{P}{V} \sqrt{\frac{8.V\sqrt{2}}{3\pi V_S}}$$

- Output capacitor

$$\Delta V_{S \text{ BF}} = \frac{P}{2\pi f_{BF} C V_S} \quad I_{C \text{ RMS}} = \frac{P}{V_S} \sqrt{\frac{16.V_S}{3\pi V\sqrt{2}} - 1}$$

- Input inductor: limit the current ripple due to switching BUT small voltage drop

$$\Delta i_{HF} = \frac{V_S}{4Lf_{HF}} \quad \frac{V}{2\pi I f_{BF}} \gg L > \frac{V_S}{4f_{HF} \Delta i_{HF}} \quad I_{L \text{ RMS}} = \frac{P}{V}$$

## Introduction

### Boost

Structure


PWM control

Hysteresis control

## Flyback

Example of  
converter


### Hysteresis control

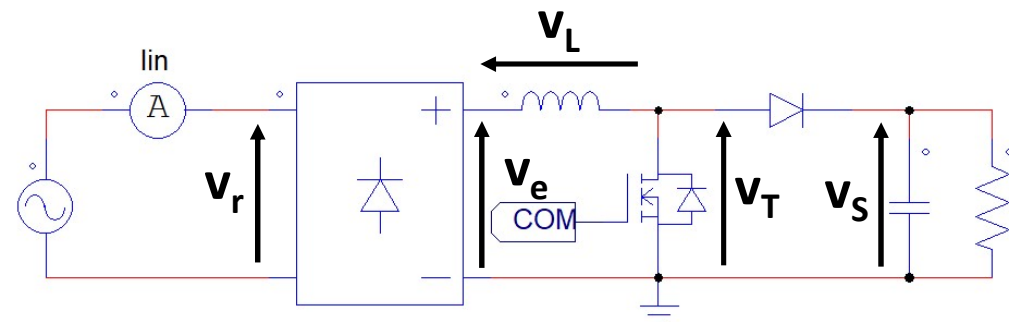

PWM control: need a current regulator to follow a sinus input

➤ Complicated to design the regulator

➤ Hysteresis control

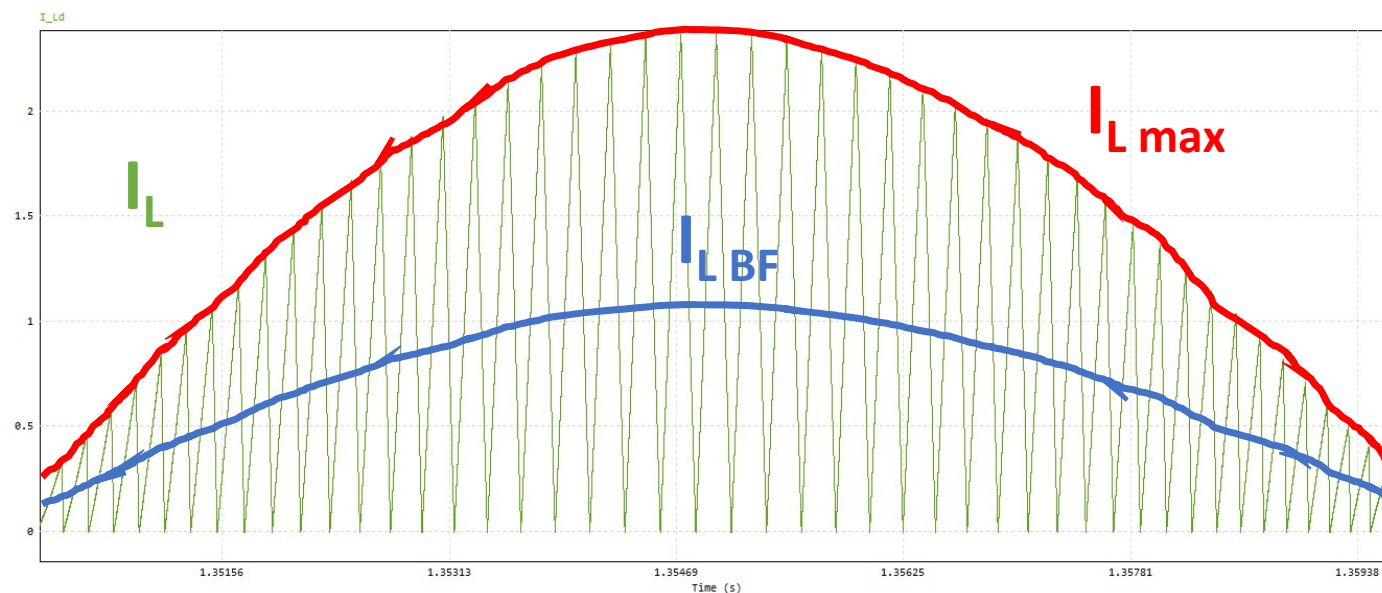

# Introduction

## Boost

Structure



PWM control

Hysteresis control

## Flyback

Example of  
converter

## Hysteresis control

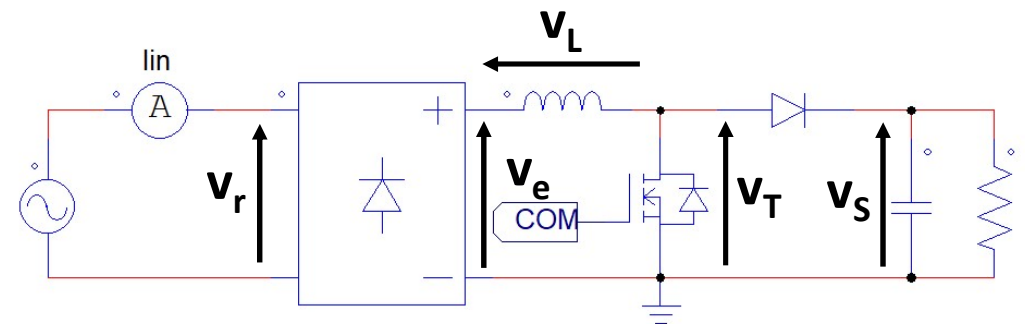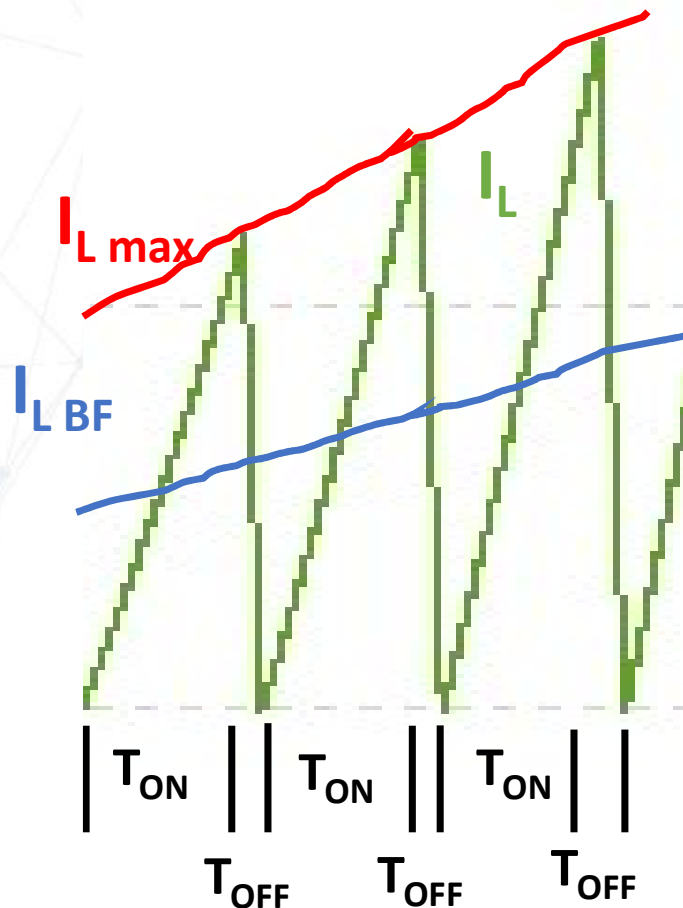

- $I_{L \max} = \frac{V_e}{L} t_{ON} = 2I_{L \text{ BF}} = 2I\sqrt{2}|\sin(\theta)|$   
 $\triangleright t_{ON} = \frac{2LI}{V} = \frac{2LP}{V^2} = \text{cst}$
- $t_{OFF} = t_{ON} \frac{1-\alpha}{\alpha} = t_{ON} \frac{V_e}{V_S - V_e}$   
 $\triangleright f_{HF} = \frac{1}{t_{ON} + t_{OFF}} = \frac{1}{t_{ON}} \left(1 - \frac{V\sqrt{2}}{V_S} |\sin(\theta)|\right)$
- $f_{HF \min} = \frac{1}{t_{ON}}$
- $f_{HF \max} = \frac{1}{t_{ON}} \left(1 - \frac{V\sqrt{2}}{V_S}\right)$

# Introduction

## Boost

Structure


PWM control

Hysteresis control

## Flyback

Example of  
converter

## Hysteresis control

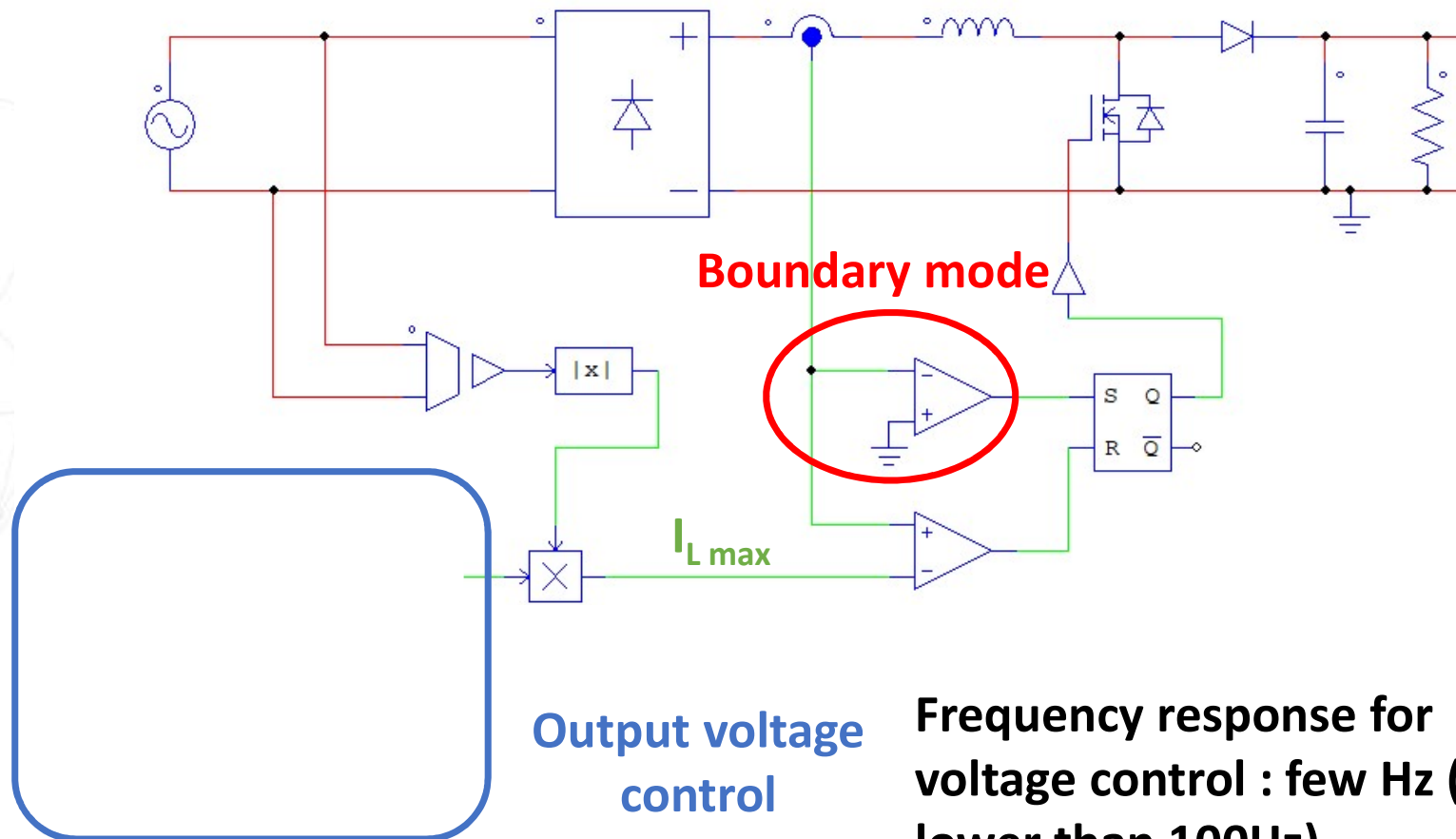

Frequency response for  
voltage control : few Hz (much  
lower than 100Hz)

# Introduction

## Boost

Structure

PWM control

Hysteresis control

## Flyback

Example of  
converter

Example: LED driver






# Introduction

**Boost**  
Structure  
PWM control  
**Hysteresis control**

## Flyback

Example of  
converter

Example: LED driver

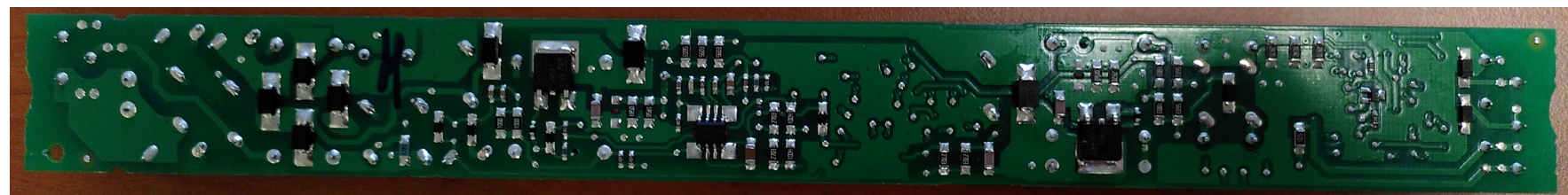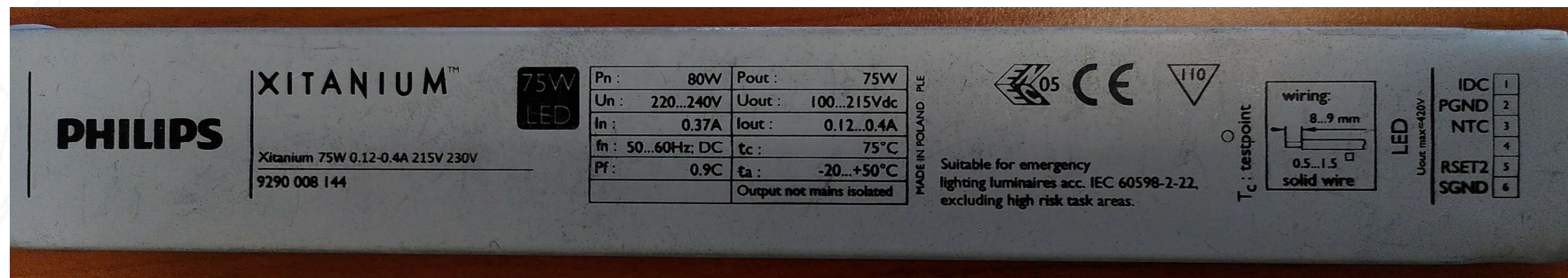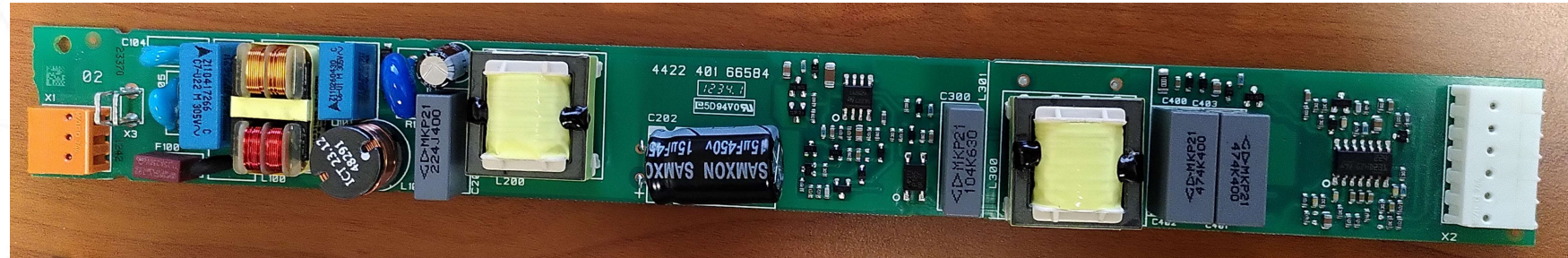

Introduction

Boost

**Flyback**

Example of  
converter

Flyback for PFC



# Introduction


## Boost

## Flyback Structure

Example of RT7306  
Control

Example of  
converter

## Structure

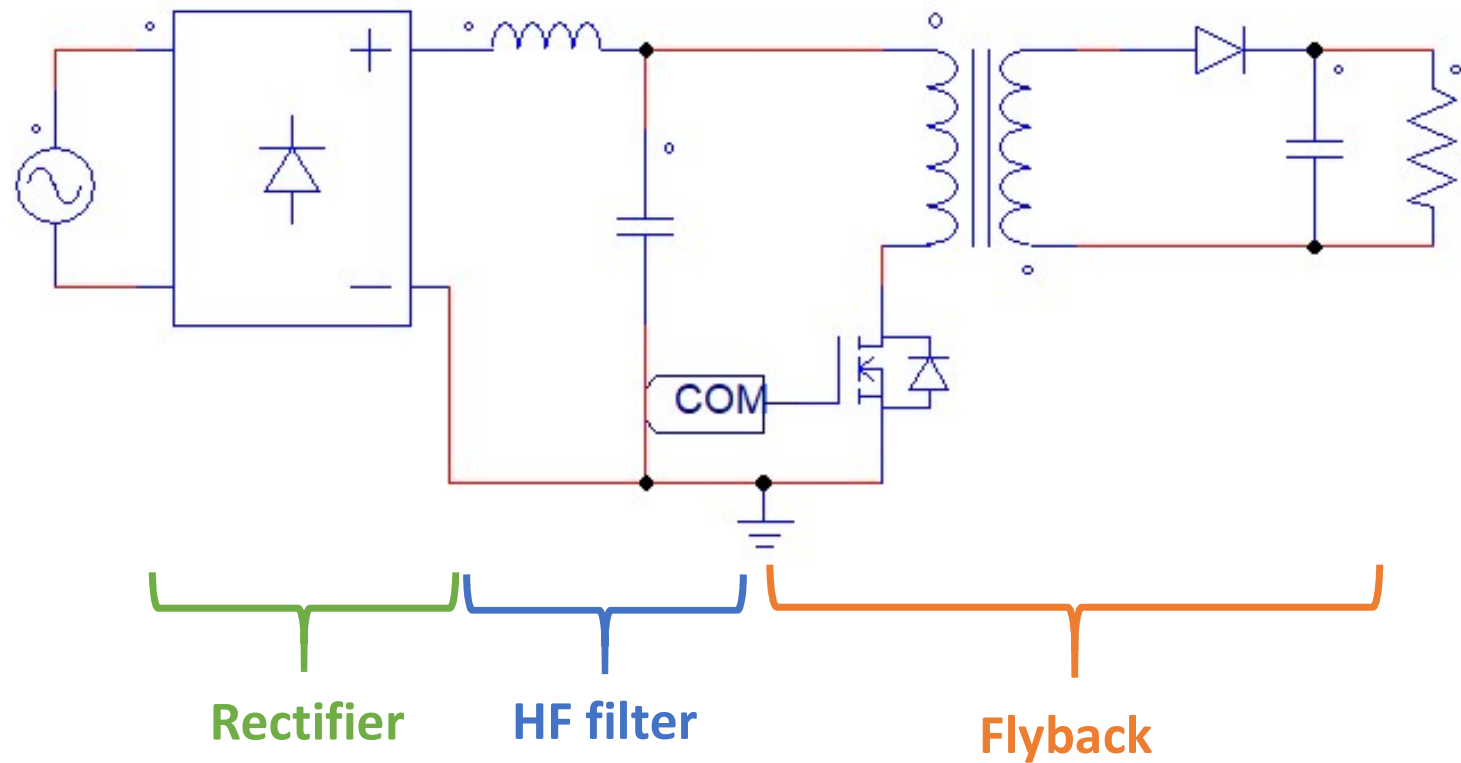

# Introduction

## Boost

## Flyback

## Structure

## Example of RT7306

## Control

## Example of converter


Example of RT7306  
(LED driver)

Rectifier

Flyback

Auto-supply  
with auxiliary  
winding

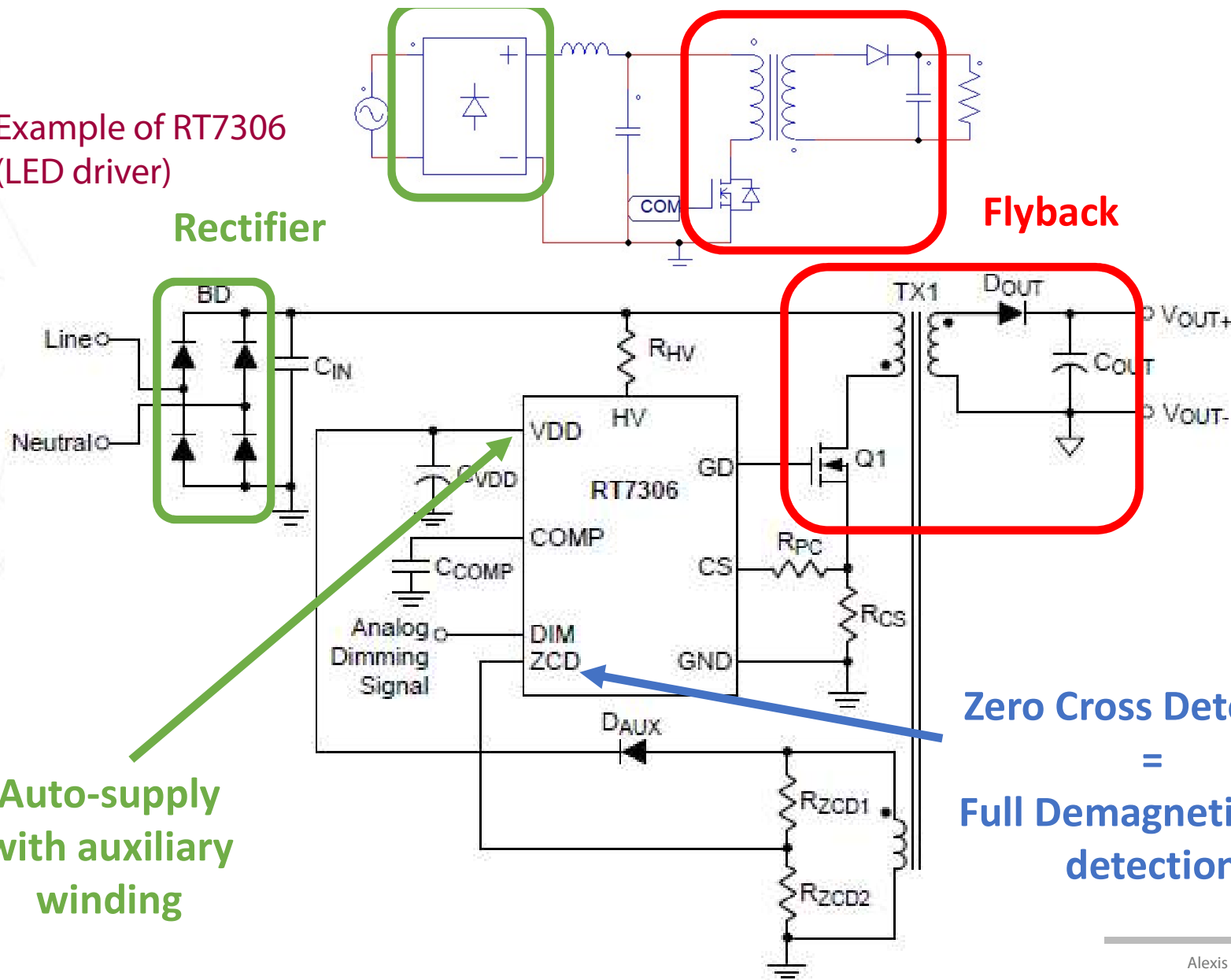Zero Cross Detection  
=  
Full Demagnetization  
detection



## Introduction


## Boost

## Flyback Structure Example of RT7306 Control

## Example of converter

Example of RT7306: Functional Block Diagram

Full demagnetization  
detection

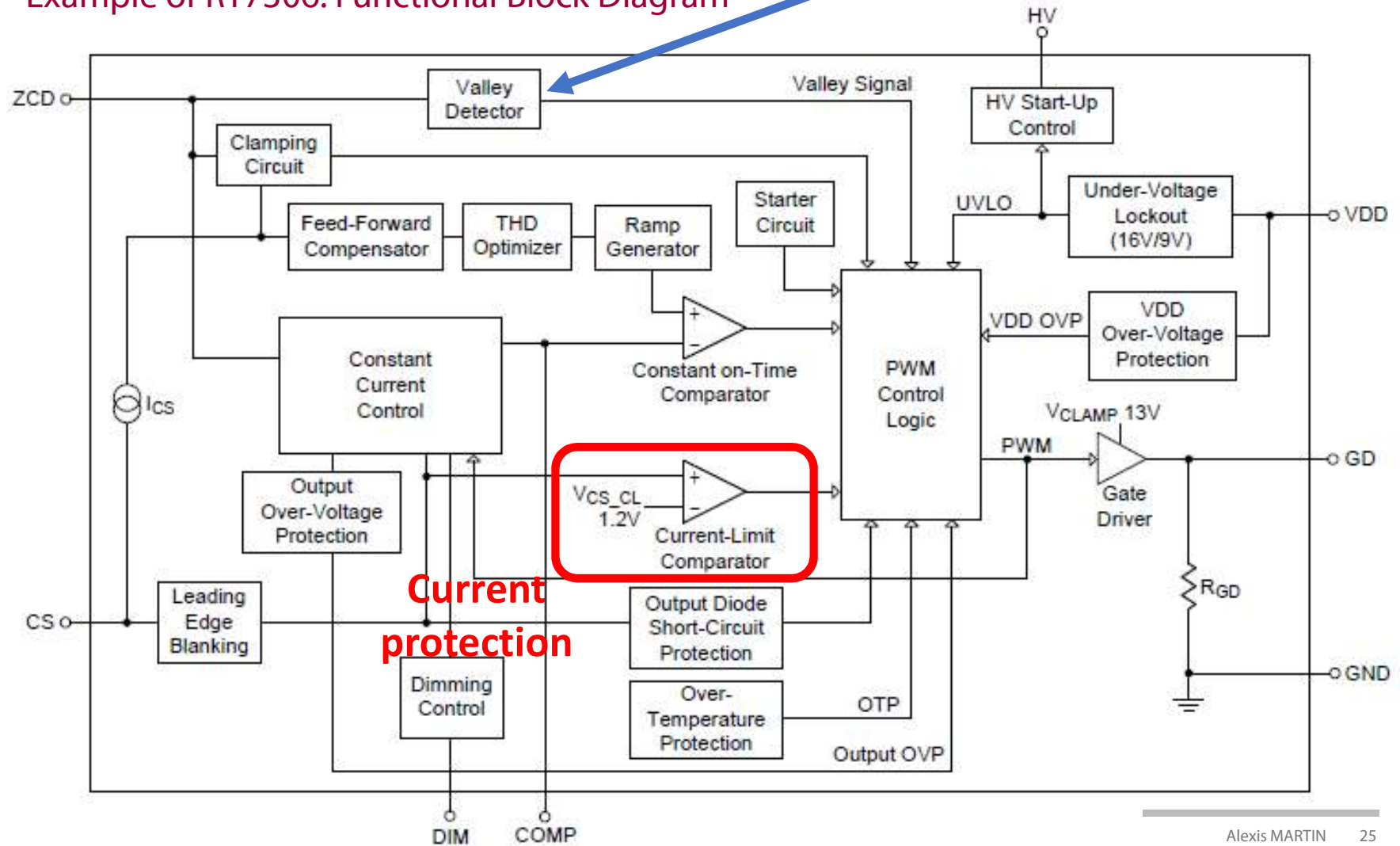

## Introduction


## Boost

## Flyback

Structure  
Example of RT7306  
Control

Example of  
converter

Hysteresis control

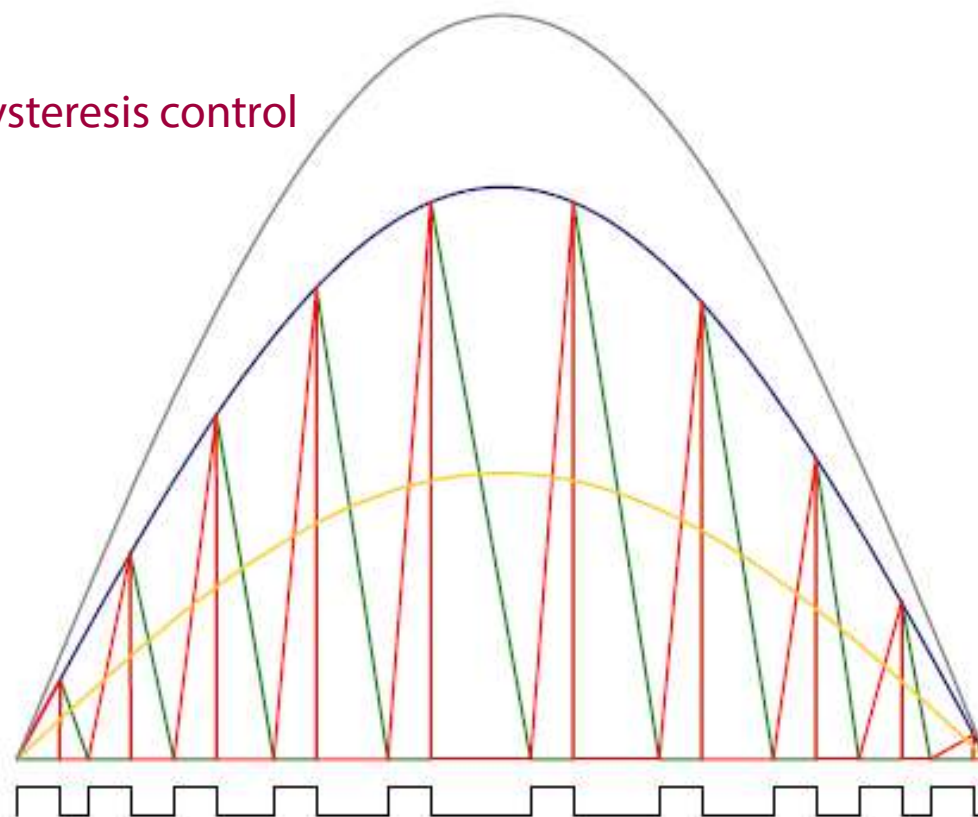

— VIN	Input Voltage
— IL_PK	Peak Inductor Current
— IQ1_DS	MOSFET Current
— Iin_avg	Average Input Current
— IDo	Output Diode Current
— VQ1_GS	MOSFET Gate Voltage

$$I_{L\_PK} = \frac{V_{IN}}{L_m} \times t_{ON}$$

$$I_{L\_PK} = \frac{V_{IN\_PK} \times |\sin(\theta)| \times t_{ON}}{L_m}$$



# Introduction

## Boost

## Flyback Structure Example of RT7306 Control

## Example of converter

### Constant on-time control

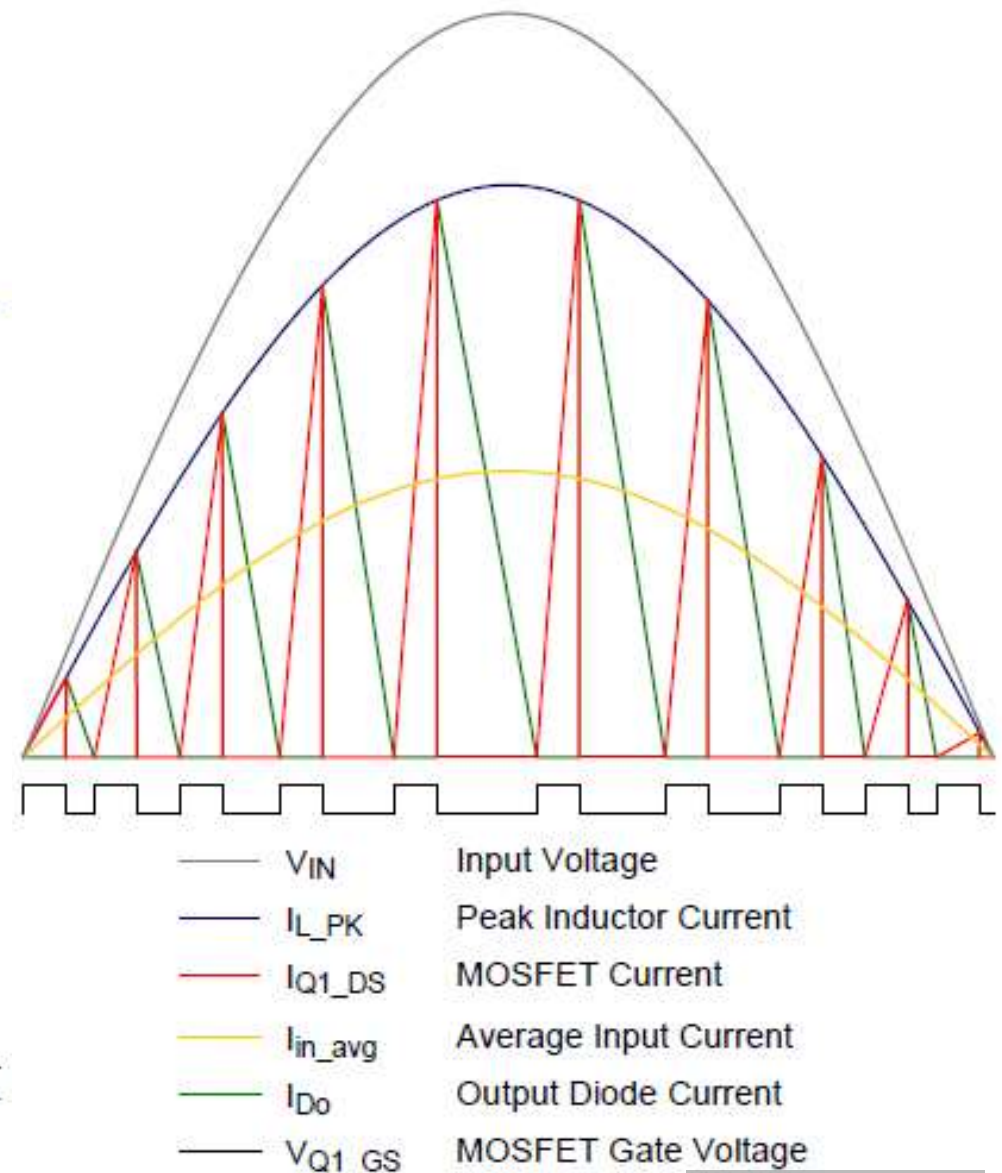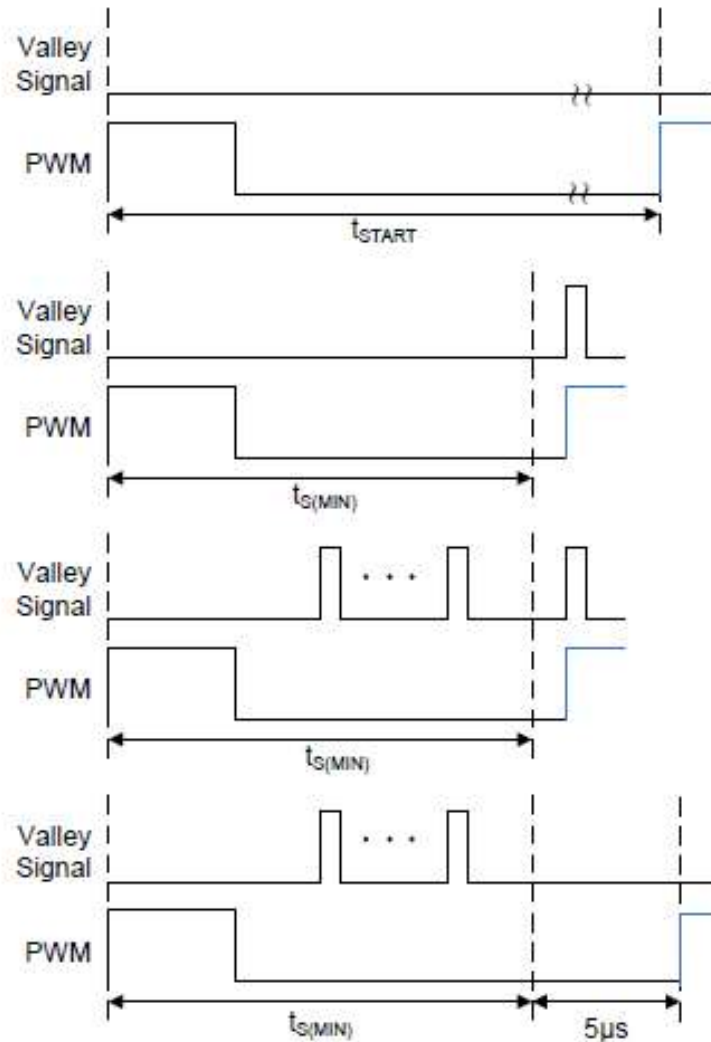



Introduction

Boost

Flyback

**Example of  
converter**

Example of a full converter

Introduction

Boost

Flyback

Example of  
converter

Example: EVL400W-80PL





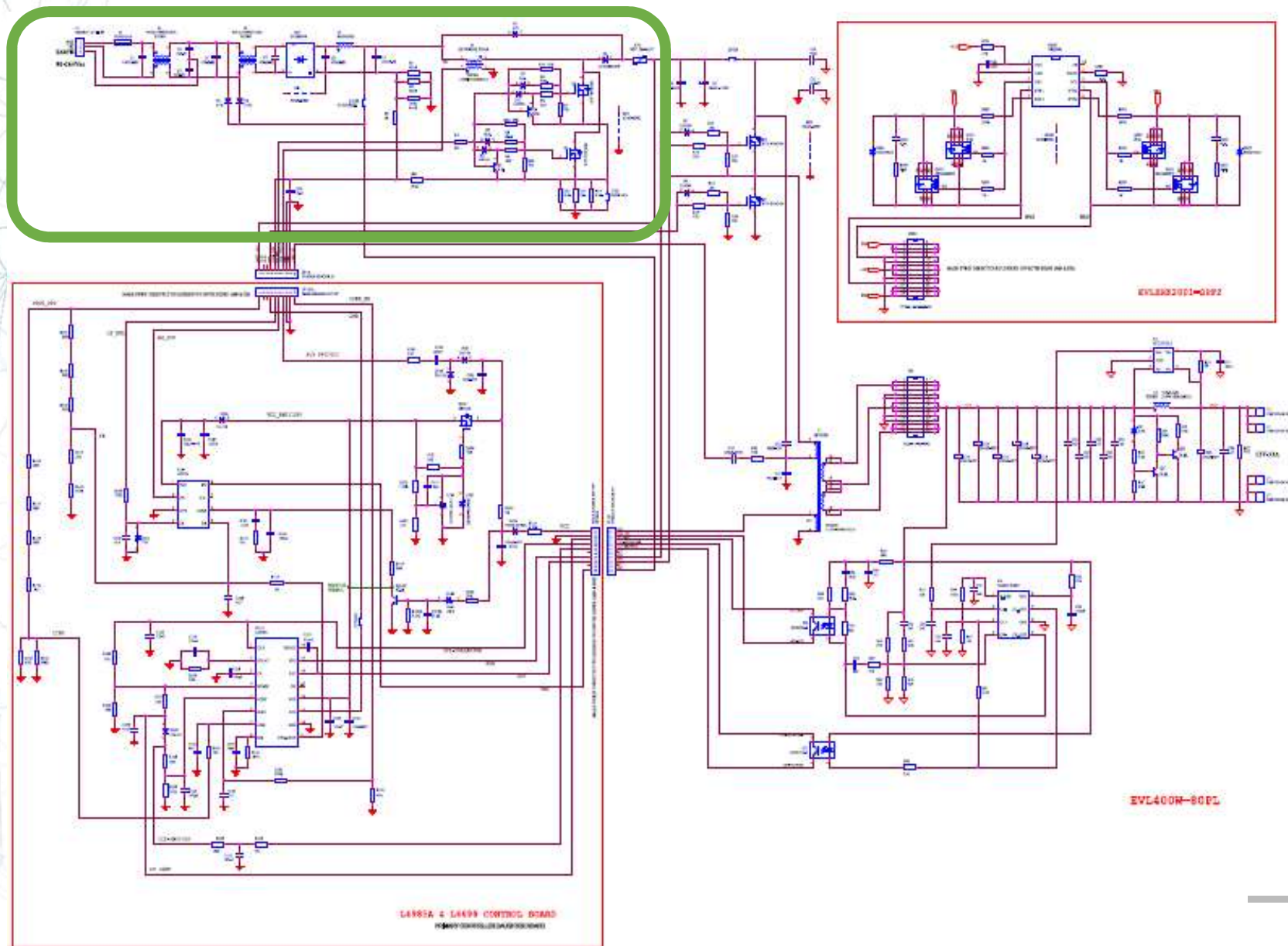
## Example: EVL400W-80PL

The architecture is based on a two-stage approach: a front-end PFC pre-regulator based on a CCM (Continuous Conduction Mode) boost PFC controller using the L4985A, and a downstream LLC resonant half-bridge converter, designed around the L6699.


- Universal input mains voltage range: from 90 Vac to 264 Vac – frequency from 45 to 65 Hz
- Output voltage: 12 V at 33 A continuous operation
- Overall efficiency at full load: > 89%, according to ENERGY STAR® 6.1 limit for computer and compliant with 80Plus PLATINUM level
- Average efficiency: > 89%, according to European CoC ver. 5 Tier 2 for external power supplies
- Efficiency at 250 mW > 50%, compliant to EuP lot 6 Tier 2 limit for household and office equipment
- No load mains consumption: < 150 mW at 230 Vac, below European CoC ver. 5 Tier 2 limit for external power supplies
- Mains harmonics: meets EN-61000-3-2 Class-D and JEITA-MITI Class-D
- EMI: according to EN55022 Class-B
- Safety: meets EN60950 standards
- RoHS compliant



HF filtering


Rectifier


Boost (PFC)

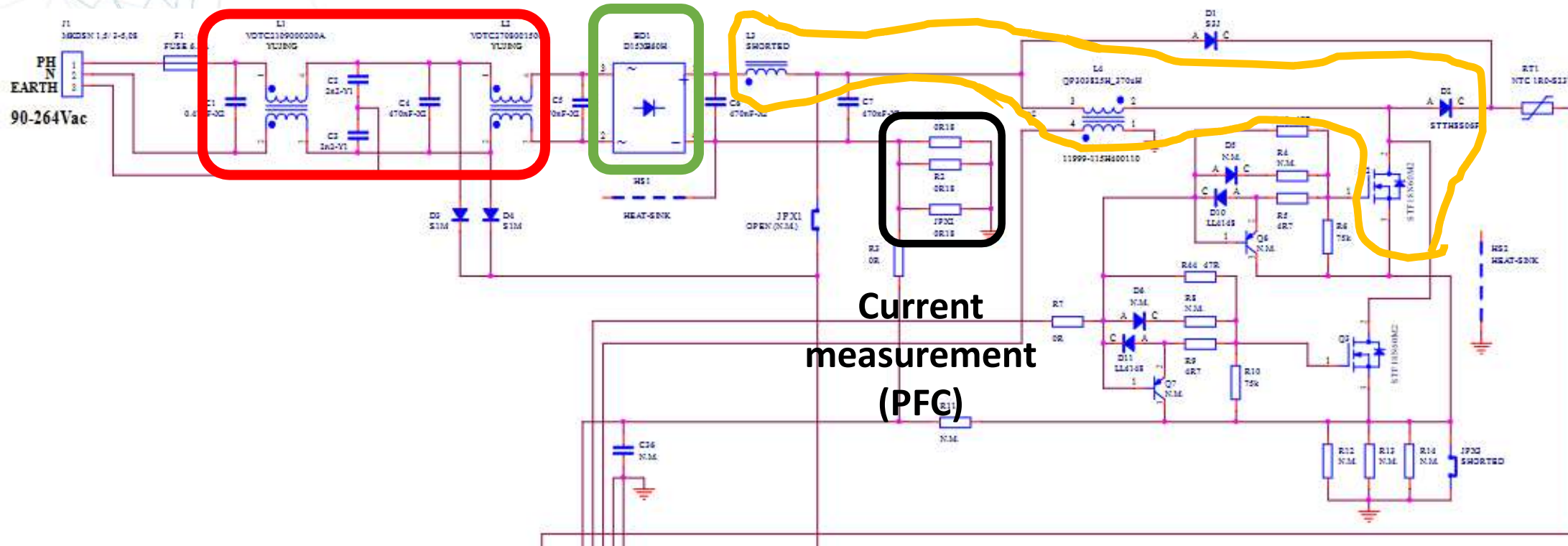


Current  
measurement  
(PFC)



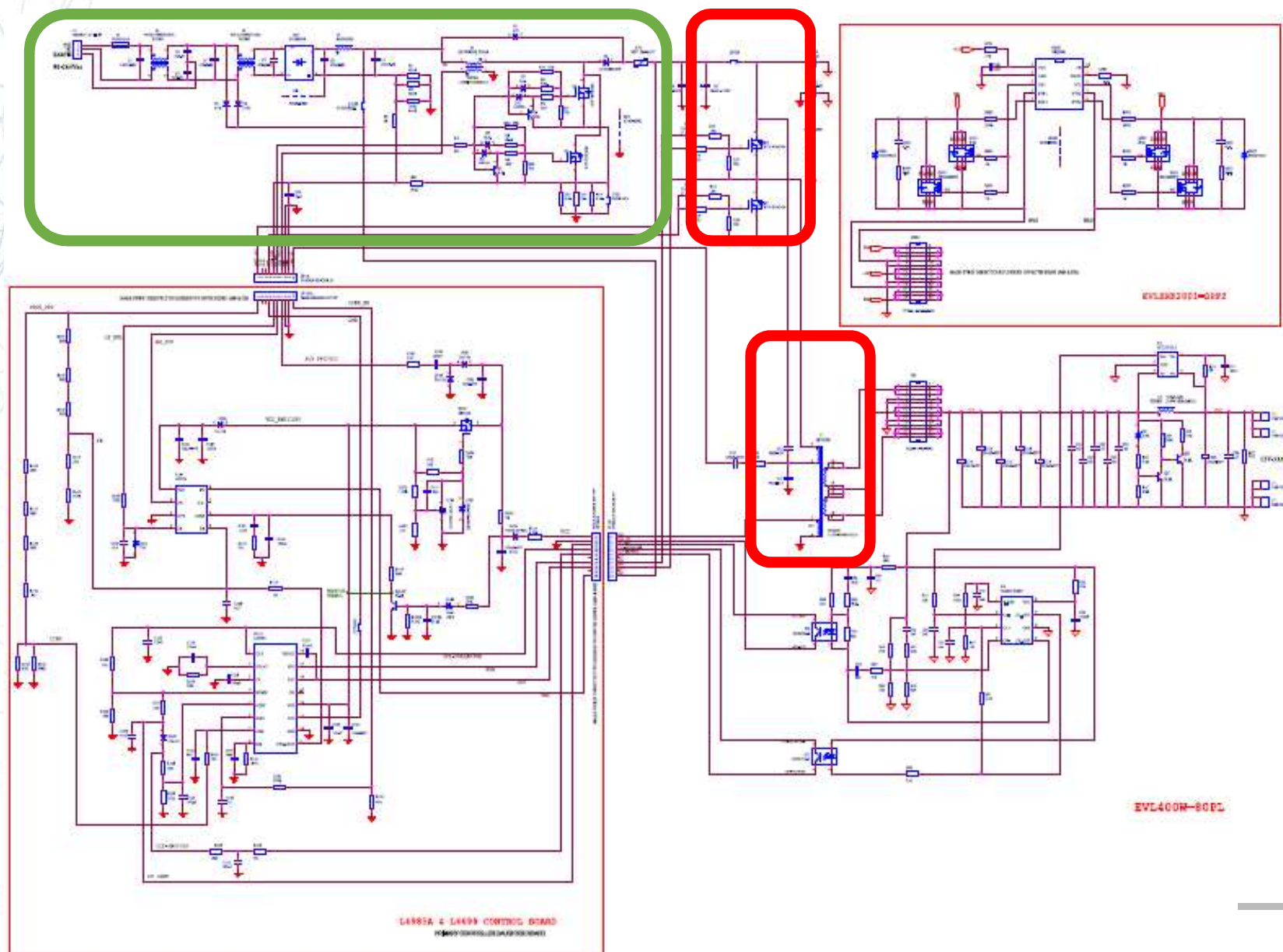


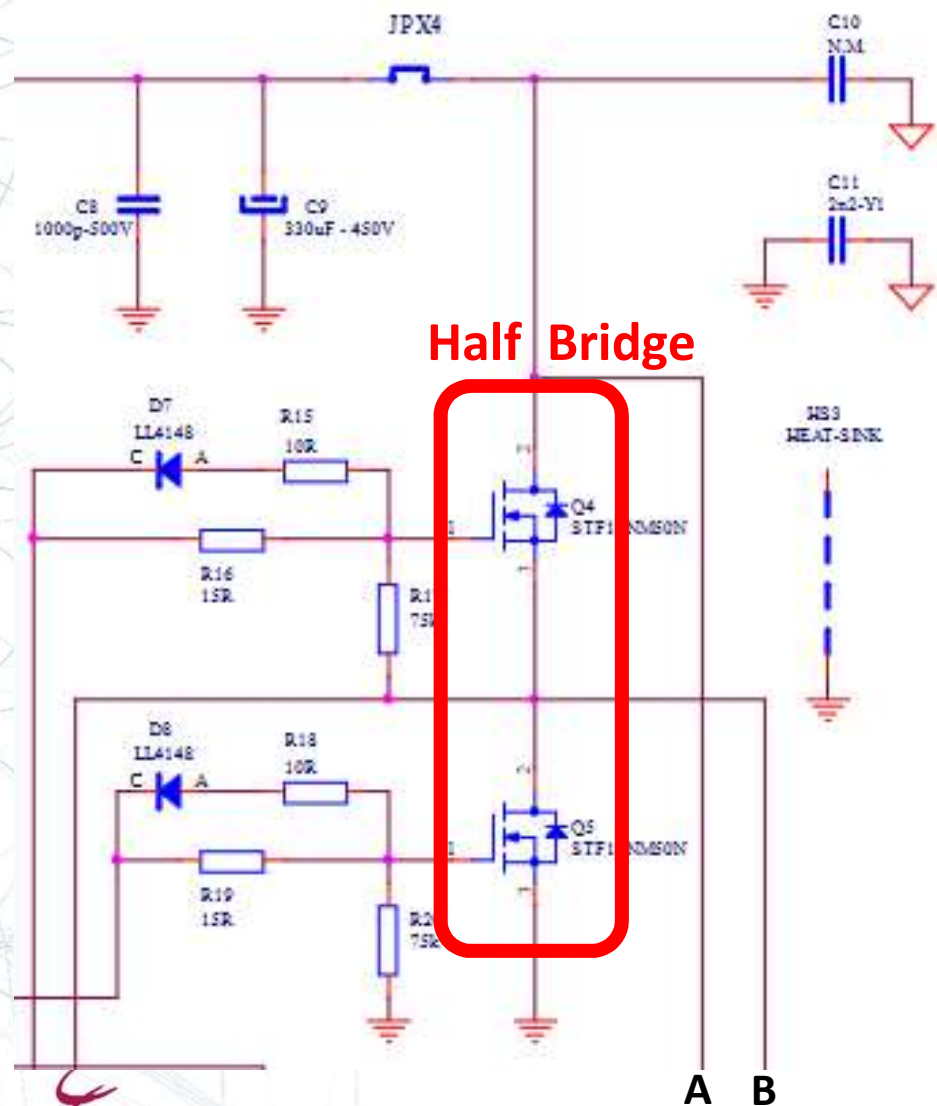


Half Bridge

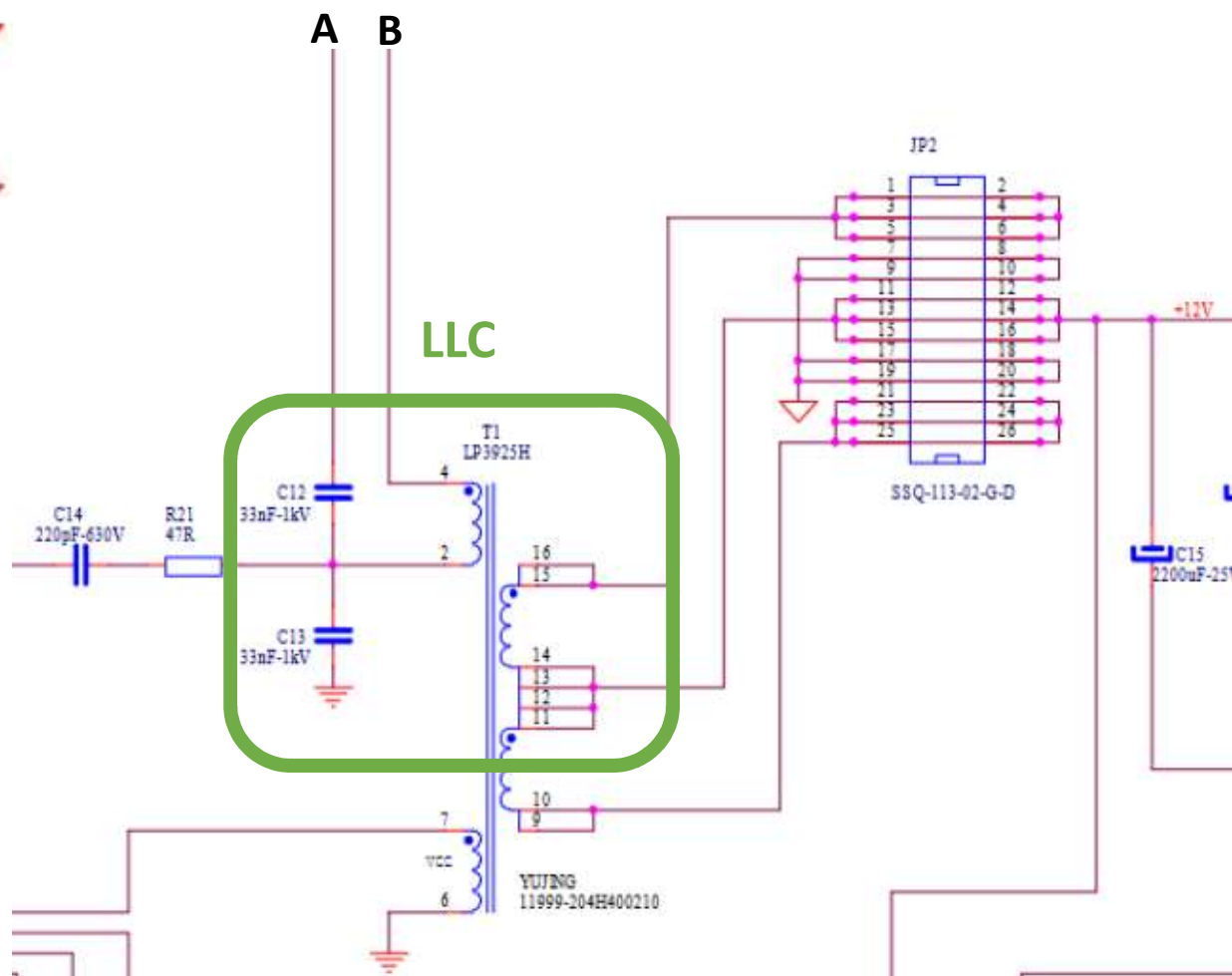


LLC

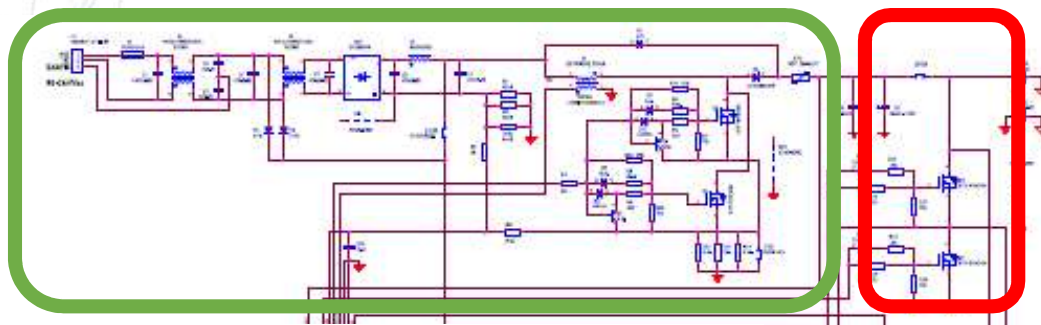


HF filtering + rectifier + Boost (PFC)

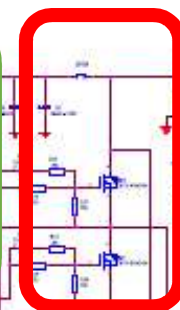

Half Bridge

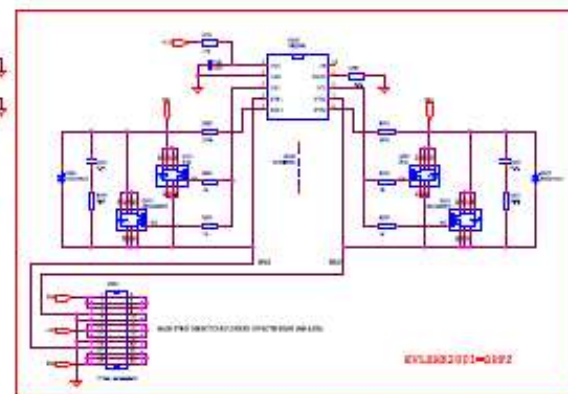



Synchronous rectifier (for LLC)

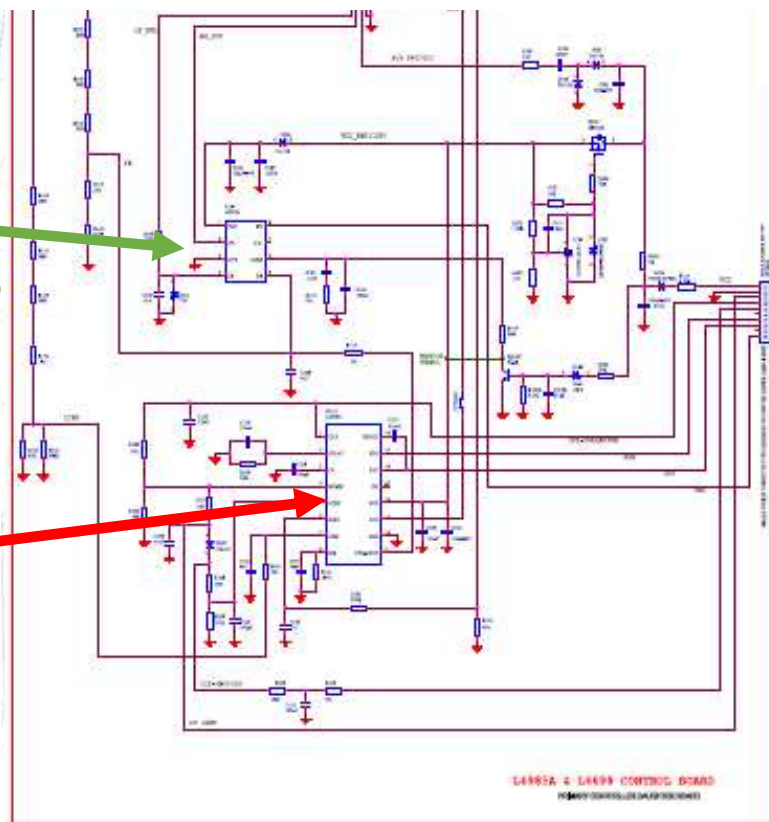


Boost (PFC) controller L4985A

Half Bridge LLC controller L6699D

LLC

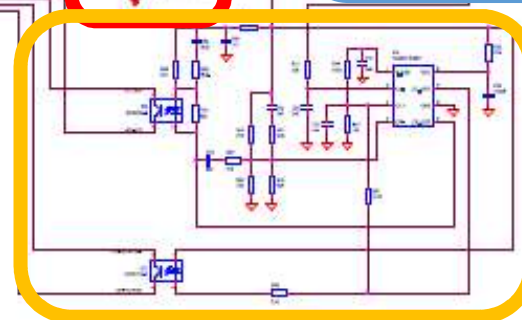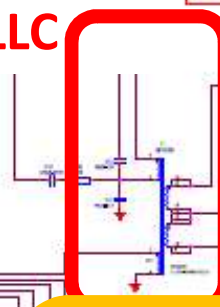

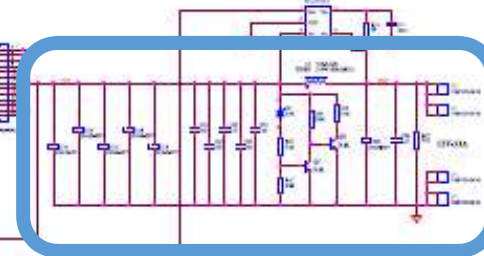Output measurement + optocoupler (isolation) for Half Bridge LLC



Output filtering





Example: EVL400W-80PL

2 transistors of Boost

Synchronous  
rectifier  
(for LLC)


Output  
filtering

Half Bridge  
LLC

Rectifier

Half Bridge controller  
+  
Boost (PFC) controller

HF input  
filtering + Boost

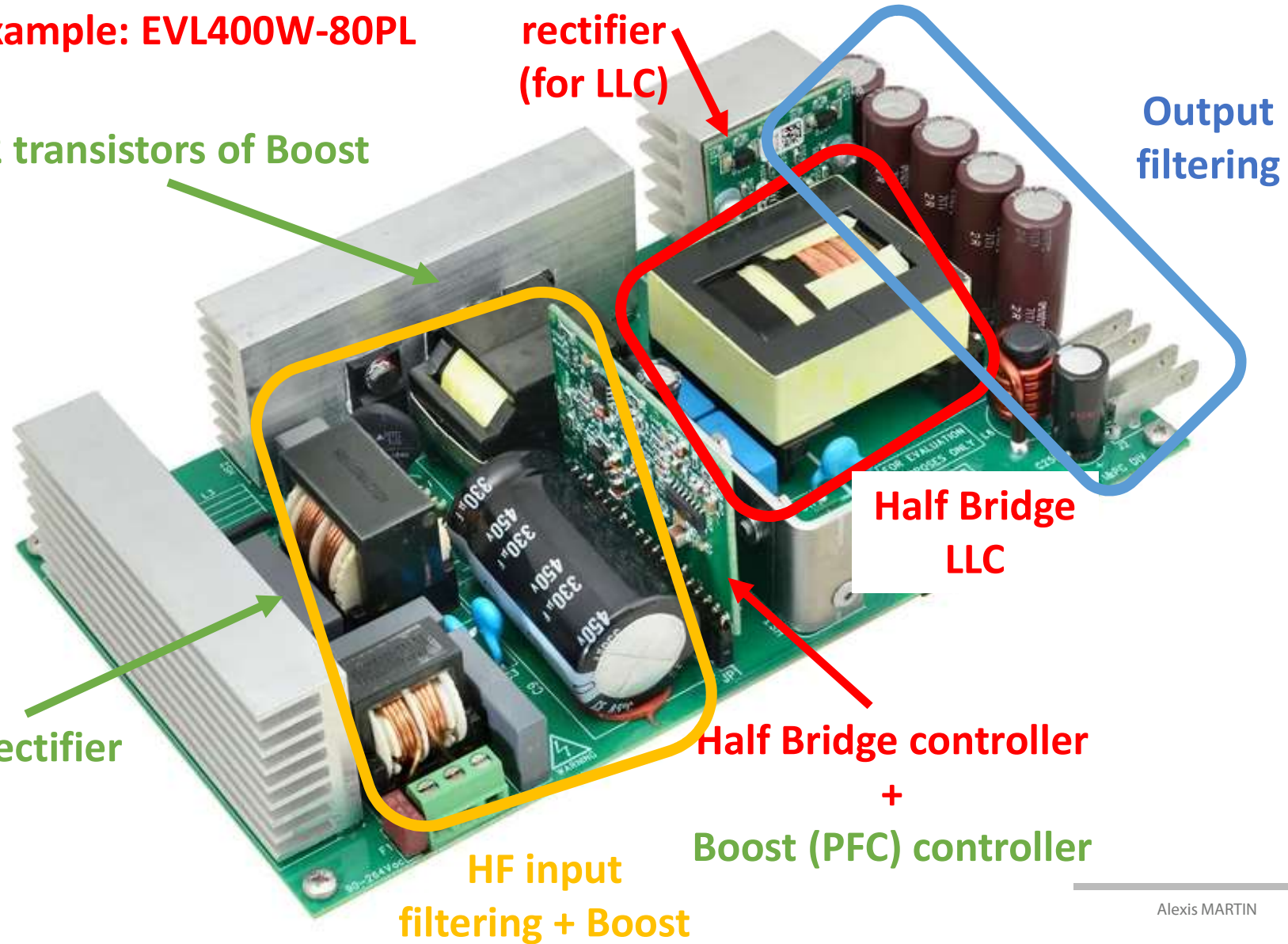



## Example: EVL400W-80PL

