



Energy Conversion I

alexis.martin@ensea.fr

Desk D216




Layout

- Non isolated choppers
 - Introduction
 - Direct conversion
 - Buck
 - Boost
 - Reversible choppers
 - Half bridge
 - H – bridge
 - Inverter
 - Energy storage based chopper
 - Buck-boost
 - Cuck
 - SEPIC
- Isolated power supplies
- Power components

Progress

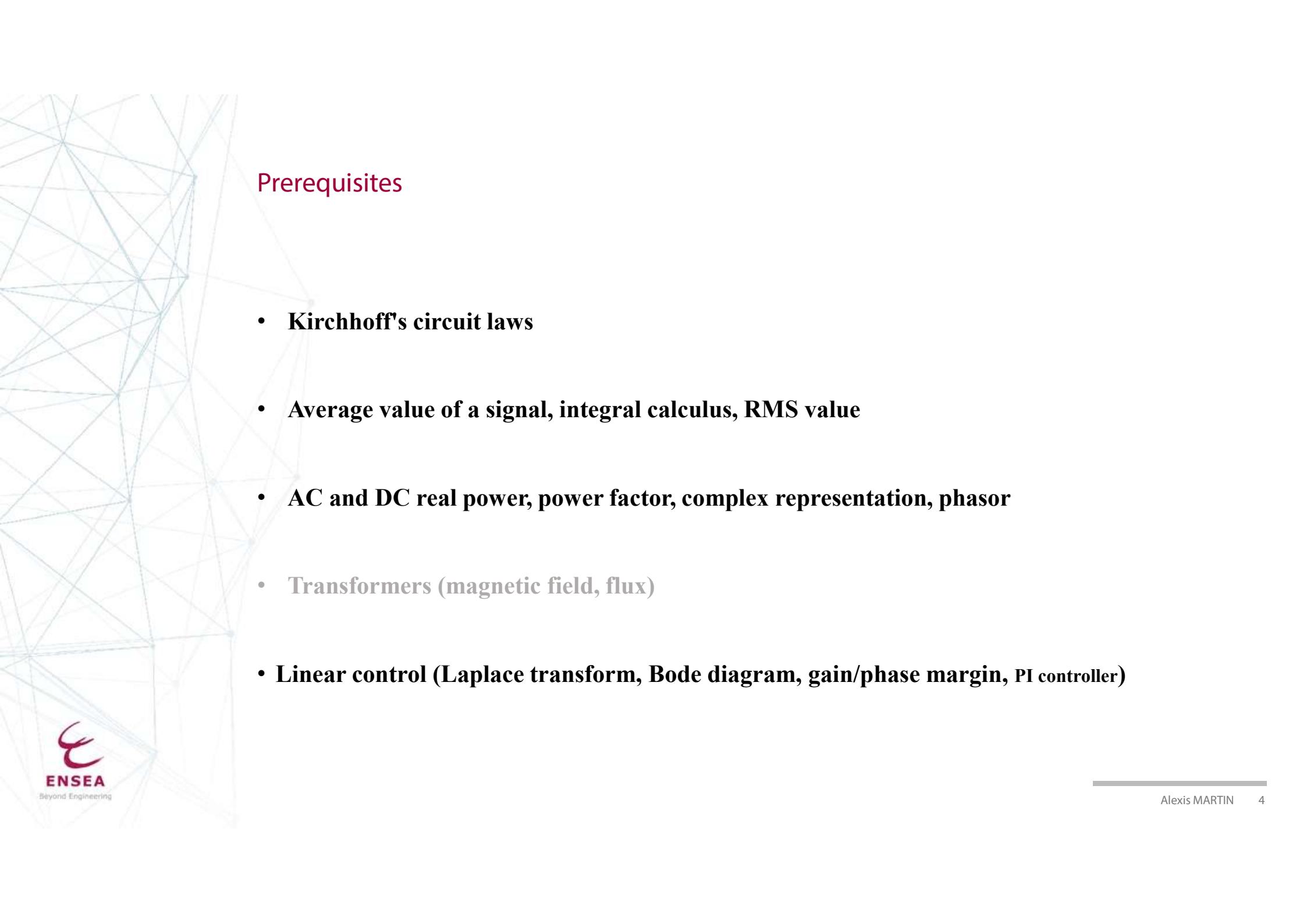- **Lesson : 8 x 2h**
- **Tutorials : 9 x 2h**
- **Labs : 4 x 4h**
 - **Buck chopper**
 - **Reversible chopper for DC motor**
 - **Switch mode power supply Flyback**
 - **Switch mode power supply Forward**
- **Marks : Final exam - Labs**



Prerequisites

- Kirchhoff's circuit laws
- Average value of a signal, integral calculus, RMS value
- AC and DC real power, power factor, complex representation, phasor
- Transformers (magnetic field, flux)
- Linear control (Laplace transform, Bode diagram, gain/phase margin, PI controller)

Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Introduction

Introduction

Direct conversion


Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Energy conversion: principles

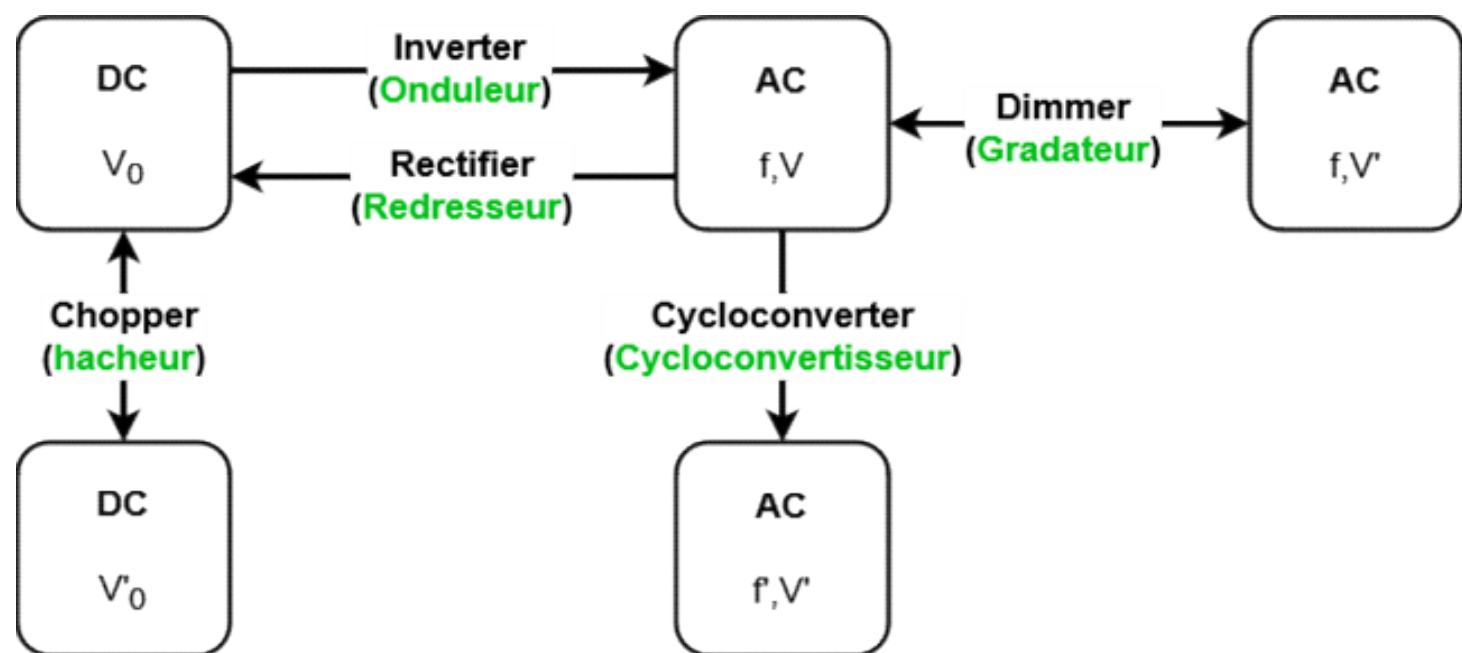

Introduction

Direct conversion


Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Micro-mechanisms

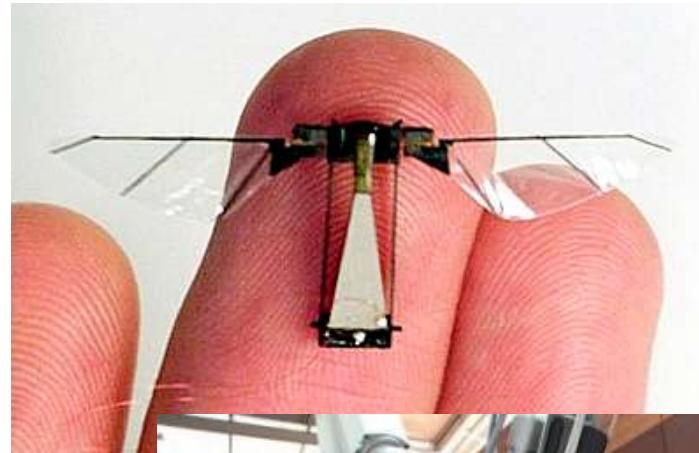

1-100 W

Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Use : automatisms



0,1 à 10 kW

Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Use : rail traction



100 kW

Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

High speed rail traction



500 kW

Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Photovoltaic plant



300 MWc

Introduction

Direct conversion


Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

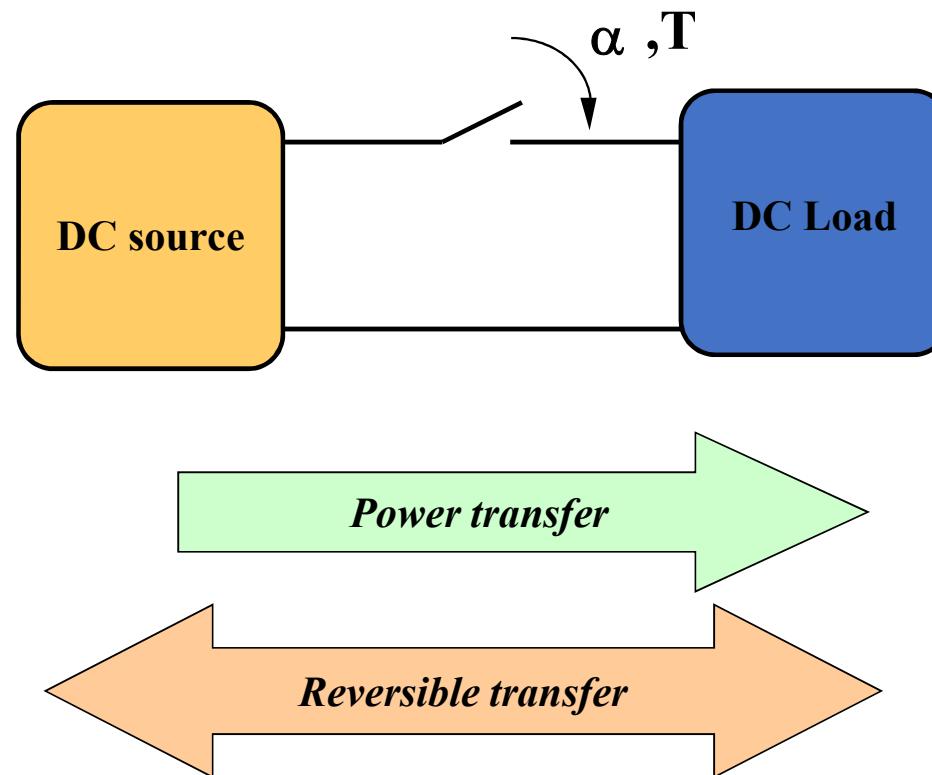«Chopper » function : a switching electronic



Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Link power sources

Voltage Source

Current Source

Active
(Energy generator)

Passive
(Energy receiver)

Theorem

**Only two sources with different category
can be directly connected.**

Introduction


Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

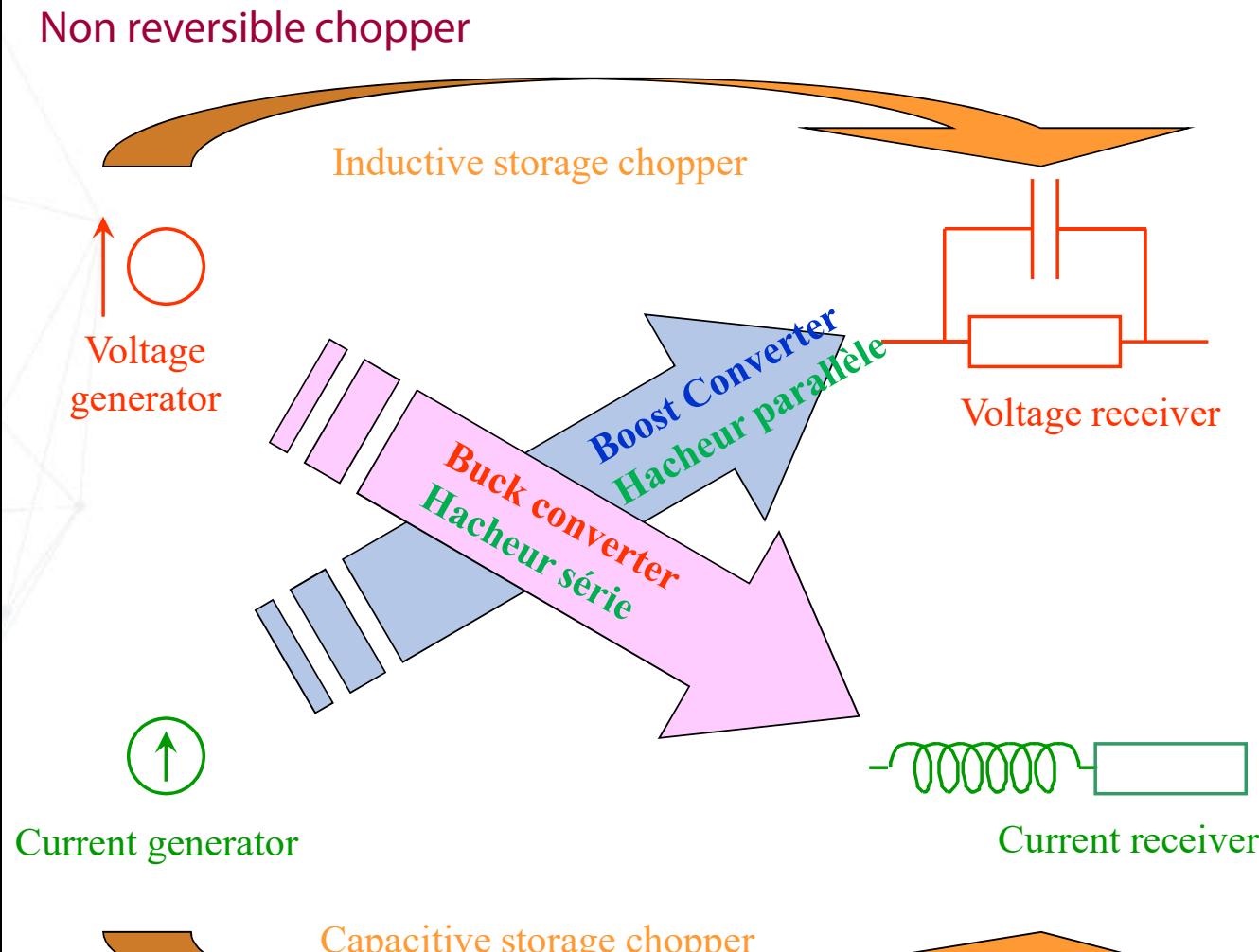

Introduction

Direct conversion



Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

« Perfect » diode

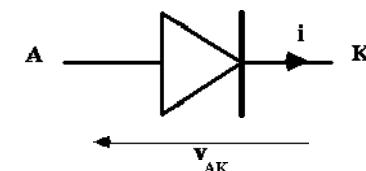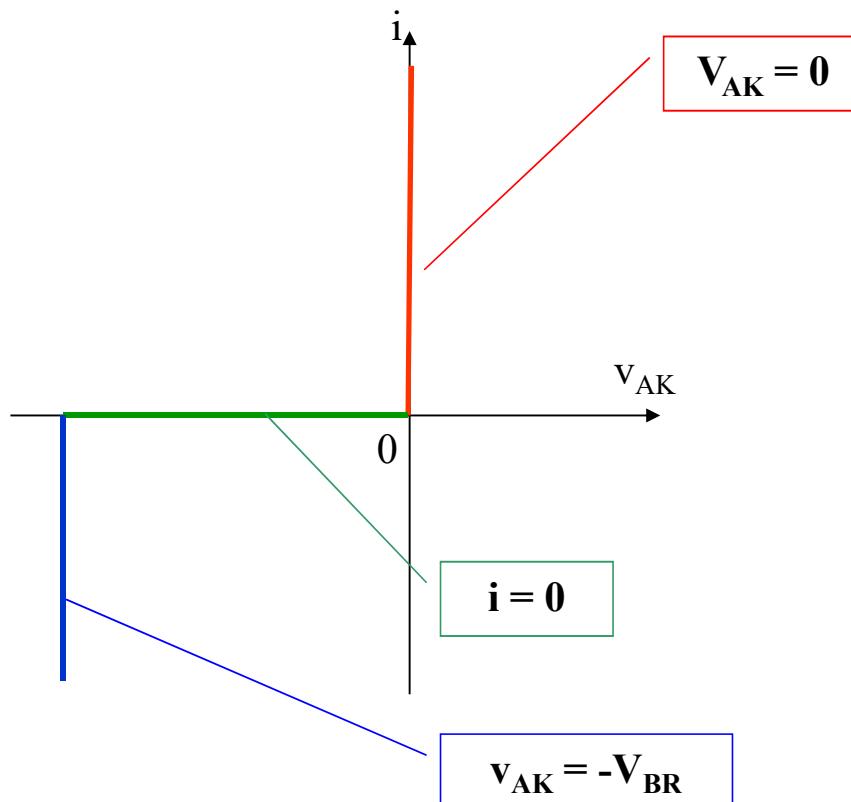

Introduction

Direct conversion

Reversible
choppers


Inverters

Closed loop
chopper control


Energy storage
based chopper

Controlled switch



MOSFET

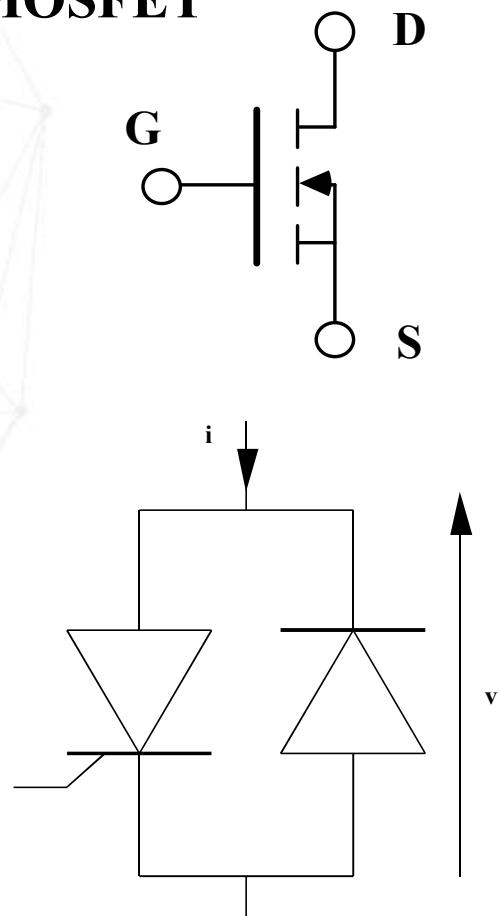

Bipolar
transistor

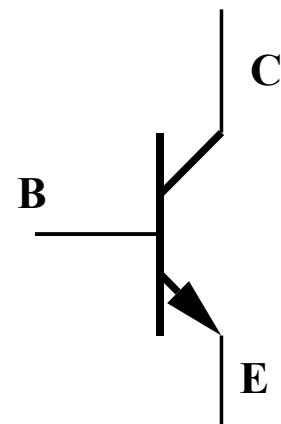

IGBT

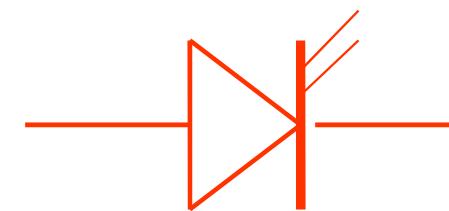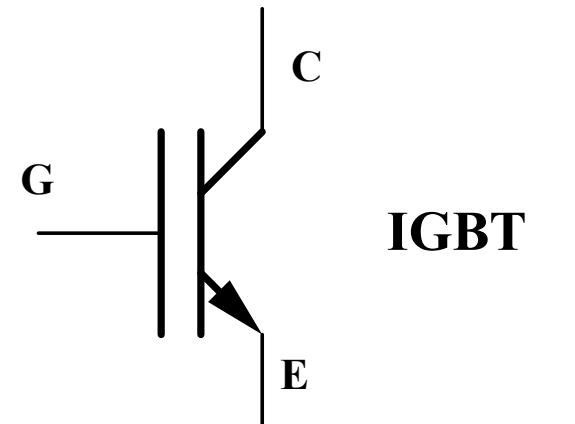

Thyristor

Introduction

Direct conversion


Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

« Perfect » controlled switch ex : IGBT

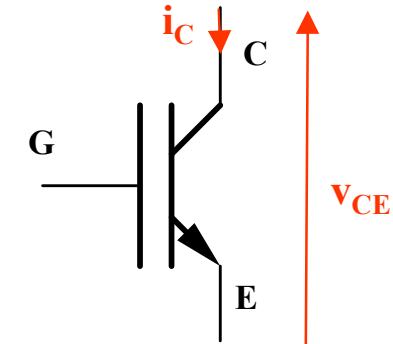

- On state: « short circuit »
 - $v_{CE} = 0$, i_C fixed by circuit
- Off state: « open circuit »
 - $i_C = 0$, v_{CE} fixed by circuit

Introduction

Direct conversion


Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Duty cycle

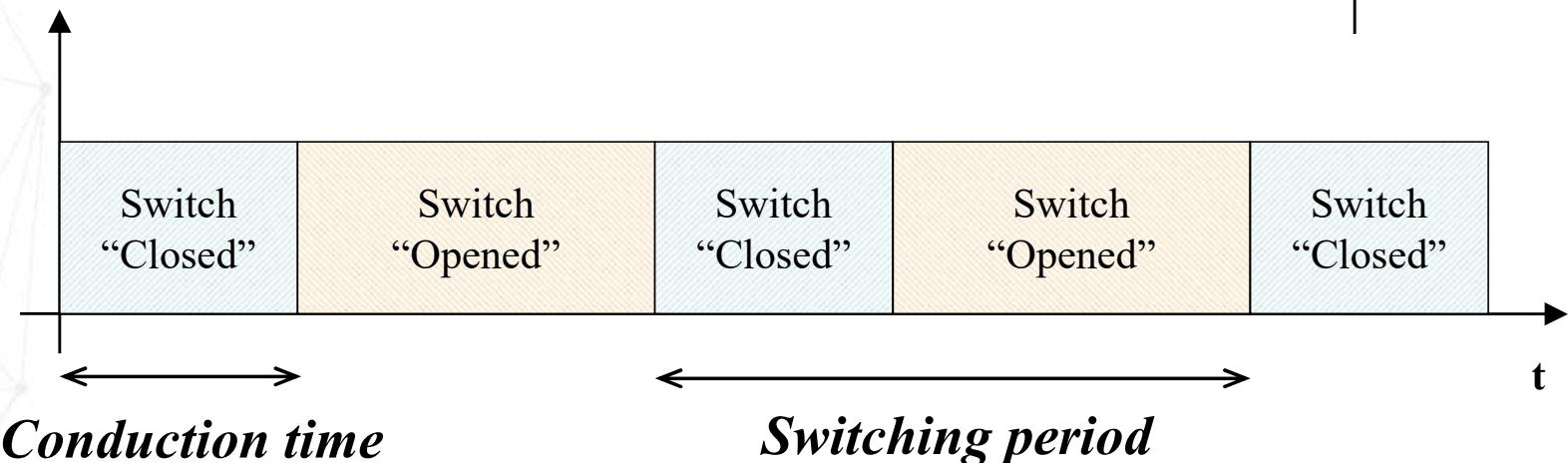

$$\alpha = \frac{\text{Conduction time}}{\text{Switching period}}$$

Introduction

Direct conversion

Buck chopper

Boost chopper

Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Buck Chopper

Introduction

Direct conversion

Buck chopper

Boost chopper


Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Buck chopper : principle

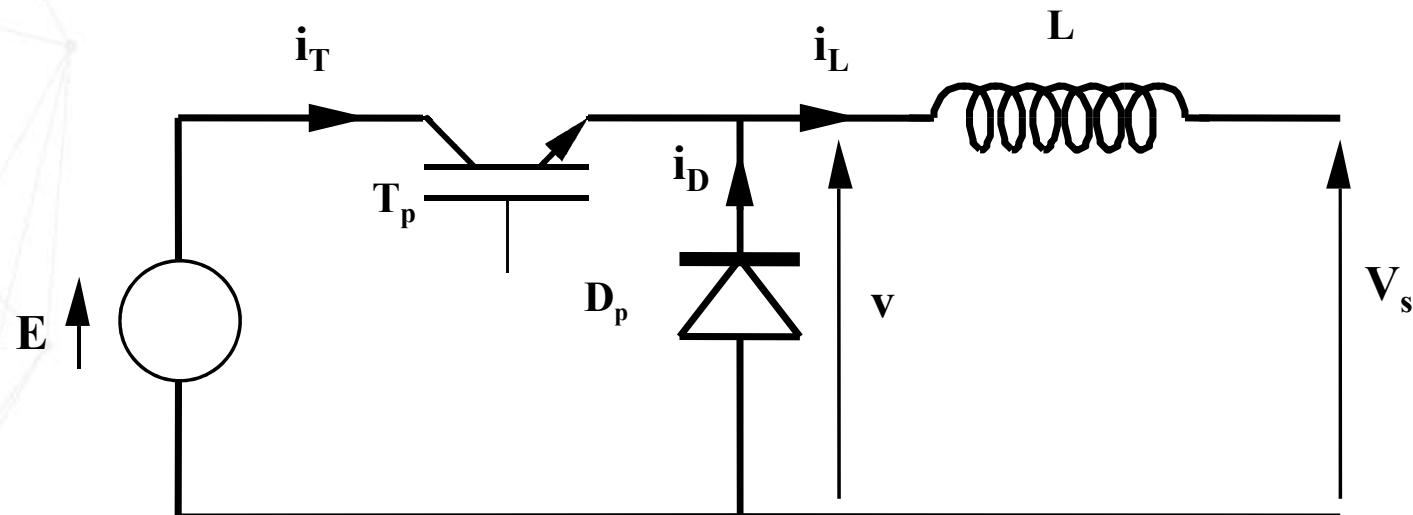

Hypothesis : $V_s = \text{constant}$

Introduction

Direct conversion

Buck chopper

Boost chopper


Reversible
choppers

Inverters


Closed loop
chopper control

Energy storage
based chopper

Control

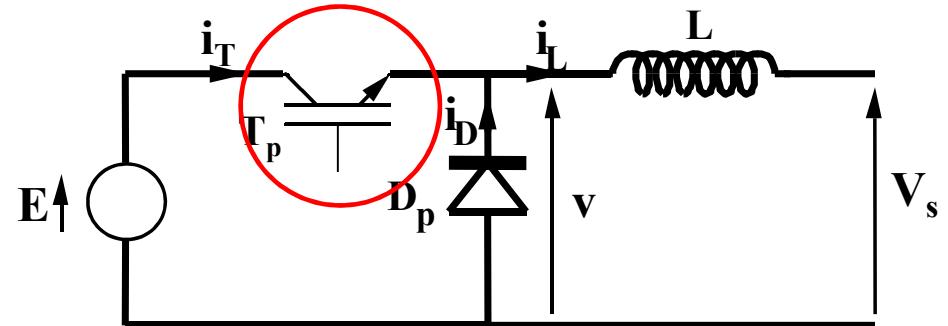

Switching period

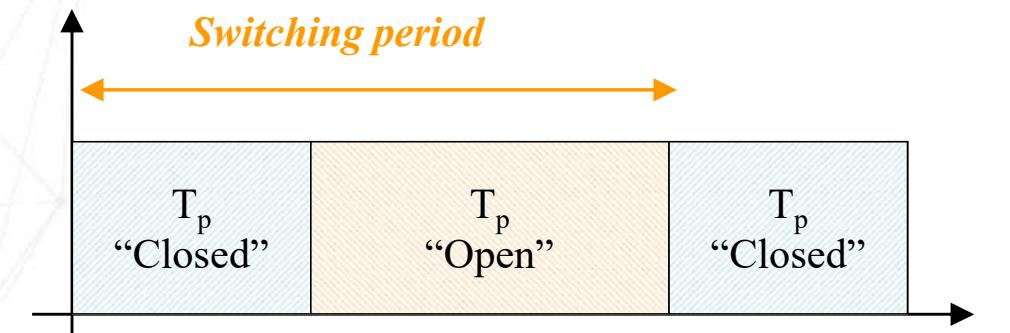

Conduction time

Introduction

Direct conversion

Buck chopper

Boost chopper


Reversible
choppers

Inverters


Closed loop
chopper control

Energy storage
based chopper

Operation

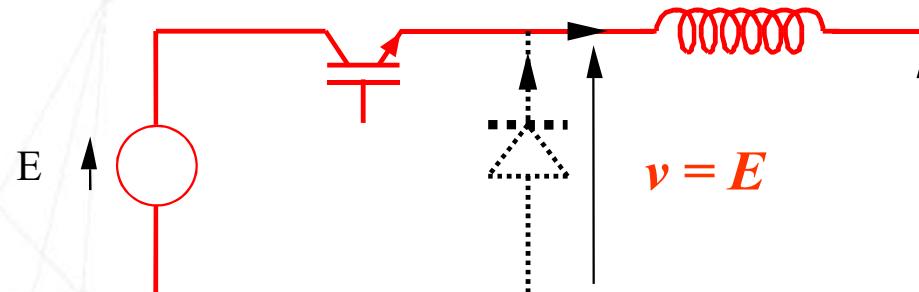

$$0 < t < \alpha T$$

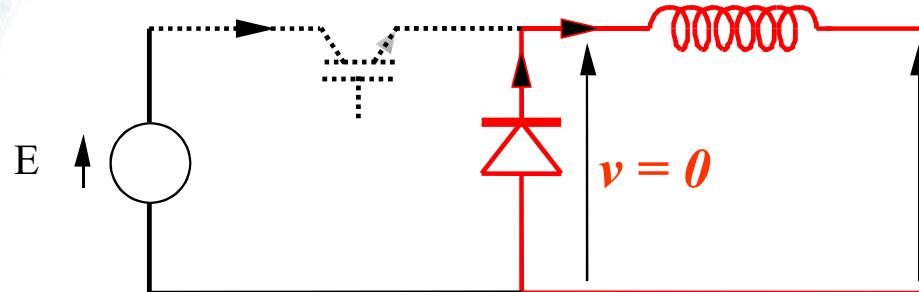

$$\alpha T < t < T$$

Introduction

Direct conversion

Buck chopper

Boost chopper

Reversible
choppers


Inverters

Closed loop
chopper control

Energy storage
based chopper

Modes

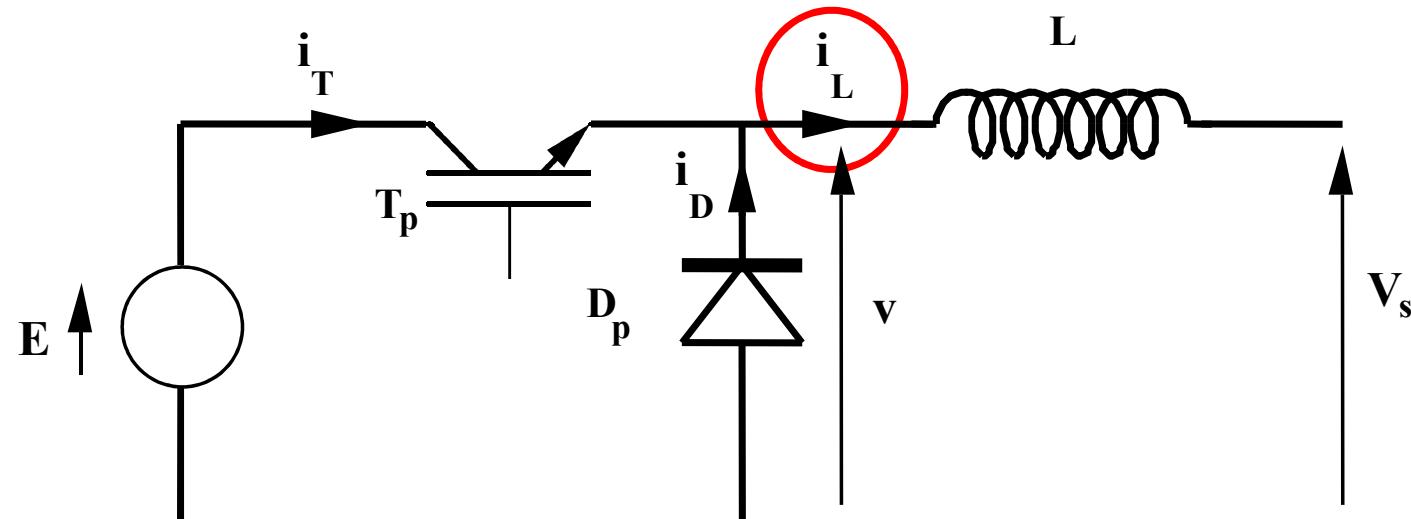- *Continuous conduction mode: $i_L > 0$*



- *Discontinuous conduction mode: $i_L(t_0) = 0 ; t_0 < T$*

Introduction

Direct conversion

Buck chopper

Boost chopper


Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Continuous mode

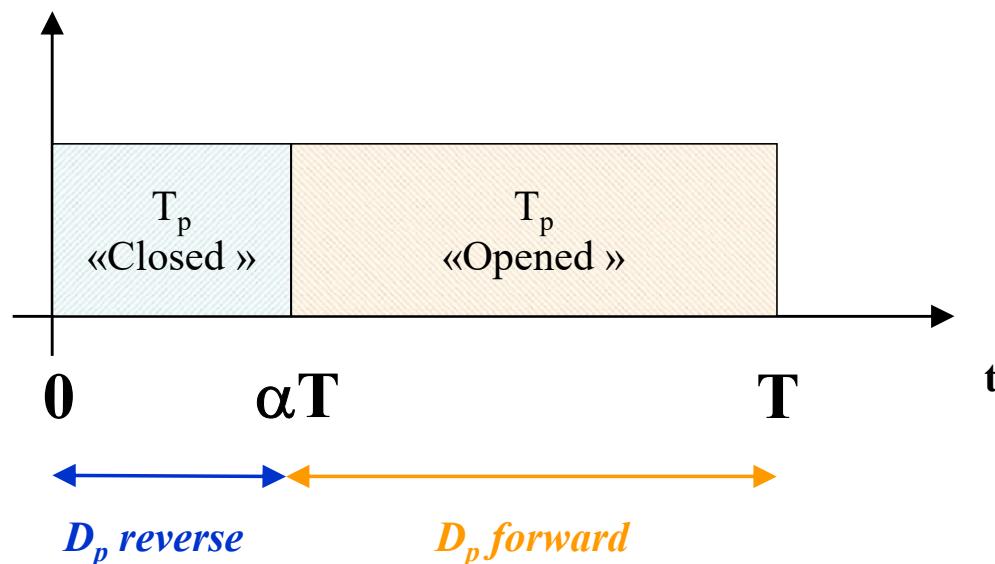

Introduction

Direct conversion

Buck chopper

Boost chopper



Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Continuous mode: Chronograms

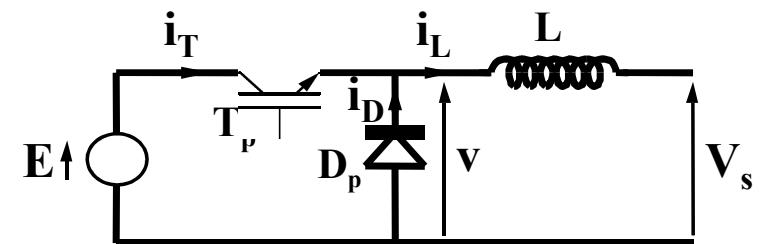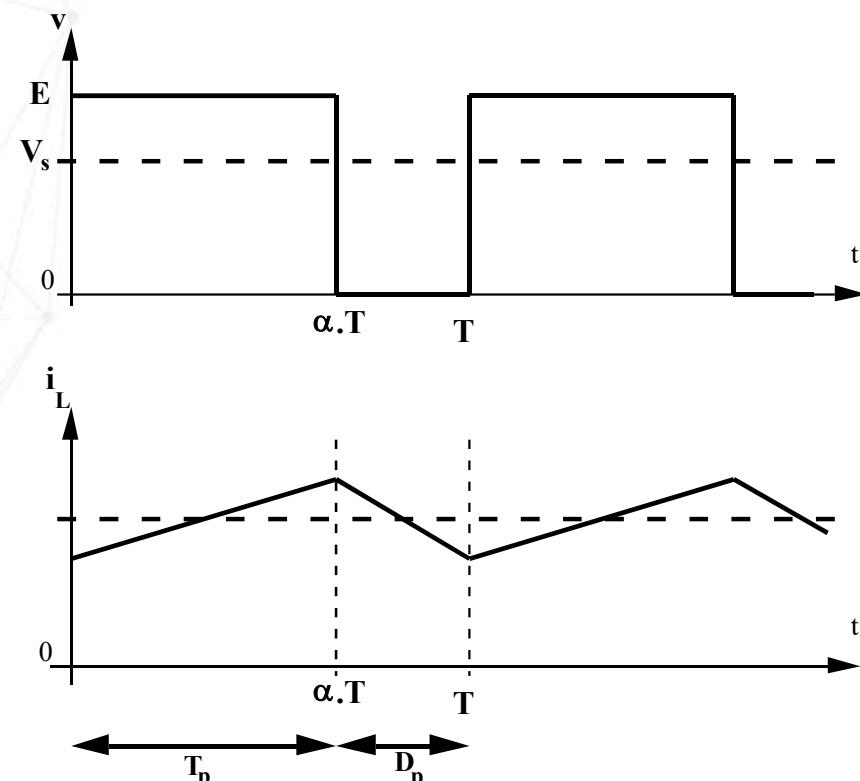

- $0 < t < \alpha T$

$$\frac{di}{dt} = \frac{E - V_s}{L}$$

- $\alpha T < t < T$

$$\frac{di}{dt} = -\frac{V_s}{L}$$

$E > V_s$

Introduction

Direct conversion

Buck chopper

Boost chopper

Reversible
choppers


Inverters

Closed loop
chopper control

Energy storage
based chopper


Continuous mode (Calculation)

Output voltage

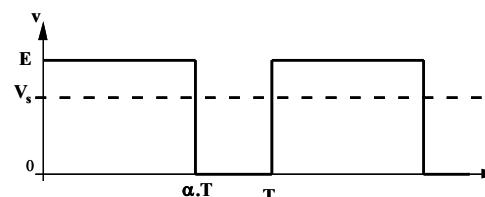

$$\langle v \rangle = \alpha \cdot E = V_s$$


Current ripple i_L

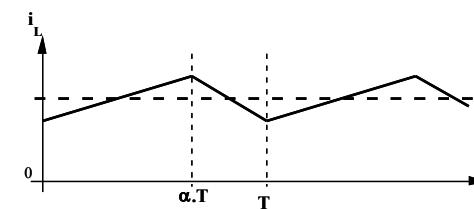

$$\Delta I_L = \alpha \cdot (1 - \alpha) \cdot \frac{E \cdot T}{L}$$

Maximum ripple
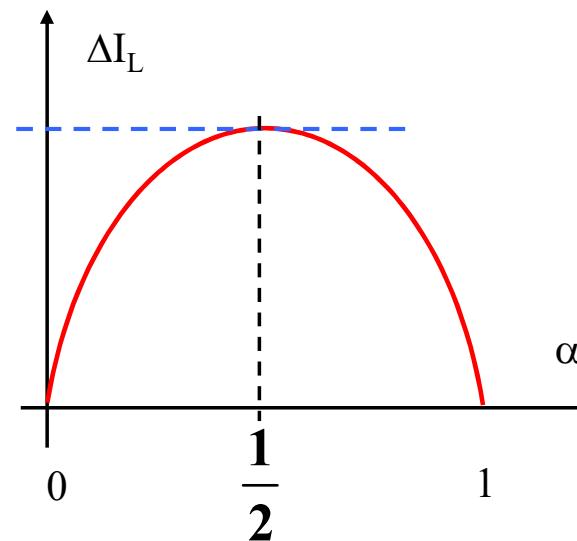
$$\Delta I_{L max} = \frac{E \cdot T}{4 L}$$



Introduction

Direct conversion

Buck chopper

Boost chopper


Reversible
choppers

Inverters


Closed loop
chopper control

Energy storage
based chopper

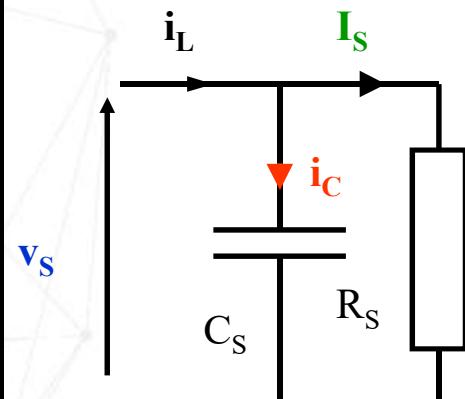Continuous mode: Output filtering principle



$$i_C = C_s \cdot \frac{dv_s}{dt}$$

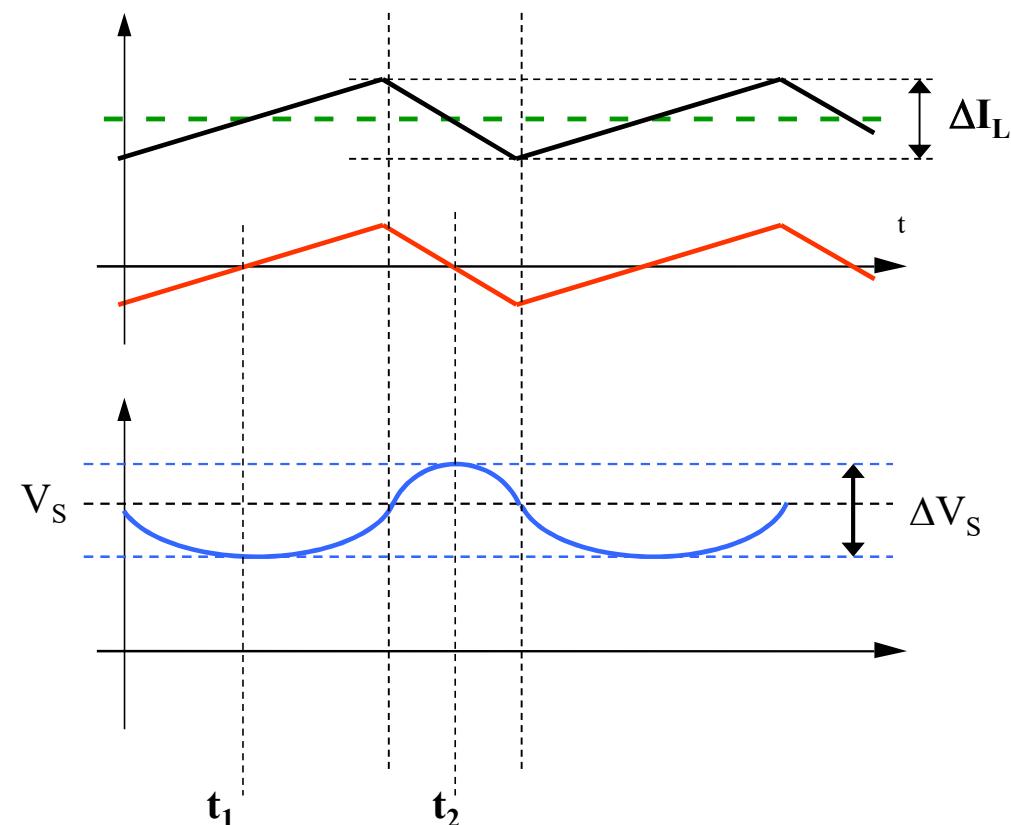

Introduction

Direct conversion

Buck chopper

Boost chopper

Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper


Continuous mode: Output filtering calculation

$$t_1 = \alpha \frac{T}{2}$$


$$t_2 = \frac{(1+\alpha).T}{2}$$

$$\Delta I_L = \alpha \cdot (1 - \alpha) \cdot \frac{E \cdot T}{L}$$

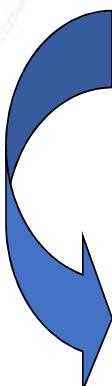
$$\Delta V_S = \frac{1}{C_S} \cdot \int_{t_1}^{t_2} i_C(t) \cdot dt = \frac{1}{C_S} \cdot \frac{1}{2} \cdot \frac{\Delta I_L}{2} \cdot (t_2 - t_1) = \frac{\Delta I_L \cdot T}{8 \cdot C_S}$$


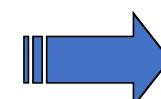
$$C_S = \frac{\alpha(1 - \alpha) \cdot E \cdot T^2}{8 \cdot L \cdot \Delta V_S}$$



C_S

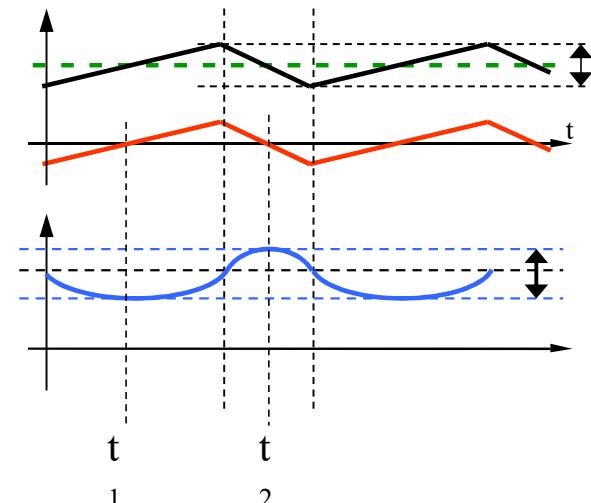

Introduction

Direct conversion

Buck chopper

Boost chopper



Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper


Boundary mode

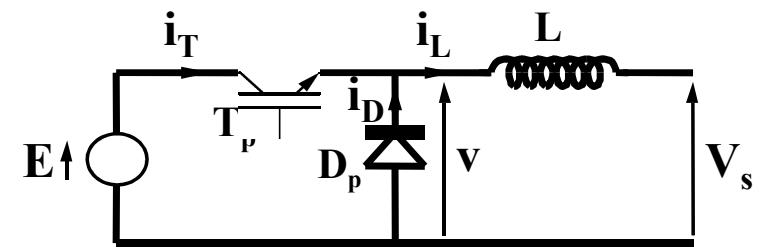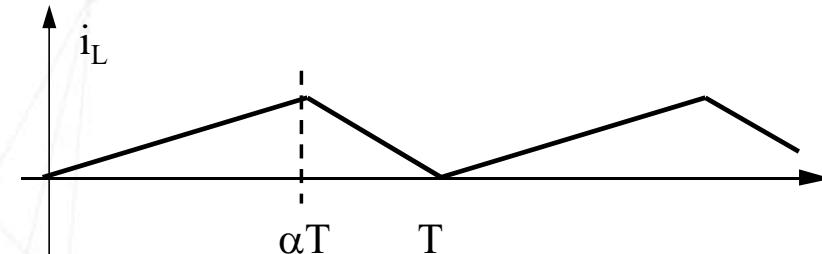

$$i_L(T) = 0$$

$$\langle I_L \rangle = \frac{1}{2} \cdot \left(\frac{E - V_s}{L} \cdot \alpha T \right) = \frac{1}{2} \cdot \frac{\alpha(1-\alpha) \cdot E \cdot T}{L}$$

$$V_s = \alpha \cdot E$$

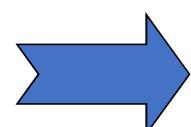

$$\boxed{\langle I_L \rangle = \frac{T}{2L} \cdot V_s \left(1 - \frac{V_s}{E} \right)}$$

Curve of mode separation (Vs, Is)

Introduction

Direct conversion

Buck chopper

Boost chopper


Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Discontinuous mode

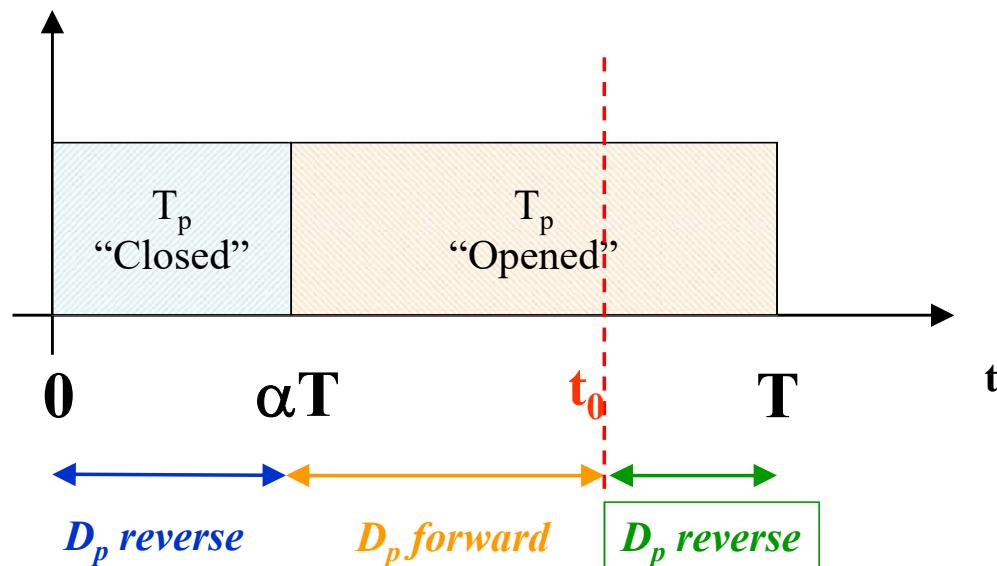

At $t_0 = \alpha \cdot T$: diode switches to reverse mode

Introduction

Direct conversion

Buck chopper

Boost chopper



Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Discontinuous mode: Chronograms

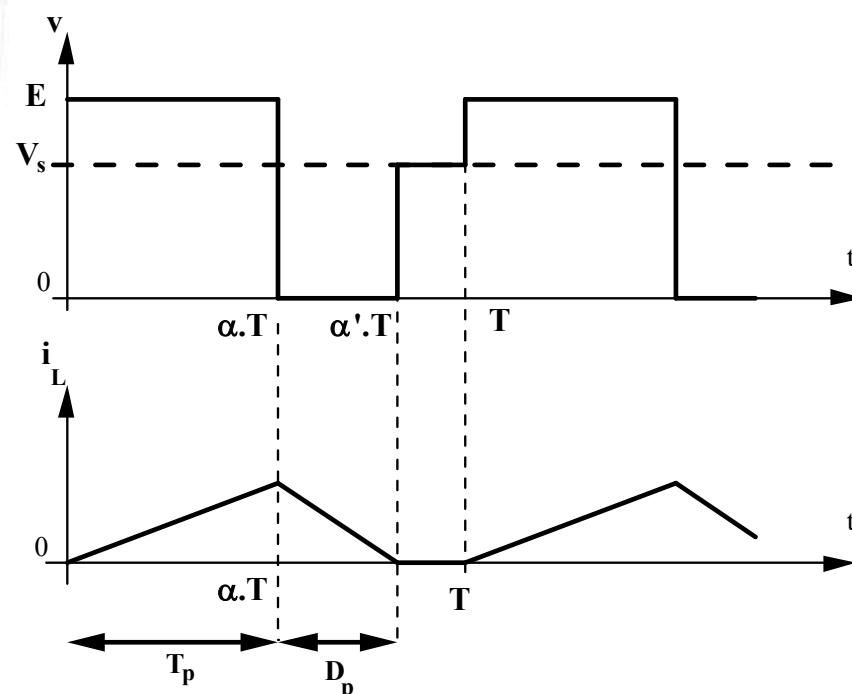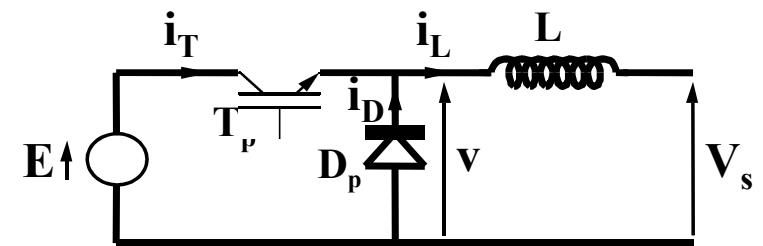

Introduction

Direct conversion

Buck chopper

Boost chopper


Reversible
choppers

Inverters

Closed loop
chopper control


Energy storage
based chopper

Discontinuous mode: calculation

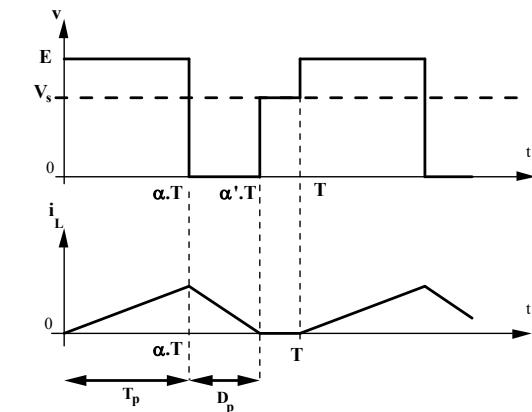

$$I_{max} = \frac{E - V_s}{L} \cdot \alpha T = \frac{V_s}{L} \cdot (\alpha' T - \alpha T) \quad \rightarrow \quad \frac{\alpha}{\alpha'} = \frac{V_s}{E}$$

$$\langle I_L \rangle = \frac{1}{2} \cdot I_{max} \cdot \alpha' = \frac{E - V_s}{2L} \cdot \alpha \cdot \alpha' \cdot T = \frac{\alpha \cdot E \cdot T}{2L} (\alpha' - \alpha) \quad \rightarrow \quad \alpha' = \alpha + \frac{2L \cdot \langle I_L \rangle}{\alpha \cdot E \cdot T}$$

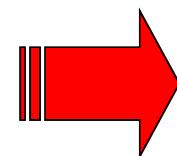
$$V_s = \frac{\alpha \cdot E}{\alpha + \frac{2L \cdot \langle I_L \rangle}{\alpha \cdot E \cdot T}}$$

Output current: $\langle I_L \rangle = I_S$

Introduction

Direct conversion

Buck chopper

Boost chopper

Reversible
choppers


Inverters

Closed loop
chopper control

Energy storage
based chopper

Output characteristics
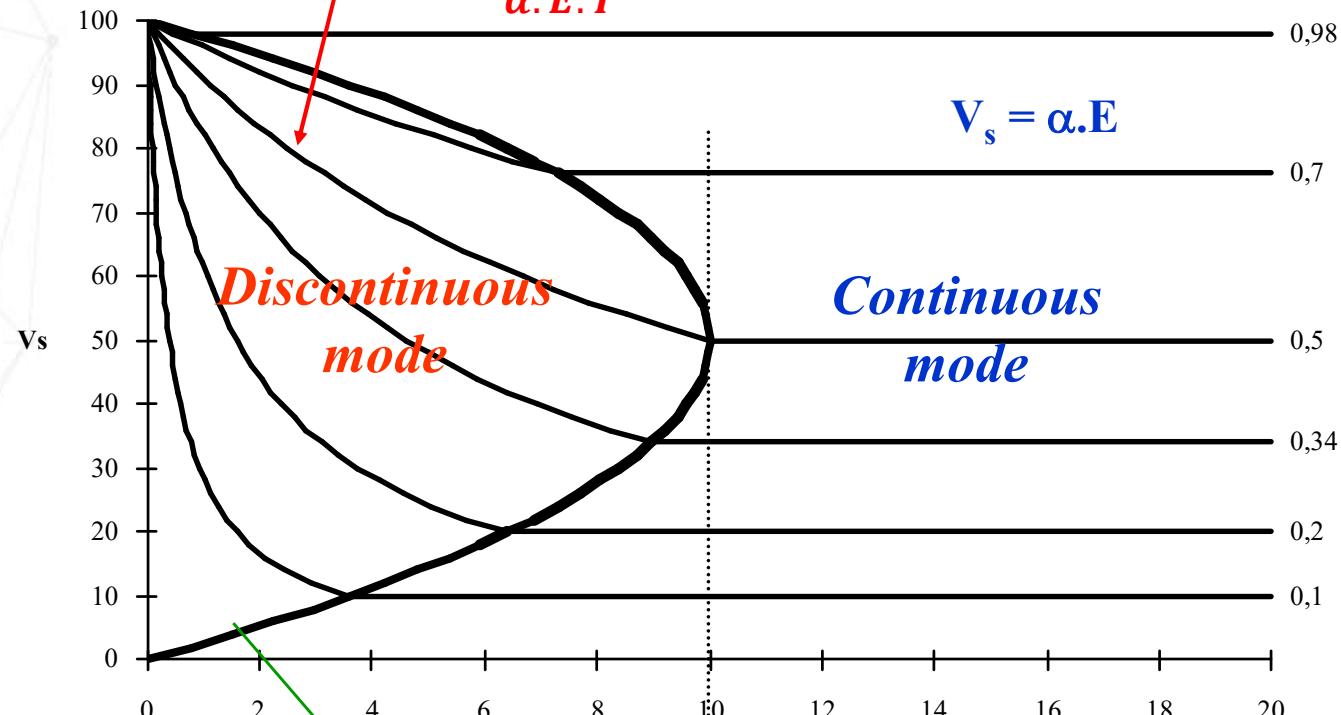
$$V_s = \frac{\alpha \cdot E}{\alpha + \frac{2L \cdot \langle I_L \rangle}{\alpha \cdot E \cdot T}}$$



$$\langle I_{Lmode} \rangle_{max} = \frac{E \cdot T}{8L}$$

Introduction

Direct conversion

Buck chopper

Boost chopper


Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Example

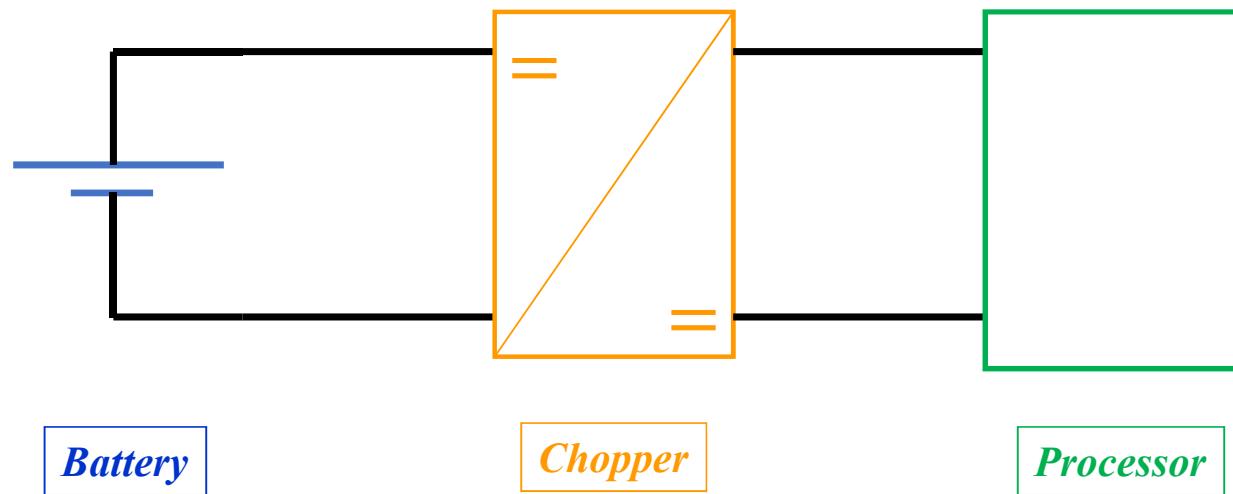

=> DC supply from battery

Introduction

Direct conversion

Buck chopper

Boost chopper


Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Example : LM3489

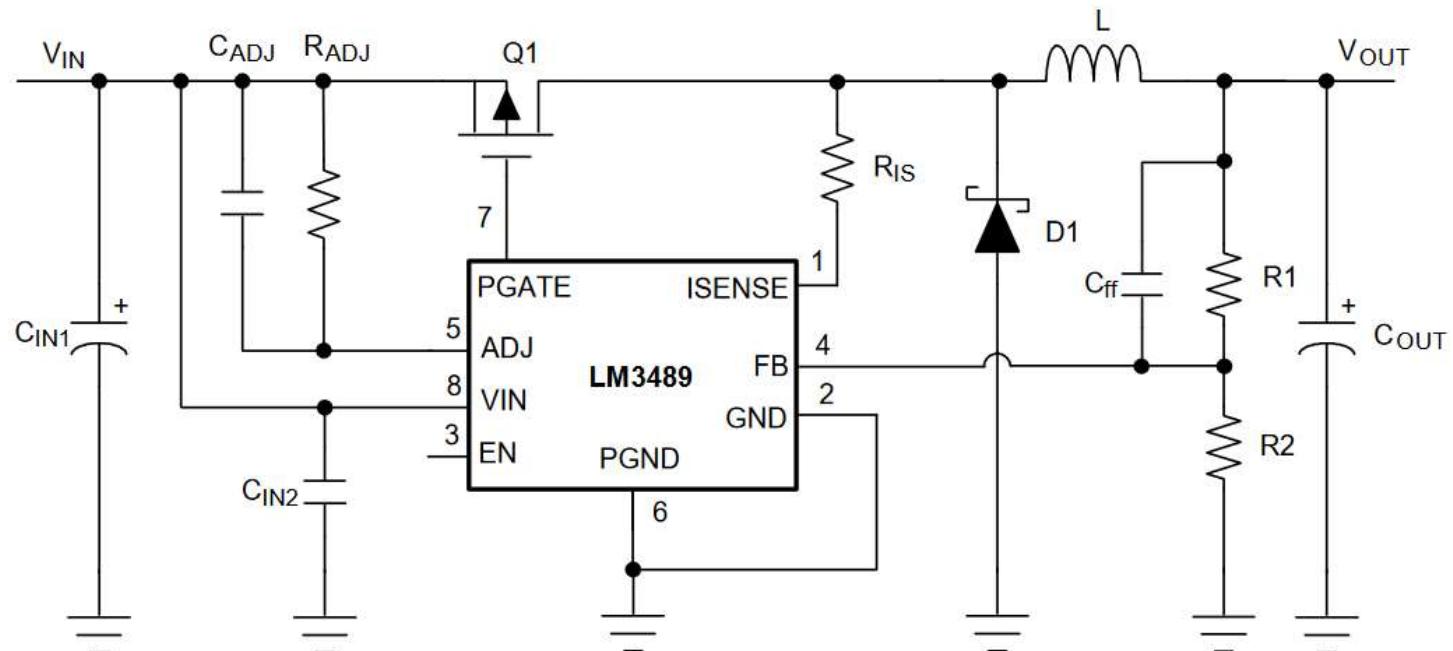

Copyright © 2016, Texas Instruments Incorporated

Introduction

Direct conversion

Buck chopper

Boost chopper



Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Example : LM3489

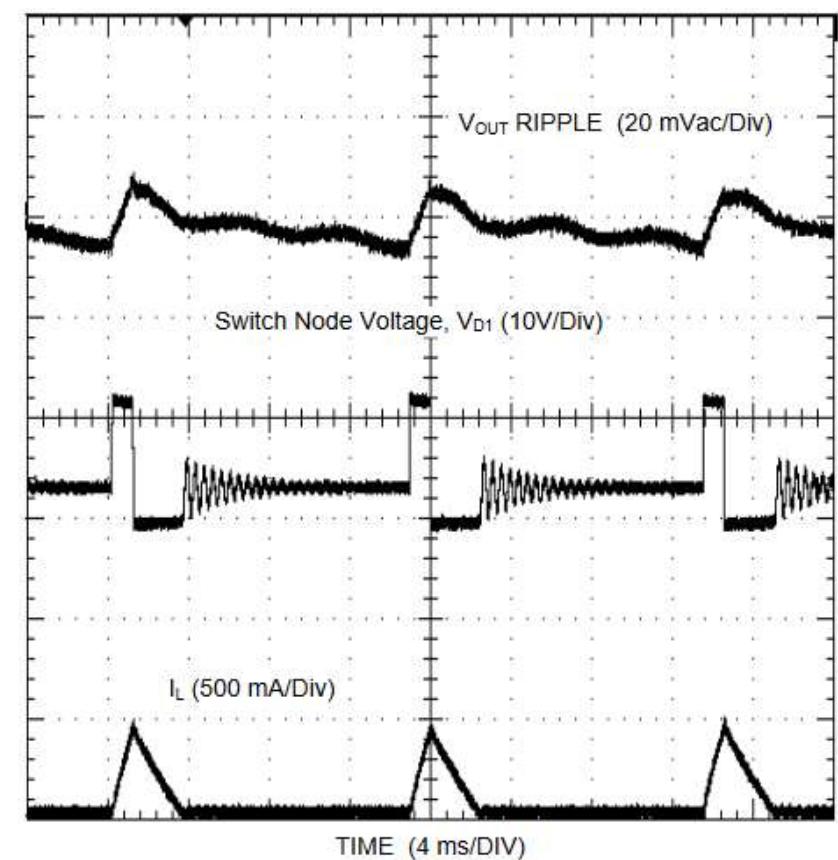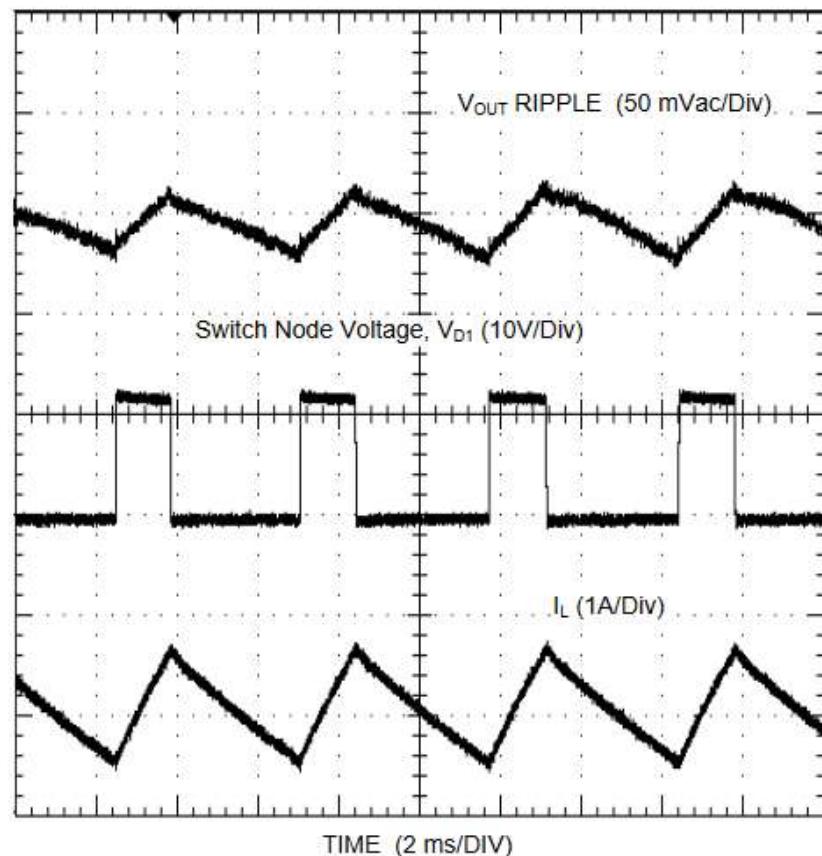

Introduction

Direct conversion

Buck chopper

Boost chopper


Reversible
choppers

Inverters


Closed loop
chopper control

Energy storage
based chopper

Example : LM3489

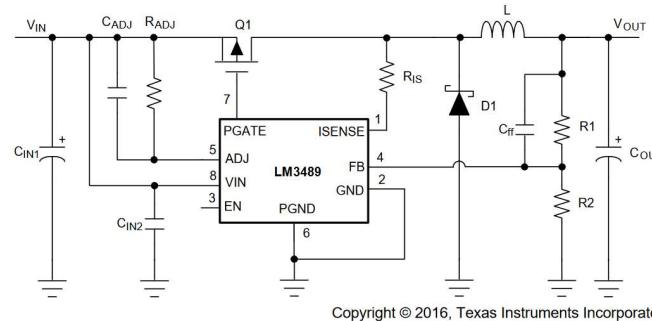

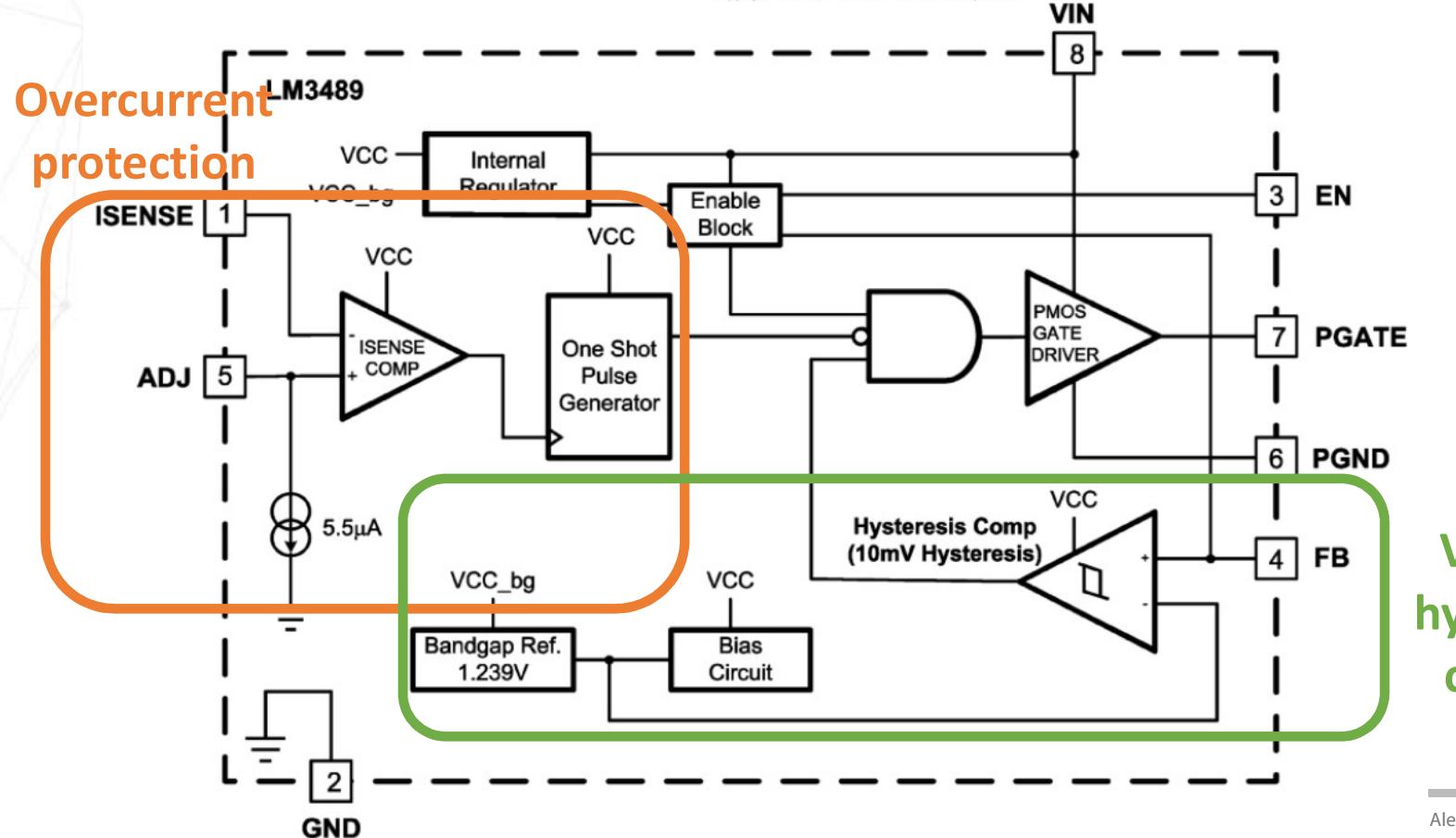Copyright © 2016, Texas Instruments Incorporated



Voltage
hysteresis
control

Introduction

Direct conversion

Buck chopper

Boost chopper


Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Example : A7985A

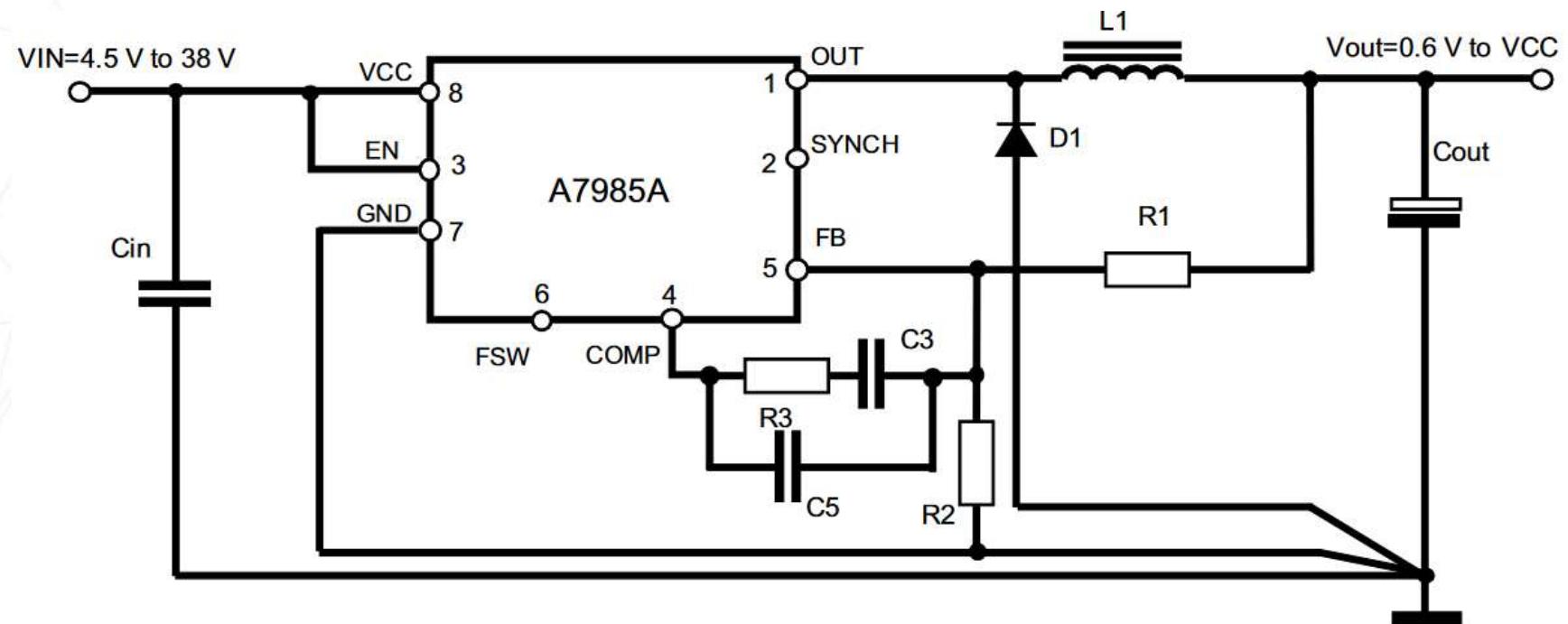

Introduction

Direct conversion

Buck chopper

Boost chopper



Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Example : A7985A

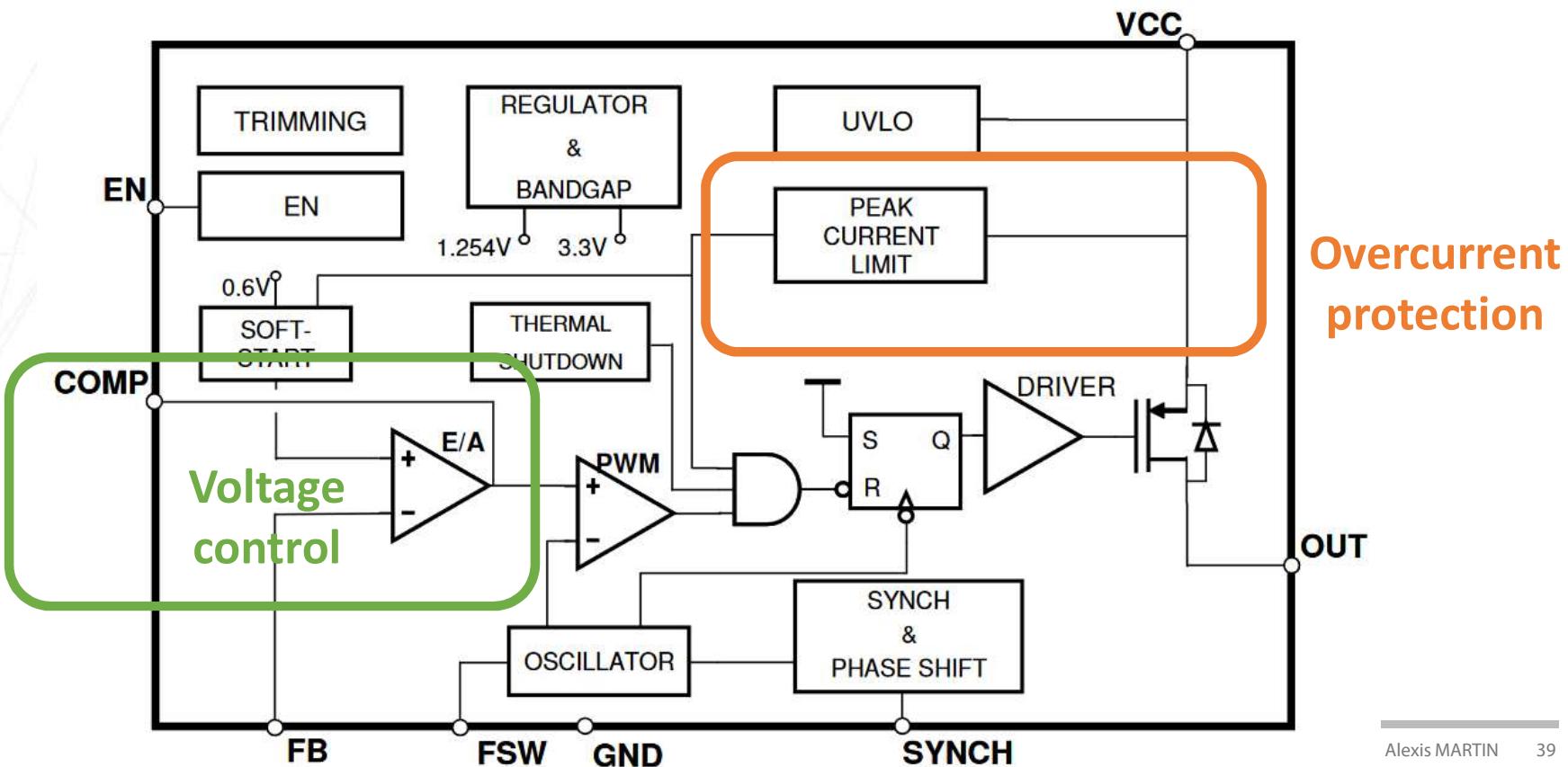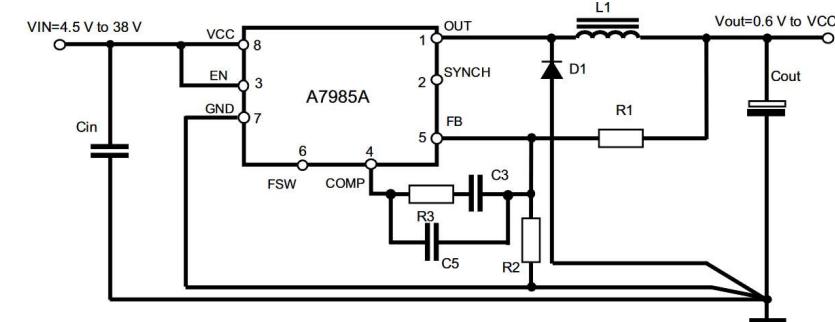

Introduction

Direct conversion

Buck chopper

Boost chopper


Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Example : A7985A

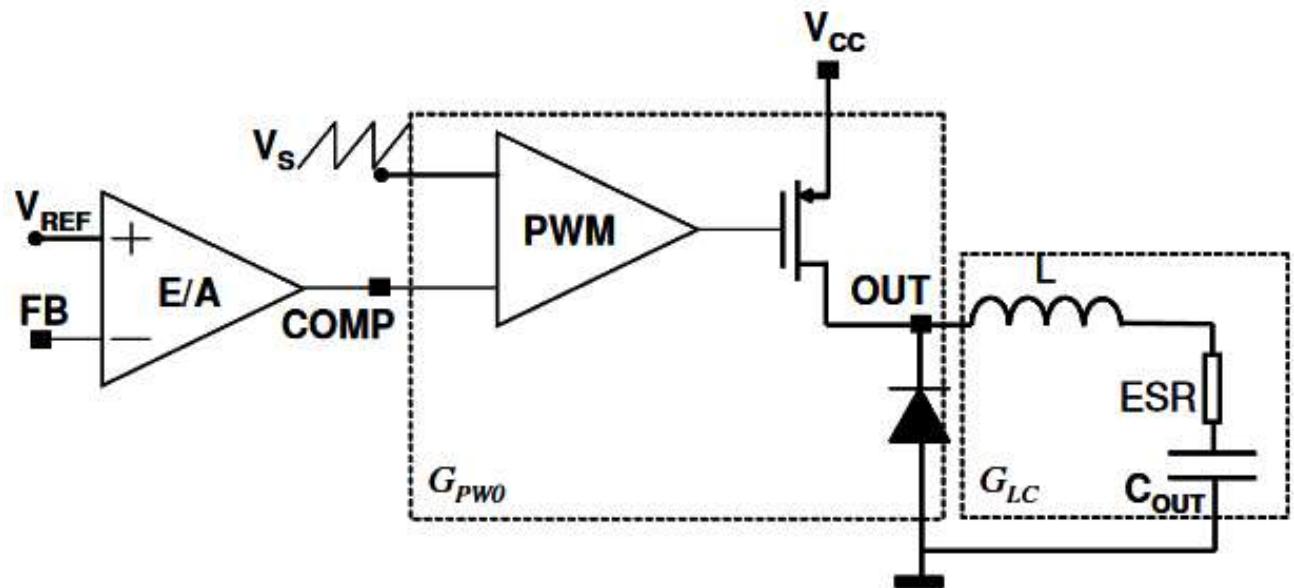

$$G_{LC}(s) = \frac{1 + \frac{s}{2\pi \cdot f_z ESR}}{1 + \frac{s}{2\pi \cdot Q \cdot f_{LC}} + \left(\frac{s}{2\pi \cdot f_{LC}}\right)^2}$$

$$f_{LC} = \frac{1}{2\pi \cdot \sqrt{L \cdot C_{OUT}}} \cdot \sqrt{1 + \frac{ESR}{R_{OUT}}}, \quad f_{zESR} = \frac{1}{2\pi \cdot ESR \cdot C_{OUT}}$$

$$Q = \frac{\sqrt{R_{OUT} \cdot L \cdot C_{OUT} \cdot (R_{OUT} + ESR)}}{L + C_{OUT} \cdot R_{OUT} \cdot ESR}$$

Usually : $f_{LC} < f_{zESR}$

→ Slightly depends on the load

Introduction

Direct conversion

Buck chopper

Boost chopper



Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Example : A7985A

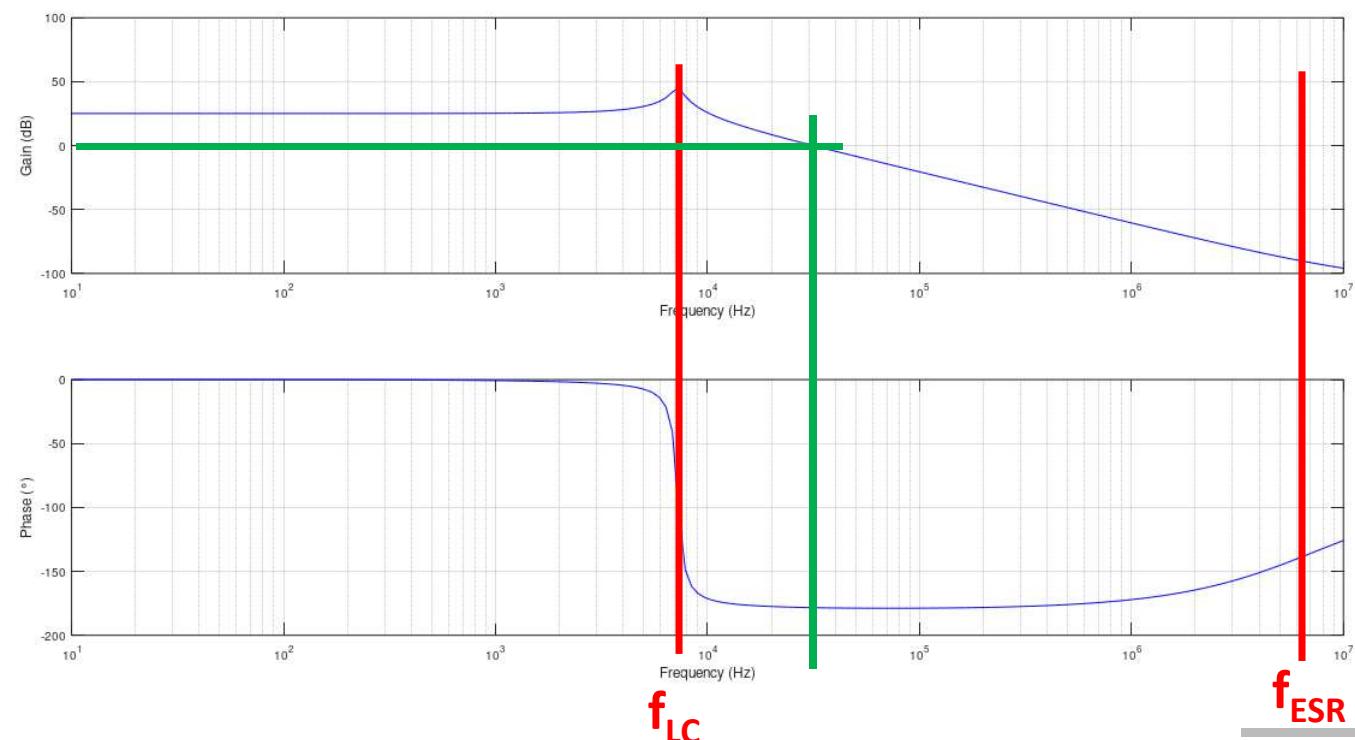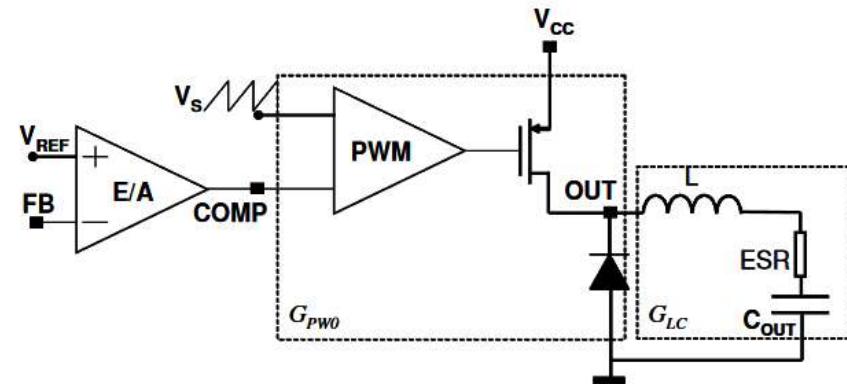

Introduction

Direct conversion

Buck chopper

Boost chopper

Reversible
choppers

Inverters

Closed loop
chopper control




Energy storage
based chopper

Example : A7985A

If $f_{zESR} \gg BW$ (desired)
($ESR < 1m\Omega$)

Zeroes : $f_{Z1} = \frac{1}{2\pi \cdot C_3 \cdot (R_1 + R_3)}, \quad f_{Z2} = \frac{1}{2\pi \cdot R_4 \cdot C_4}$

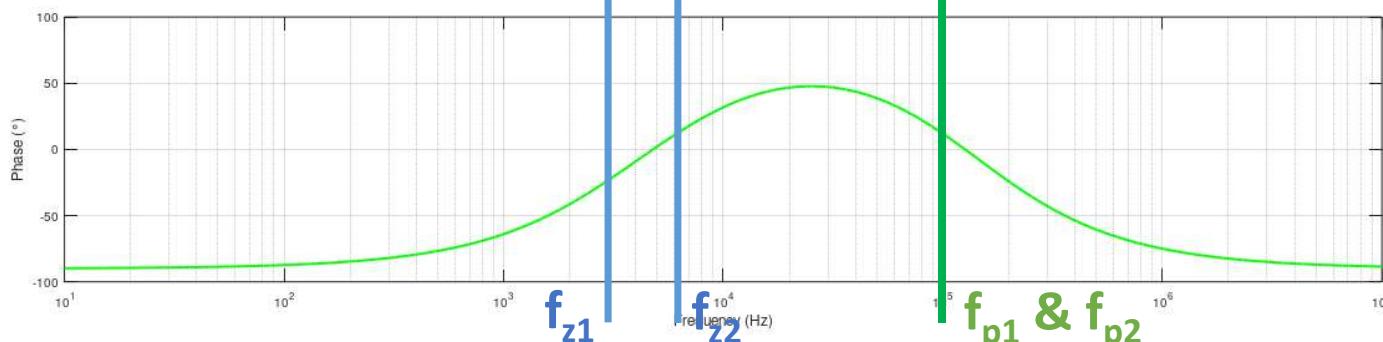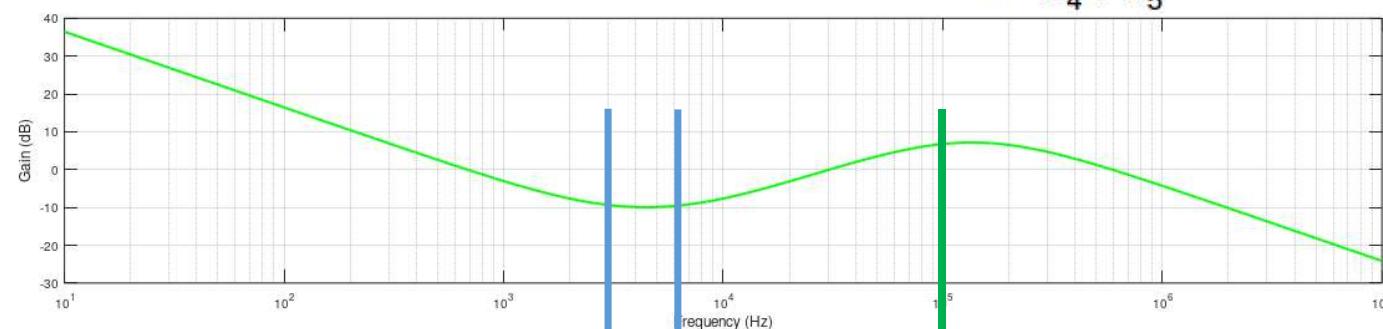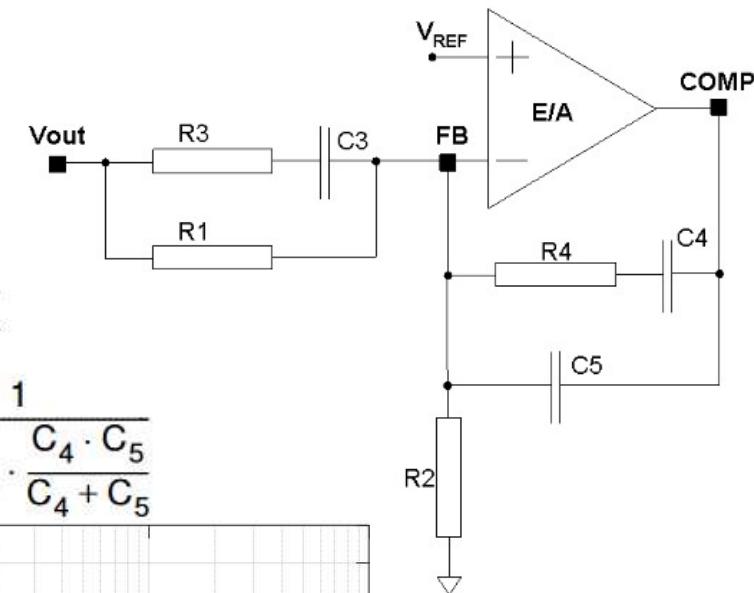Poles : $f_{P0} = 0, \quad f_{P1} = \frac{1}{2\pi \cdot R_3 \cdot C_3}, \quad f_{P2} = \frac{1}{2\pi \cdot R_4 \cdot \frac{C_4 \cdot C_5}{C_4 + C_5}}$



Introduction

Direct conversion

Buck chopper

Boost chopper


Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Example : A7985A

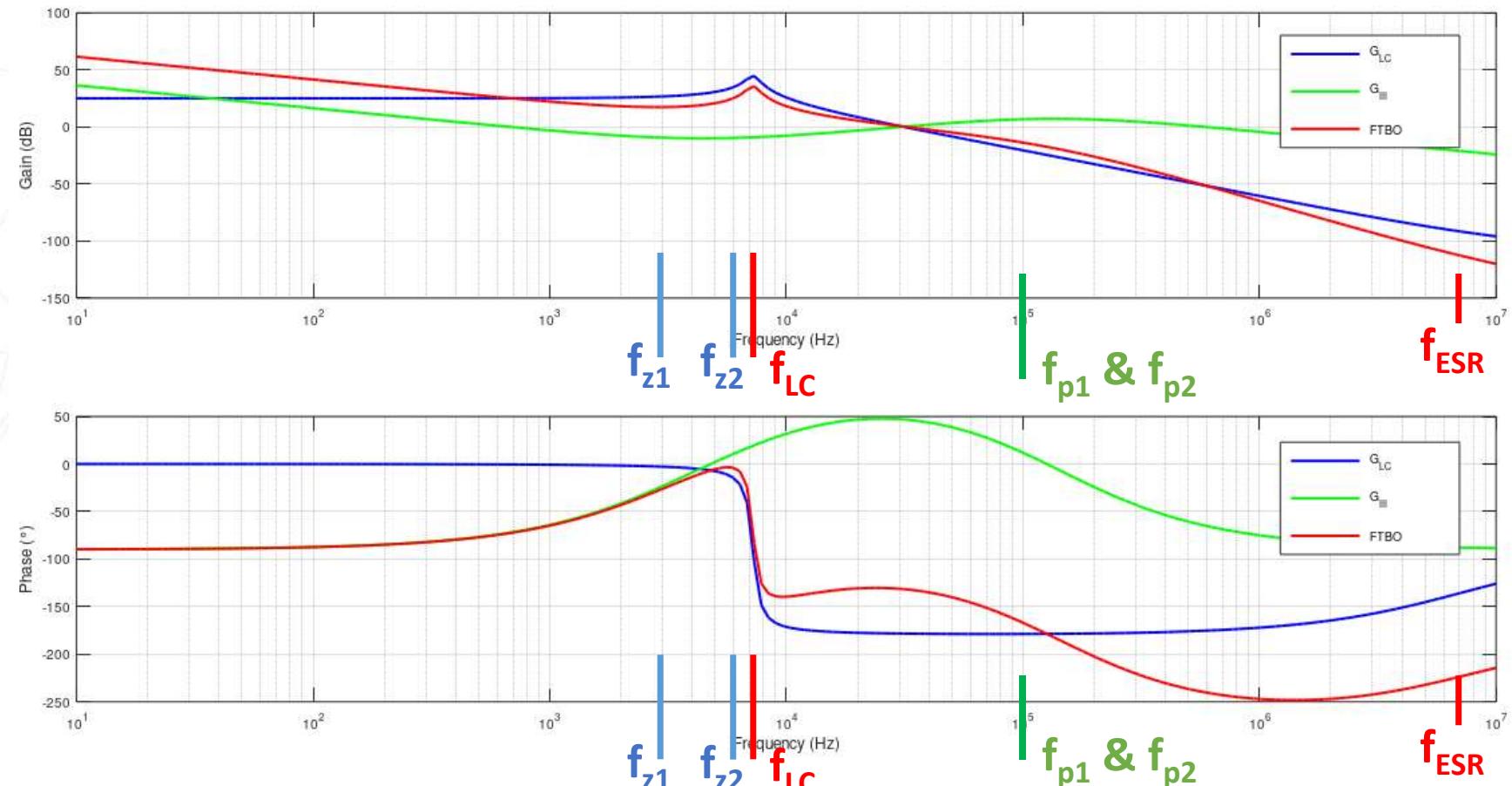

Introduction

Direct conversion

Buck chopper

Boost chopper

Reversible
choppers

Inverters


Closed loop
chopper control

Energy storage
based chopper

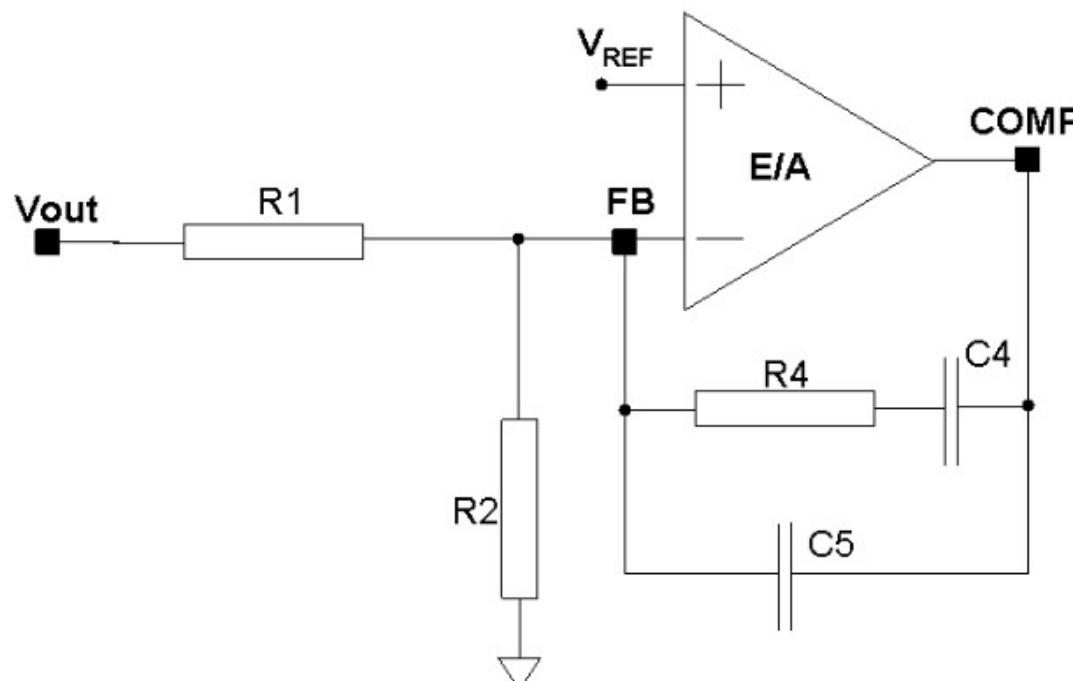Example : A7985A

If $f_{zESR} \approx BW$ (desired)
 $ESR > 30 \text{ m}\Omega$

→ Use of the zero of ESR to stabilize the loop



Zero : $f_{Z1} = \frac{1}{2\pi \cdot R_4 \cdot C_4},$

Poles : $f_{P0} = 0,$

$$f_{P1} = \frac{1}{2\pi \cdot R_4 \cdot \frac{C_4 \cdot C_5}{C_4 + C_5}}$$

Introduction

Direct conversion

Buck chopper

Boost chopper

Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Boost Chopper

Introduction

Direct conversion

Buck chopper

Boost chopper

Reversible
choppers

Inverters

Closed loop
chopper control


Energy storage
based chopper

Boost chopper

Buck chopper : Voltage source  **Current receiver**

Boost chopper : Current source  **Voltage receiver**

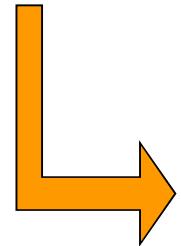Current source \Leftrightarrow **Voltage source + inductor**



Voltage receiver \Leftrightarrow **Battery or capacitive receiver**

Introduction

Direct conversion

Buck chopper

Boost chopper


Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Boost chopper: principle

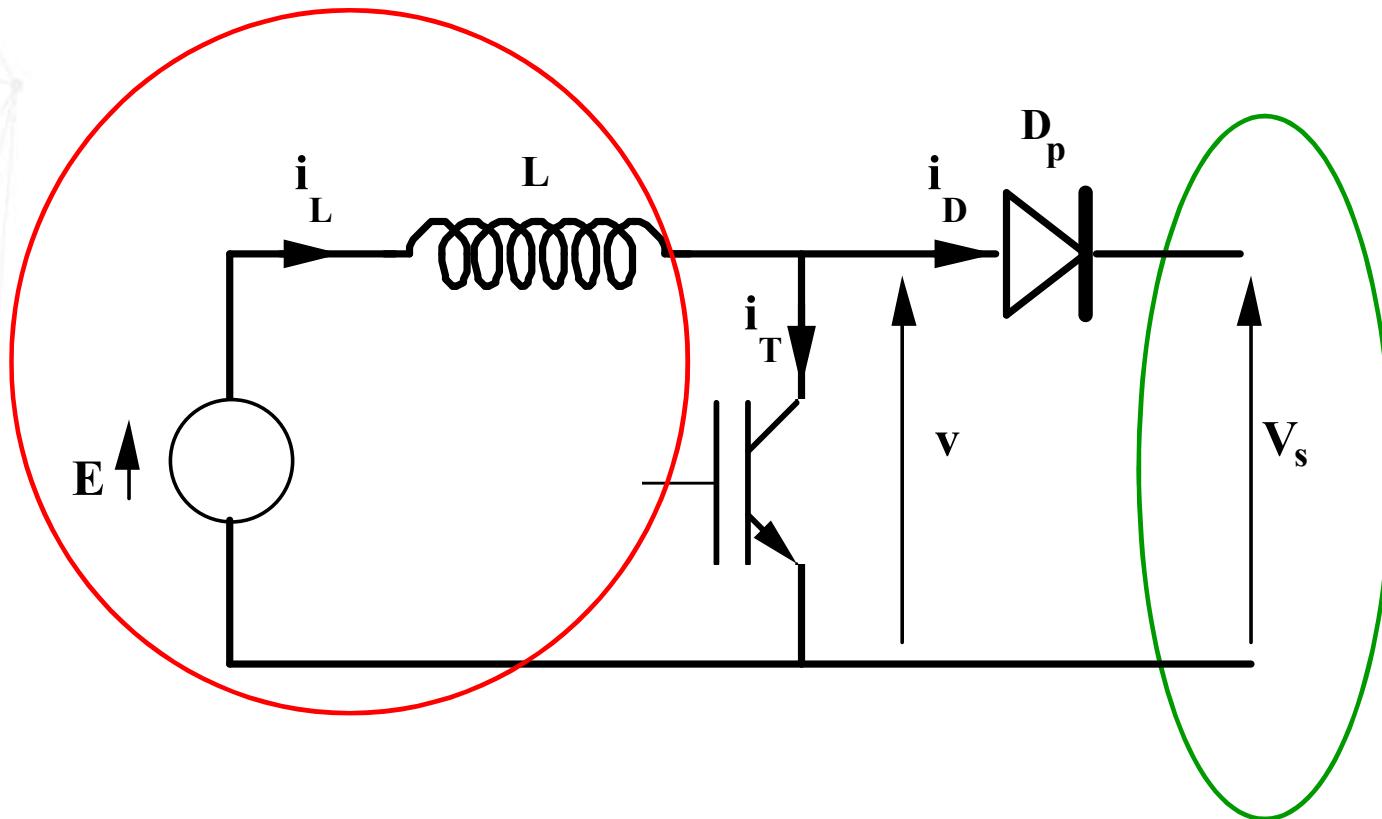

Introduction

Direct conversion

Buck chopper

Boost chopper



Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Control

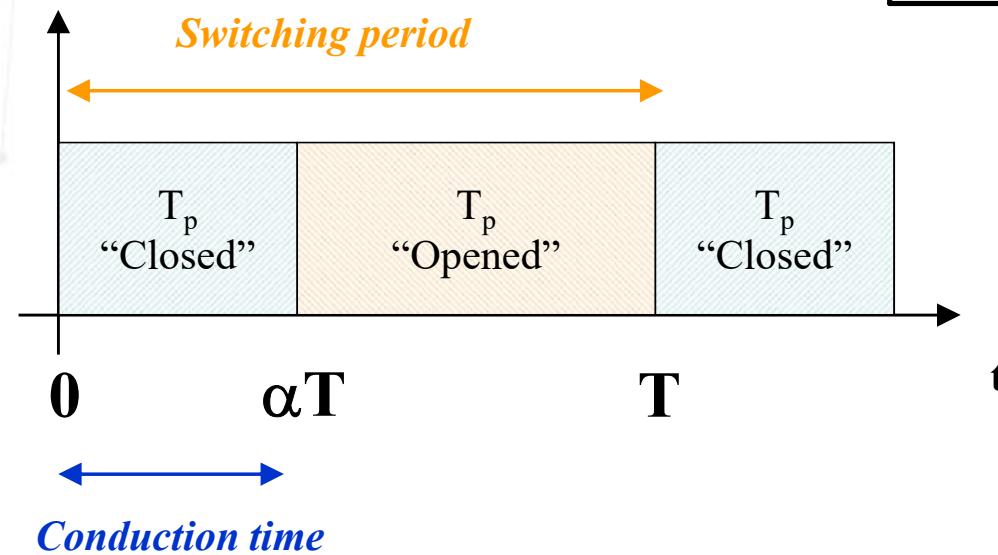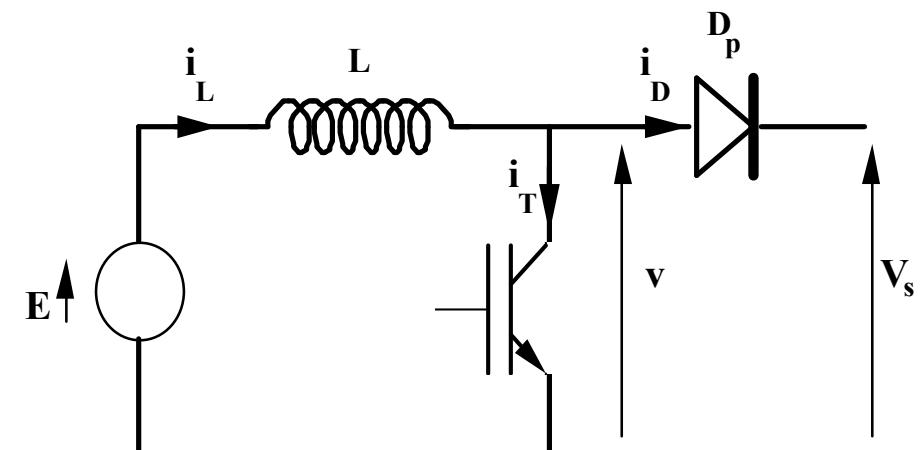

Introduction

Direct conversion

Buck chopper

Boost chopper


Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Principle

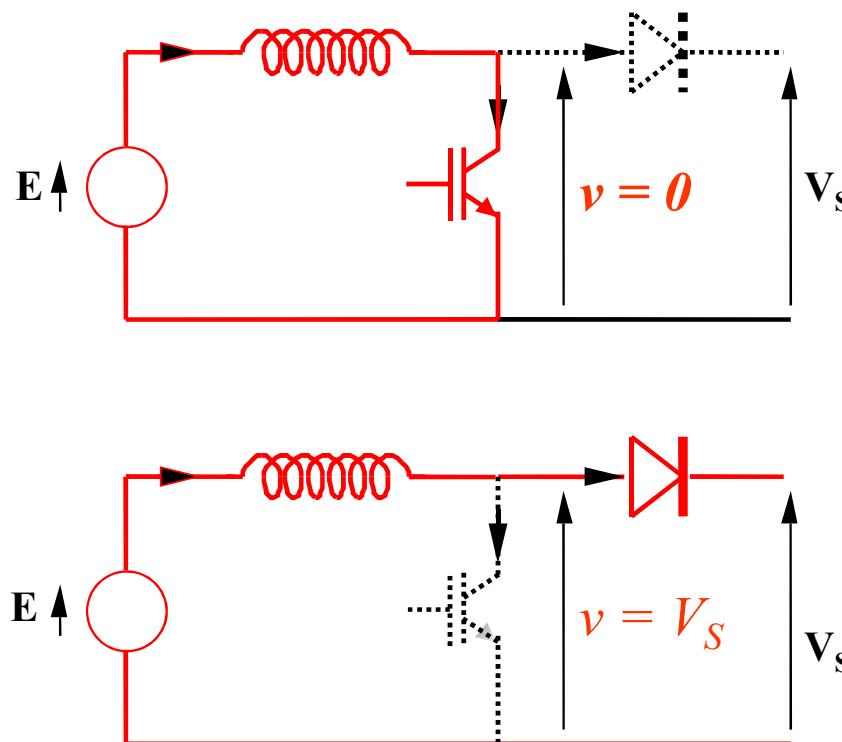

$0 < t < \alpha T$

$\alpha T < t < T$

Introduction

Direct conversion

Buck chopper

Boost chopper

Reversible
choppers


Inverters

Closed loop
chopper control

Energy storage
based chopper

Modes

- *Continuous conduction: $i_L > 0$*

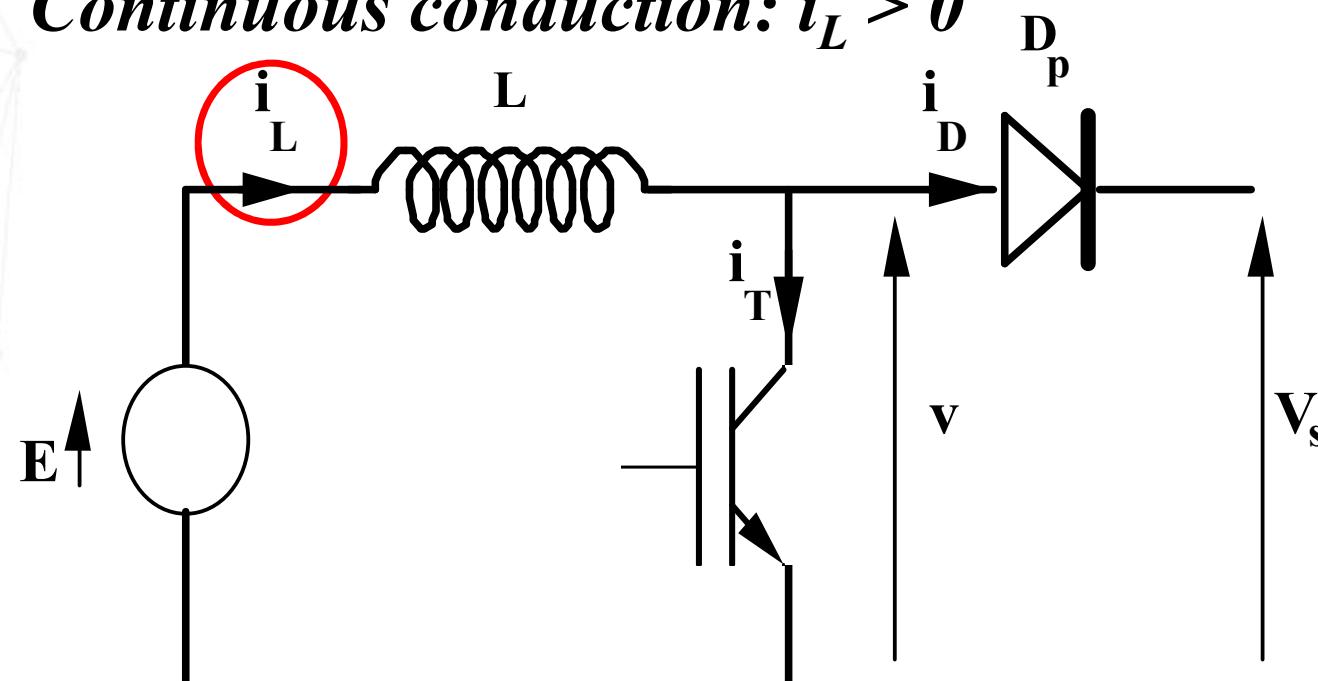

- *Discontinuous conduction: $i_L(t_0) = 0 ; t_0 < T$*

Introduction

Direct conversion

Buck chopper

Boost chopper



Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Continuous mode

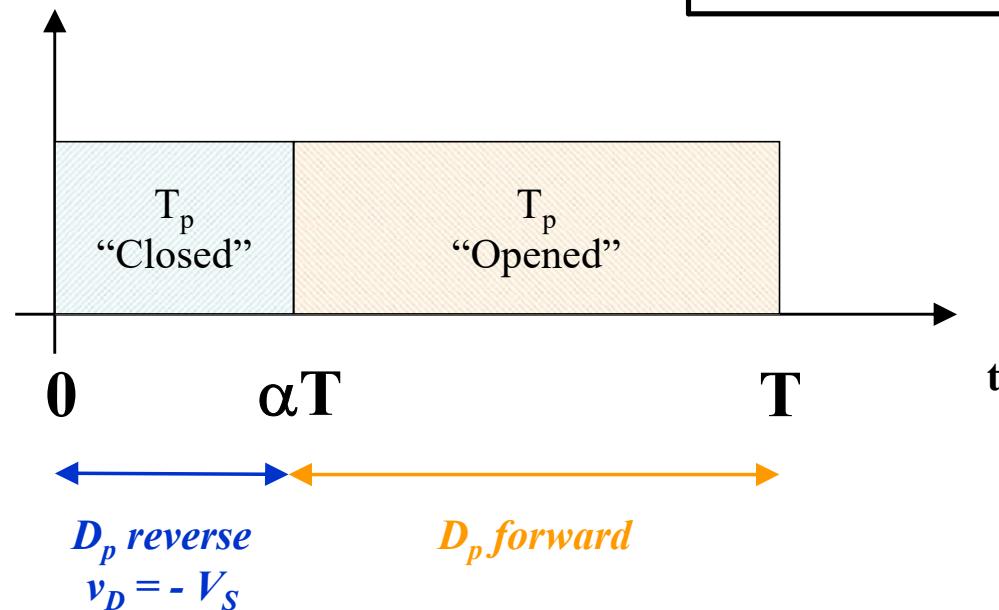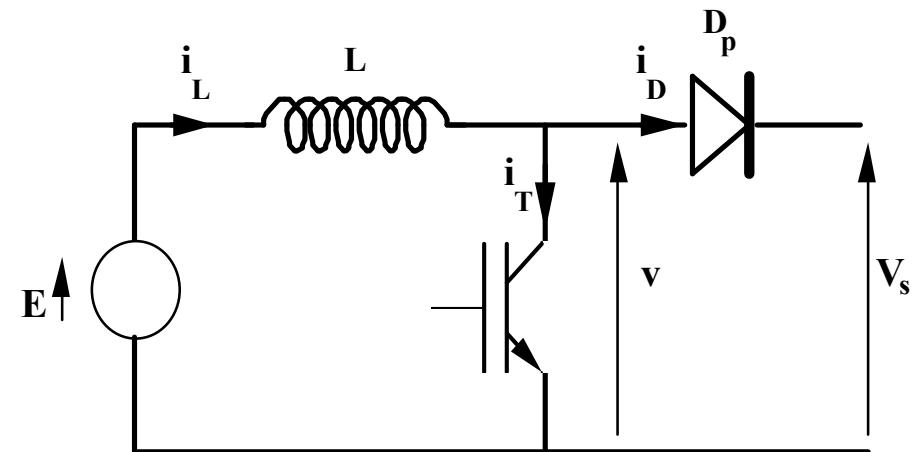

Introduction

Direct conversion

Buck chopper

Boost chopper


Reversible
choppers

Inverters


Closed loop
chopper control

Energy storage
based chopper

Continuous mode: Chronograms

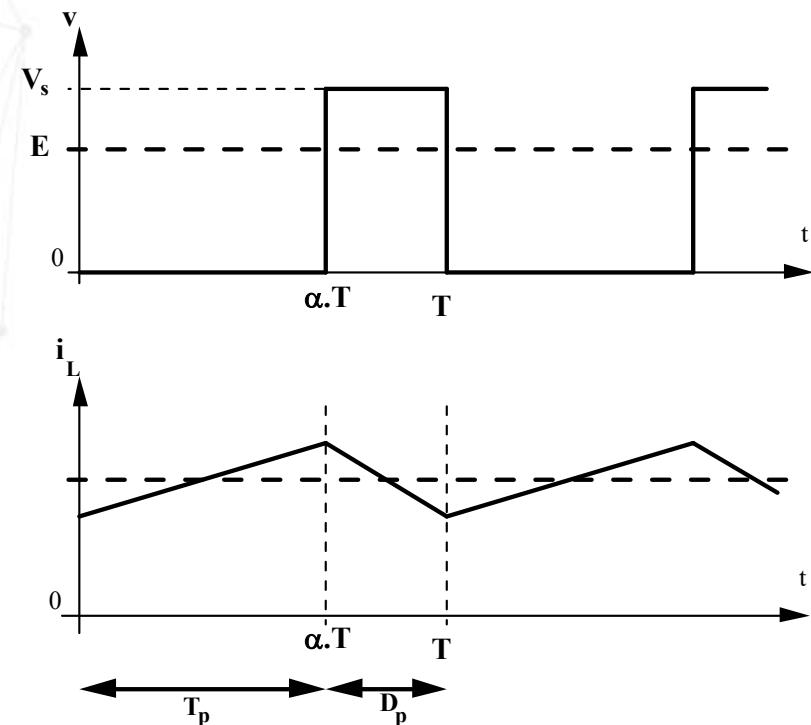

$$E < V_s$$

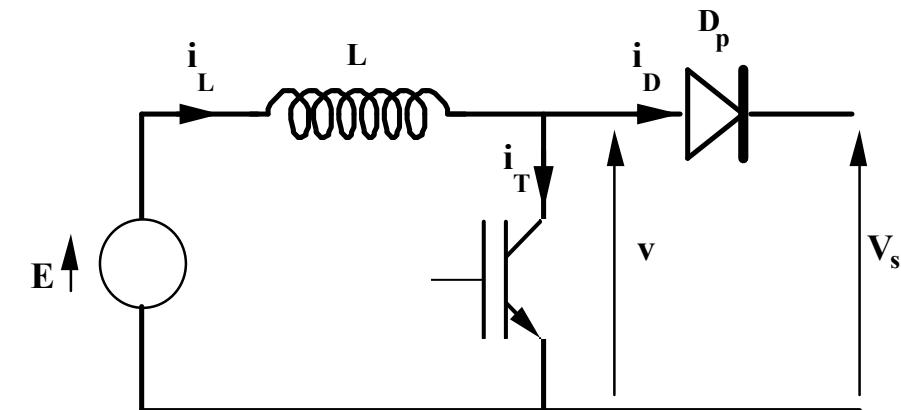

- $0 < t < \alpha T$

$$\frac{di}{dt} = \frac{E}{L}$$

- $\alpha T < t < T$

$$\frac{di}{dt} = \frac{E - V_s}{L}$$

BOOST

Introduction

Direct conversion

Buck chopper

Boost chopper

Reversible
choppers



Inverters

Closed loop
chopper control

Energy storage
based chopper

Continuous mode:
Output voltage calculation

$$V_s = \frac{E}{1 - \alpha}$$

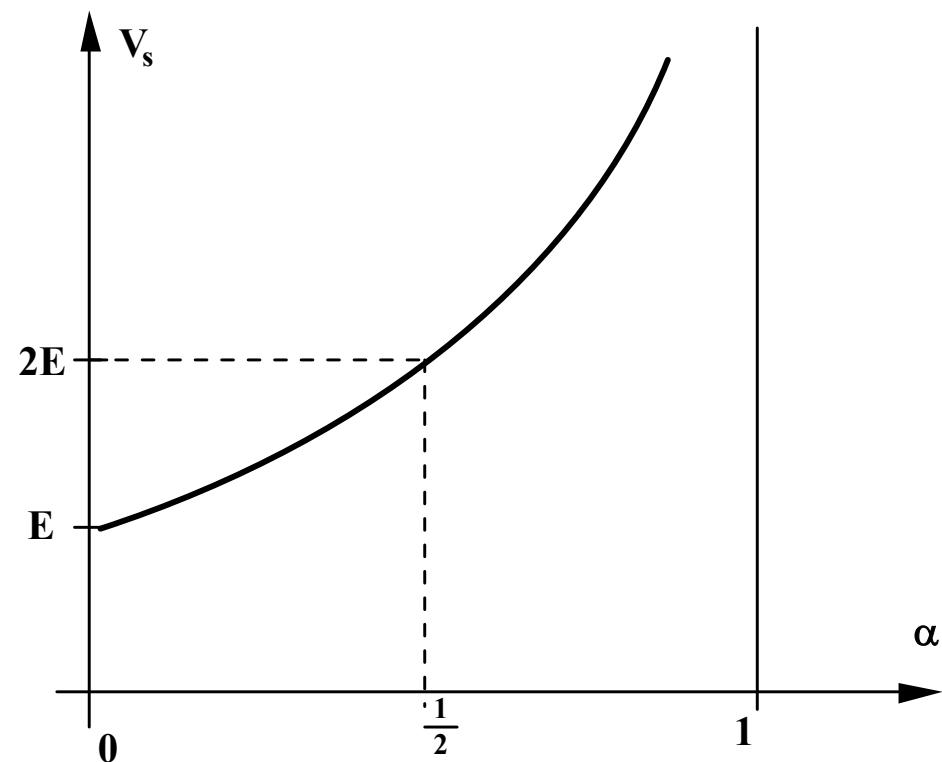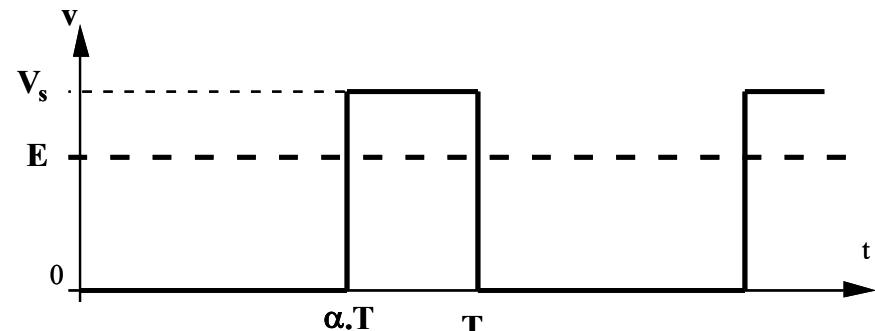

Introduction

Direct conversion

Buck chopper

Boost chopper


Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

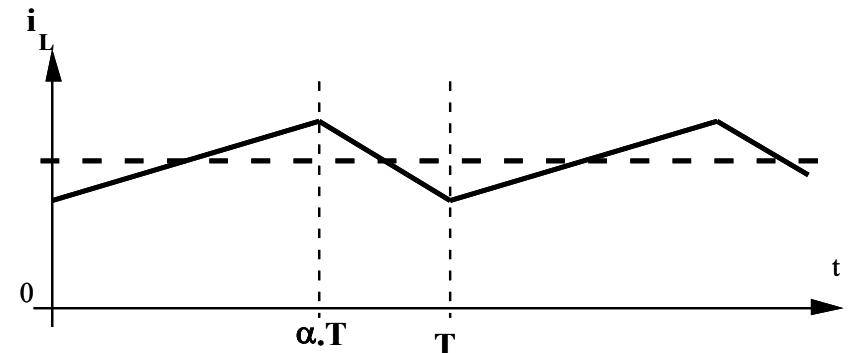Continuous mode:
Current ripple calculation



Current ripple i_L

$$\Delta I_L = \alpha \cdot \frac{E \cdot T}{L}$$

Maximum ripple ($\alpha = 1$)

$$\Delta I_{L max} = \frac{E \cdot T}{L}$$

Introduction

Direct conversion

Buck chopper

Boost chopper



Reversible
choppers

Inverters


Closed loop
chopper control

Energy storage
based chopper

Continuous mode: Output filtering

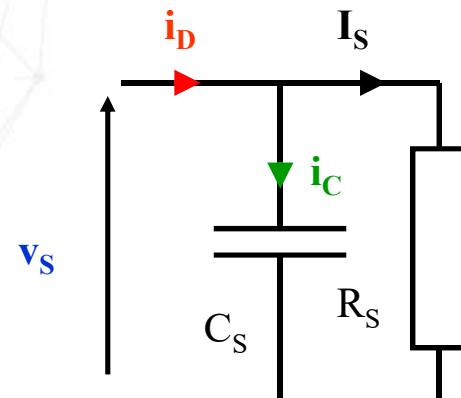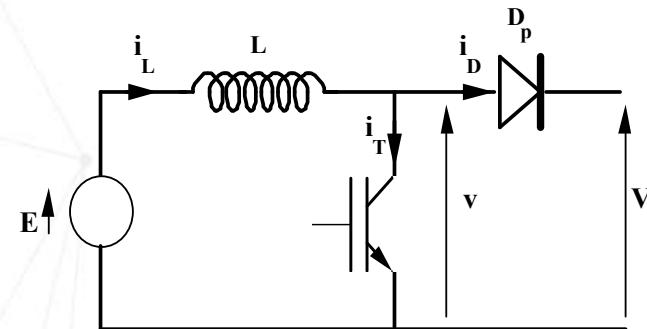

$$i_C = C_s \cdot \frac{dv_s}{dt}$$

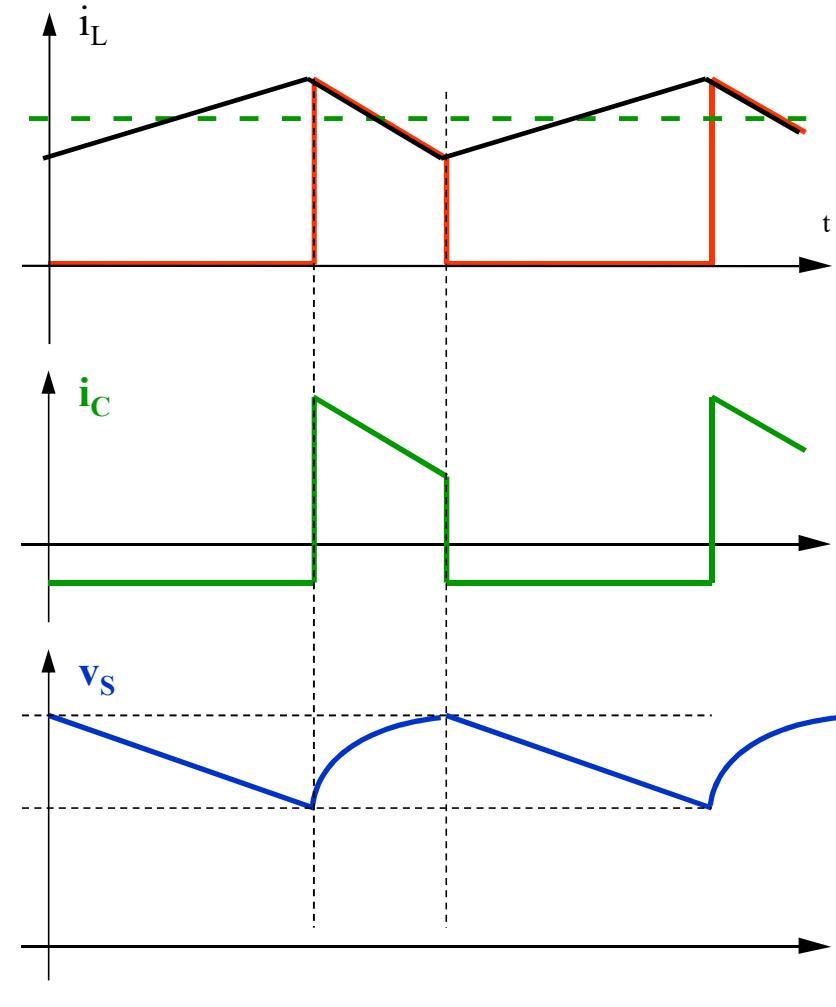

Introduction

Direct conversion

Buck chopper

Boost chopper

Reversible
choppers

Inverters

Closed loop
chopper control


Energy storage
based chopper

Continuous mode: Output filtering

$$\Delta V_S = \frac{1}{C_S} \cdot \int_{t_1}^{t_2} i_C(t) \cdot dt = \frac{I_S \cdot \alpha T}{C_S}$$

$$\text{or } I_S = \frac{V_S}{R_S} = \frac{E}{(1-\alpha)R_S}$$
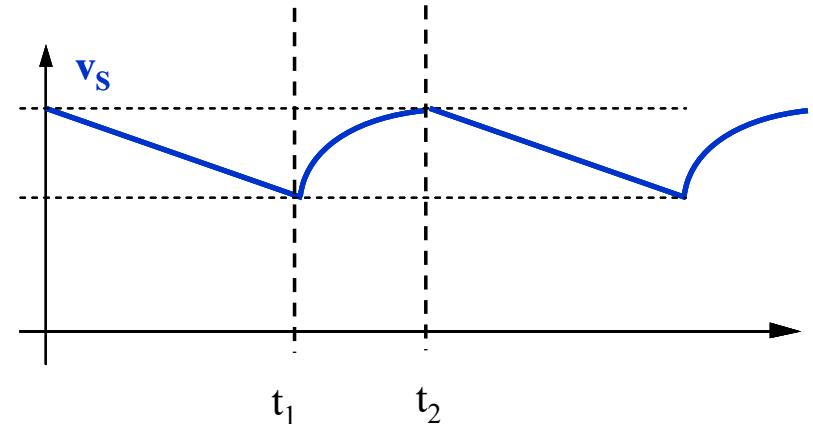
$$\Delta V_S = \frac{ET}{R_S C_S} \cdot \frac{\alpha}{1-\alpha}$$



→ **C_S**

Introduction

Direct conversion

Buck chopper

Boost chopper



Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Boundary mode: $i_L(T)=0$

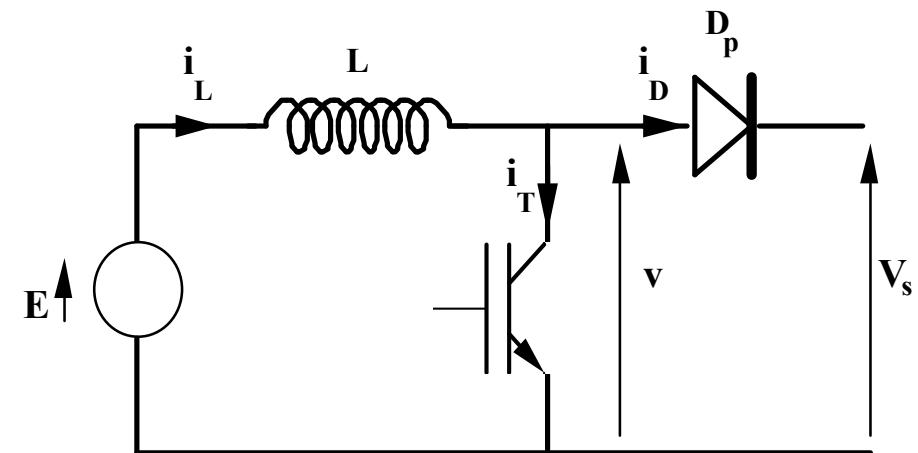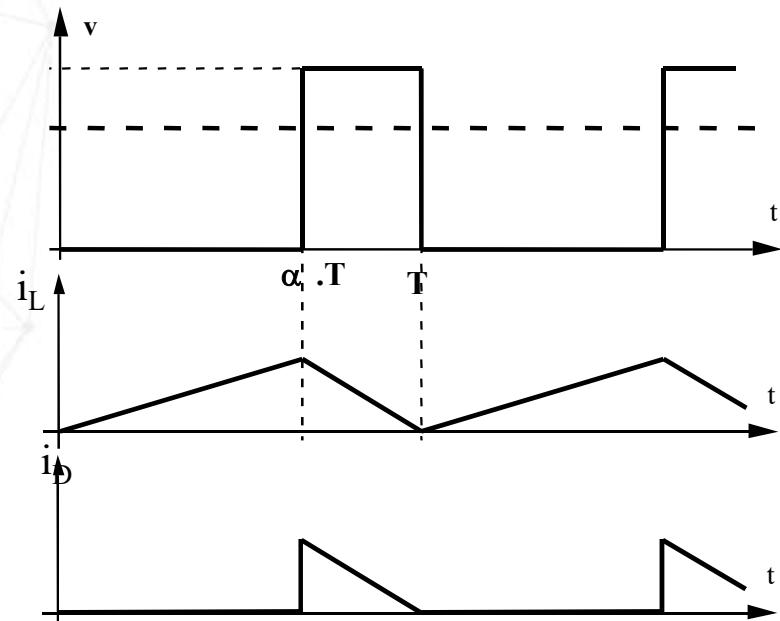

$$I_S = \langle i_D \rangle = \frac{1}{2} \cdot I_{L\max} \cdot (1 - \alpha) = \frac{ET}{2L} \cdot \alpha(1 - \alpha)$$

$$V_S = \frac{E}{1 - \alpha}$$

$$I_S = \frac{ET}{2L} \cdot \frac{E}{V_S} \cdot \left(1 - \frac{E}{V_S} \right)$$

Introduction

Direct conversion

Buck chopper

Boost chopper


Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Discontinuous mode

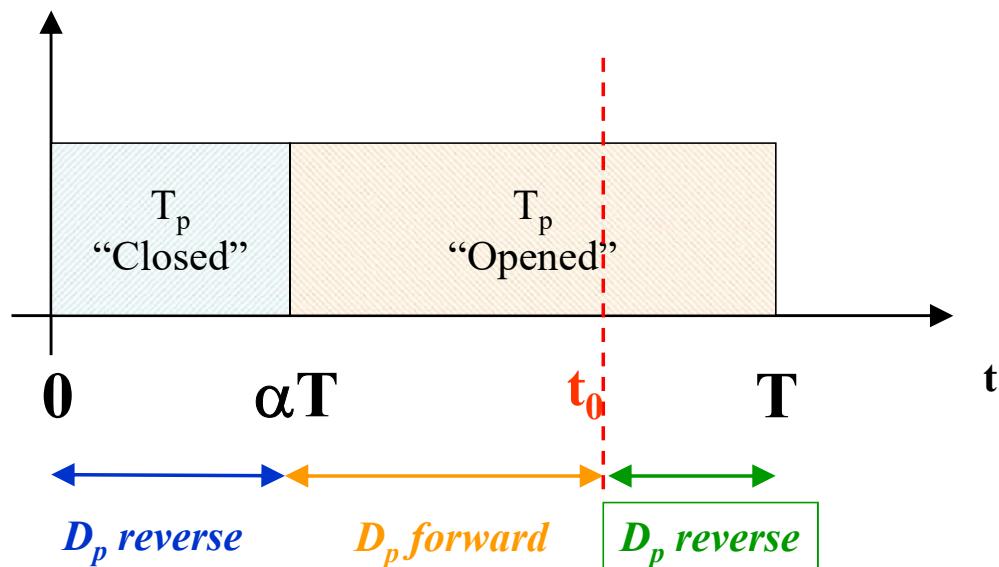

At $t_0 = \alpha' \cdot T$: diode switches to reverse mode

Introduction

Direct conversion

Buck chopper

Boost chopper


Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Discontinuous mode: Chronograms

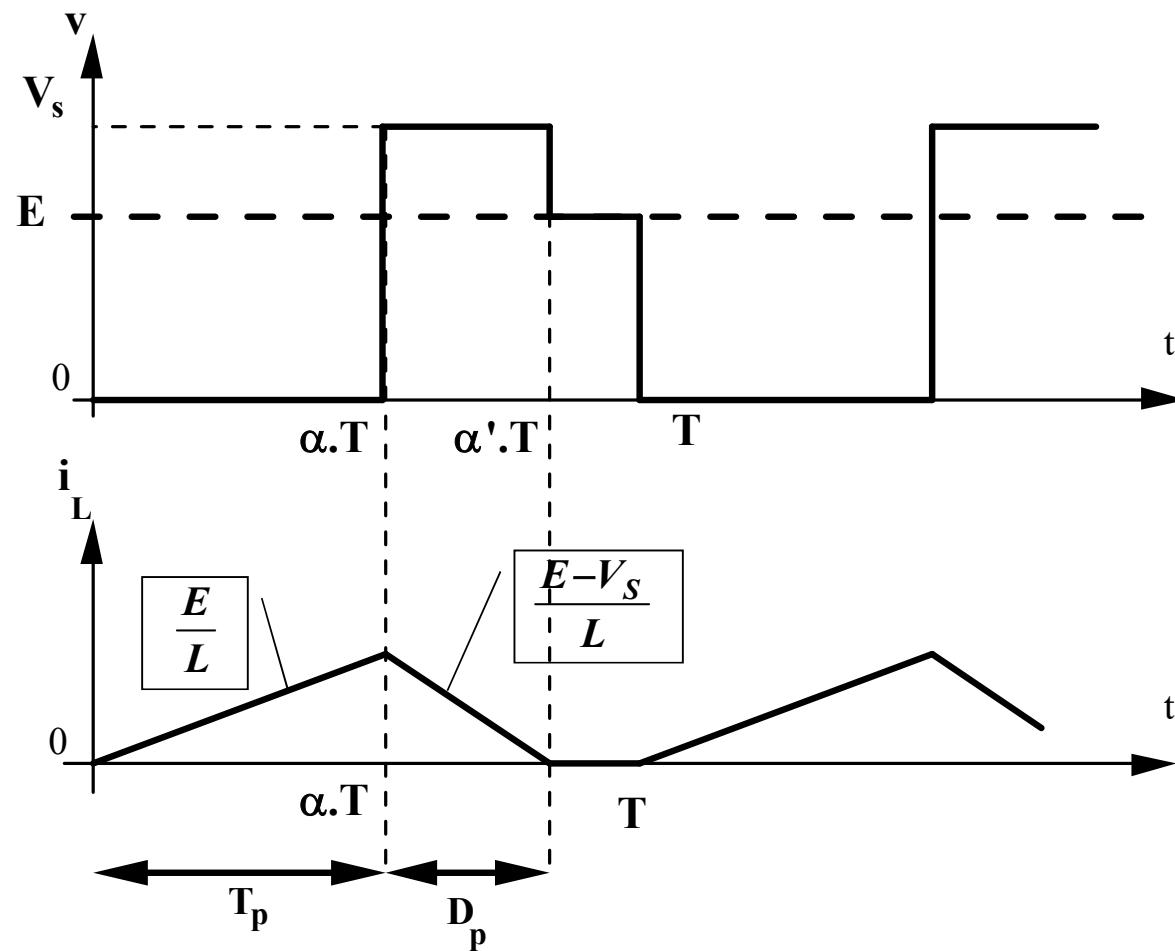

Introduction

Direct conversion

Buck chopper

Boost chopper

Reversible
choppers

Inverters


Closed loop
chopper control

Energy storage
based chopper

Discontinuous mode: calculation

$$\frac{E}{L}\alpha T = \frac{V_S - E}{L}(\alpha' - \alpha)T \quad \Rightarrow \quad V_S = \frac{\alpha'}{\alpha' - \alpha} E$$
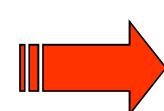
$$I_S = \langle i_D \rangle = \frac{1}{2} \cdot I_{L\max} \cdot (\alpha' - \alpha) = \frac{ET}{2L} \cdot \alpha(\alpha' - \alpha)$$



$$V_S = E + \frac{\alpha^2 E^2 T}{2 L I_S}$$

Introduction

Direct conversion

Buck chopper

Boost chopper


Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

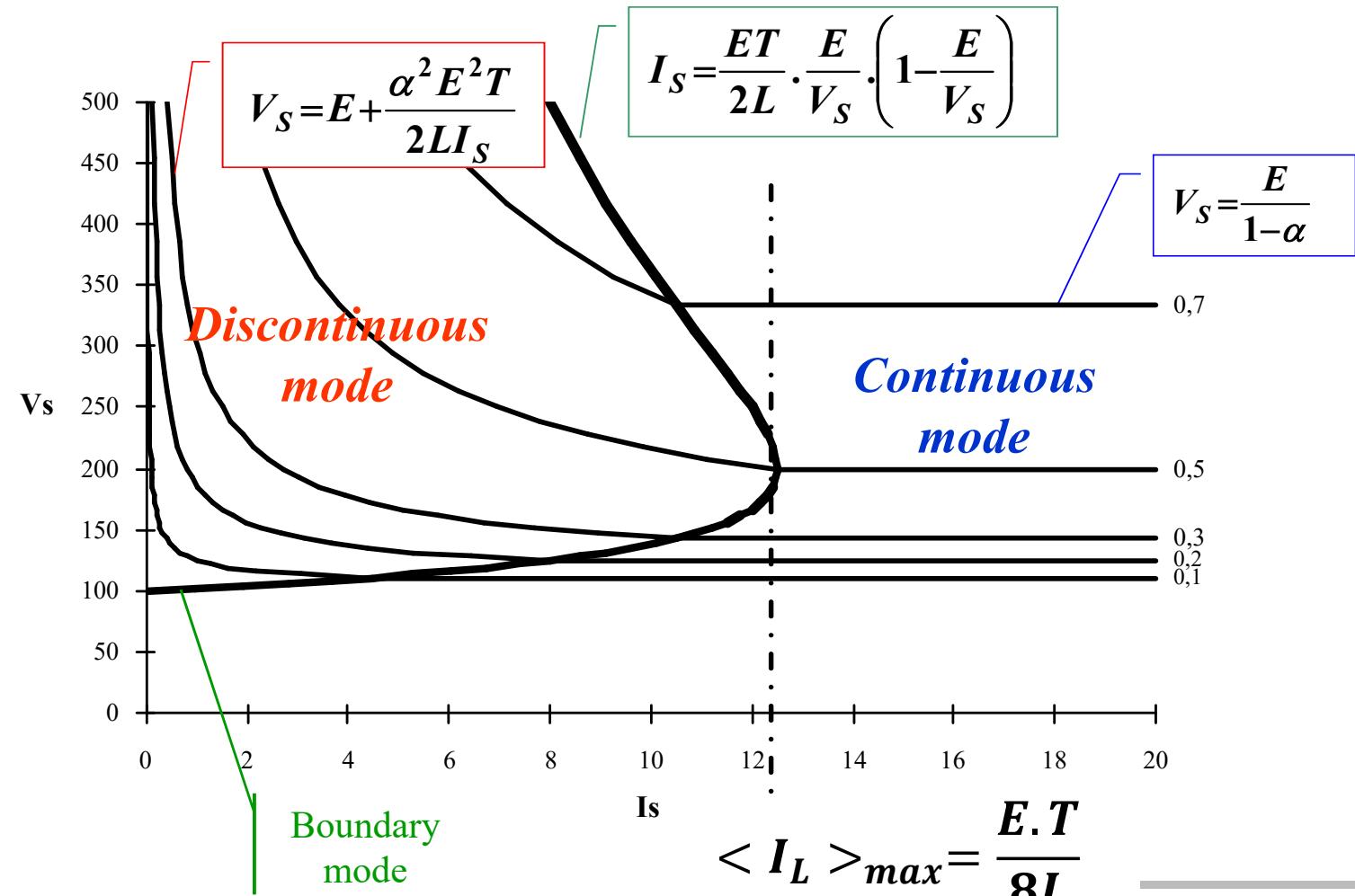Discontinuous mode: output characteristics



Introduction

Direct conversion

Buck chopper

Boost chopper


Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Example : TPS61170

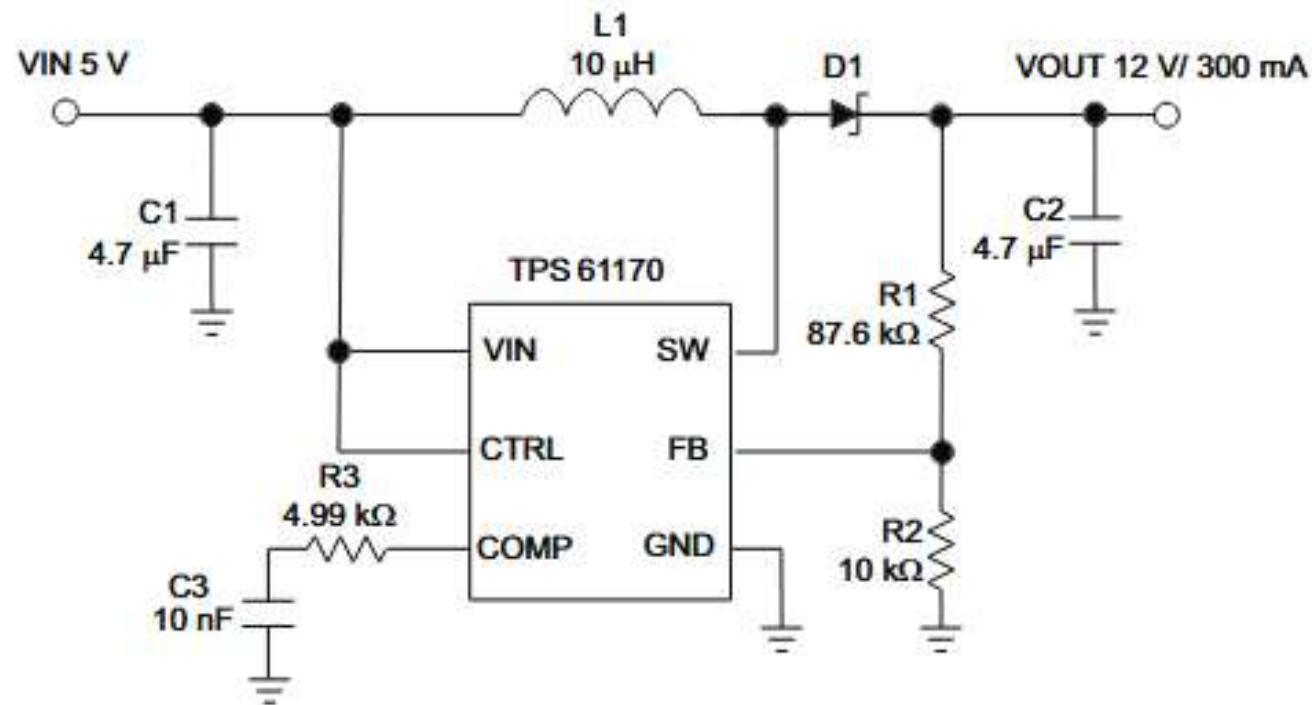

Introduction

Direct conversion

Buck chopper

Boost chopper


Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Example : TPS61170

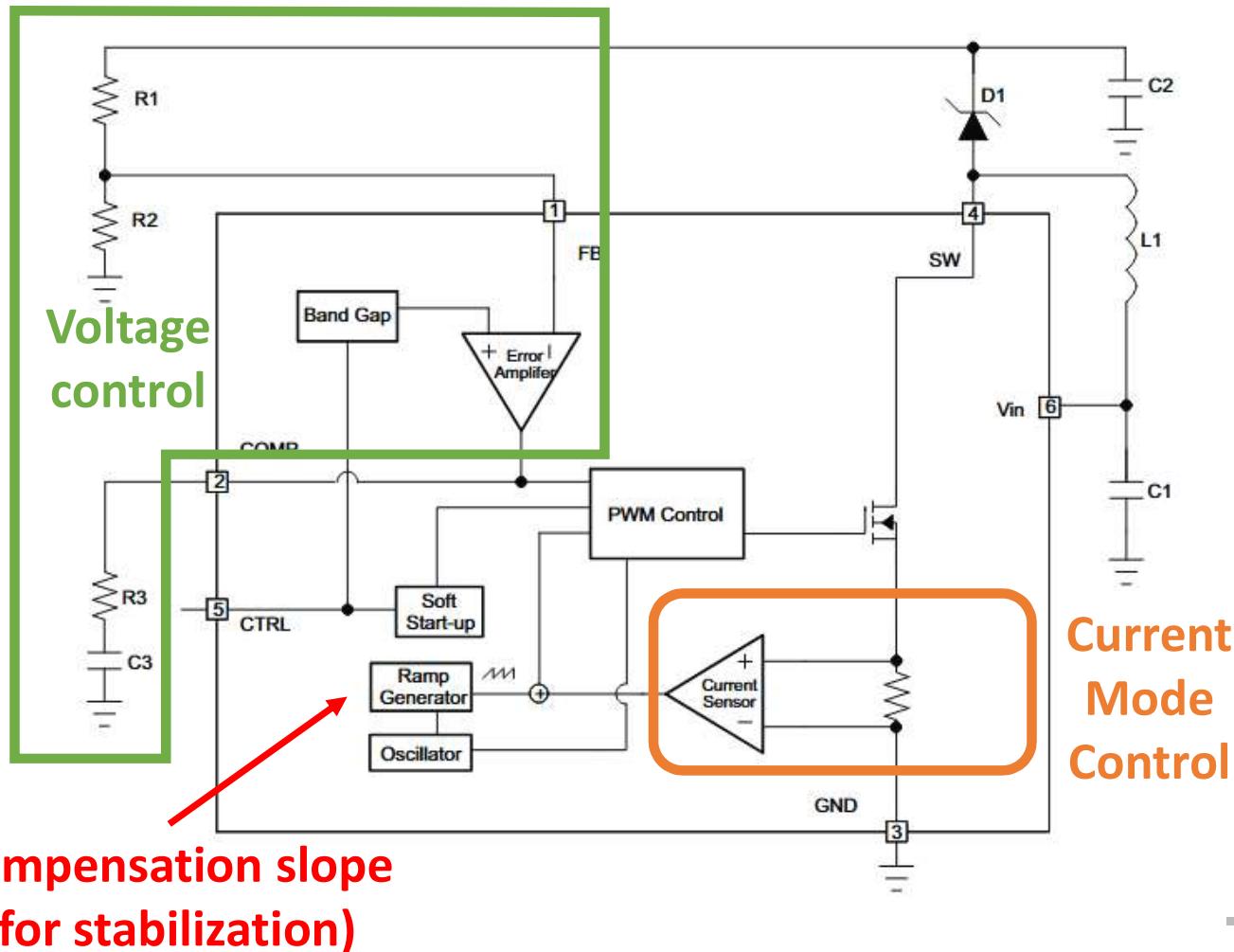

Introduction

Direct conversion

Buck chopper

Boost chopper


Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Reminder : buck chopper

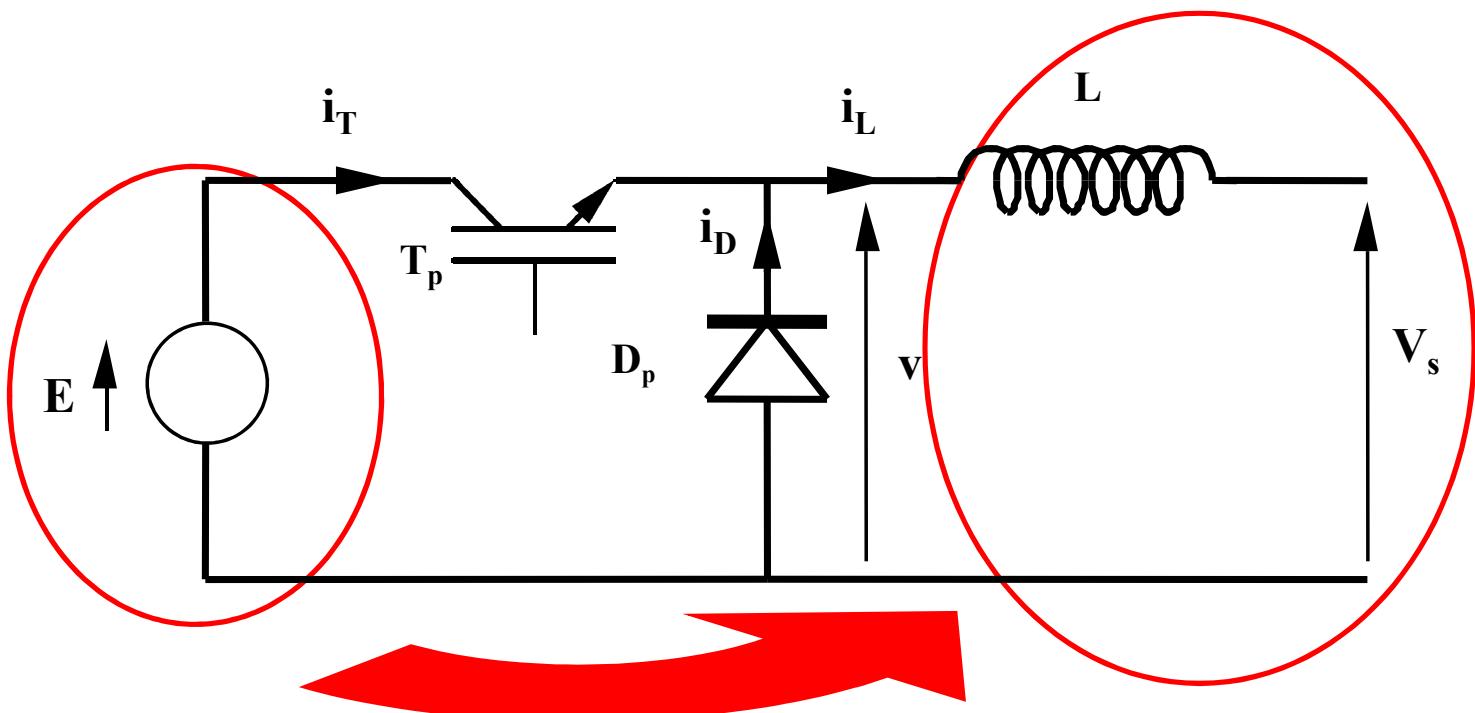

Introduction

Direct conversion

Buck chopper

Boost chopper


Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Reminder : boost chopper

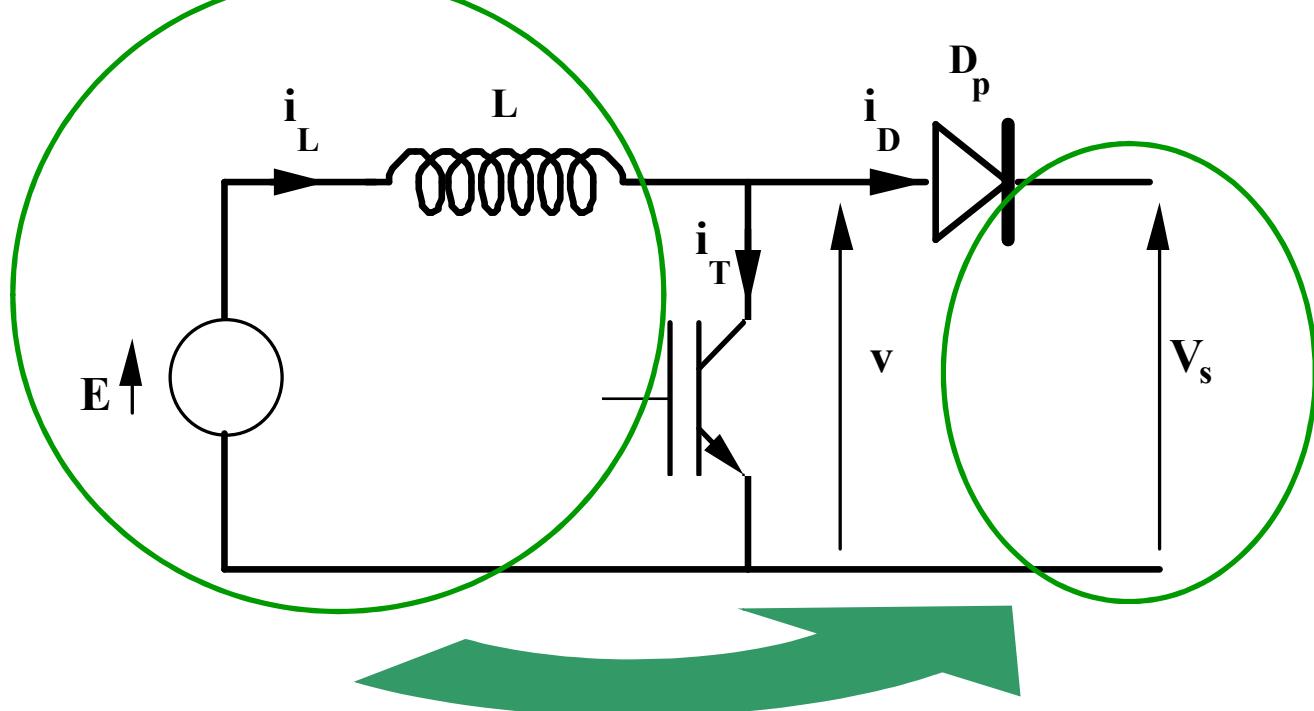

Introduction

Direct conversion

Buck chopper

Boost chopper


Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Linked sources

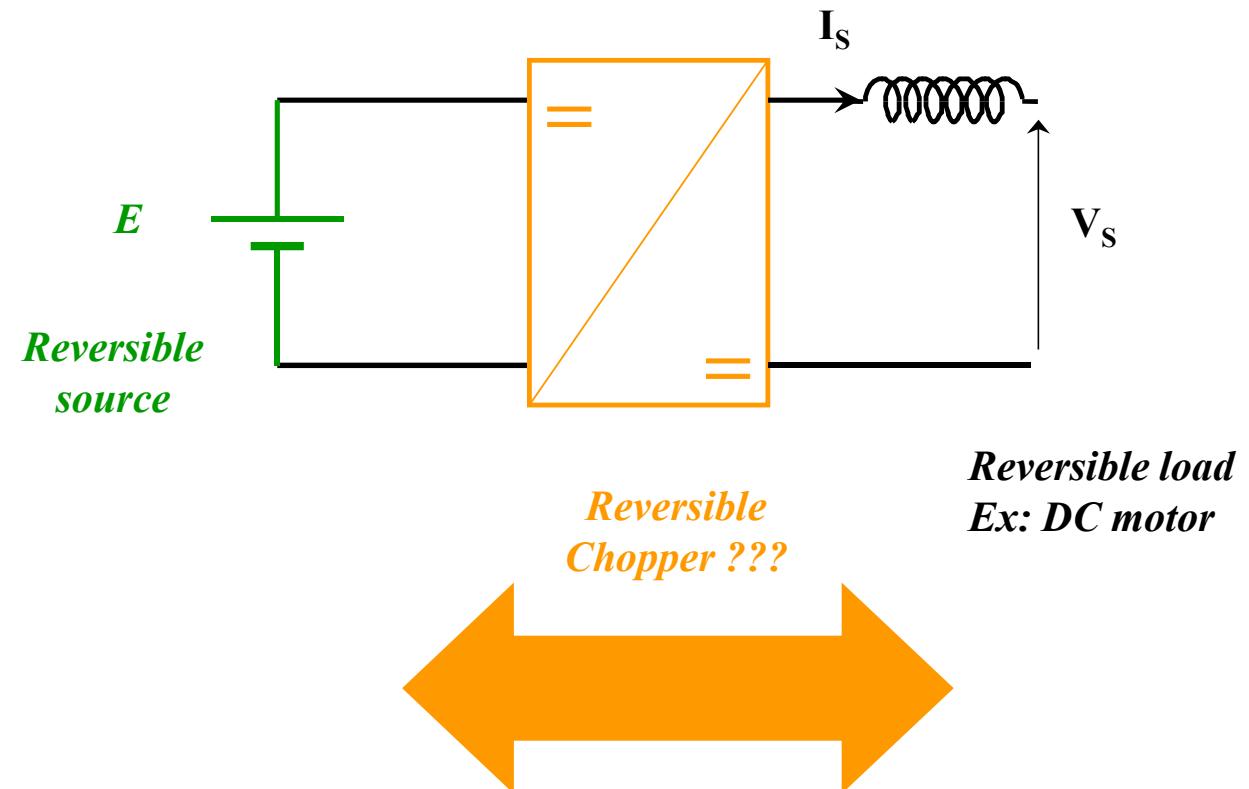

Introduction

Direct conversion

**Reversible
choppers**

Inverters

Closed loop
chopper control

Energy storage
based chopper



Reversible Chopper

Introduction

Direct conversion

Reversible choppers


2 quadrants chopper
4 quadrants chopper

Inverters

Closed loop
chopper control

Energy storage
based chopper

Reversible choppers: quadrants

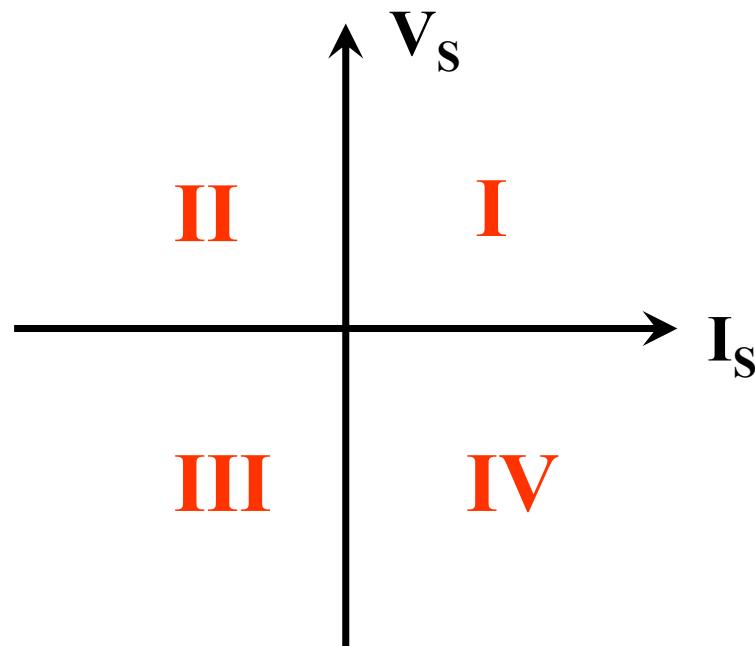

Introduction

Direct conversion

Reversible
choppers

2 quadrants chopper


4 quadrants chopper

Inverters

Closed loop
chopper control

Energy storage
based chopper

Two quadrants reversible chopper

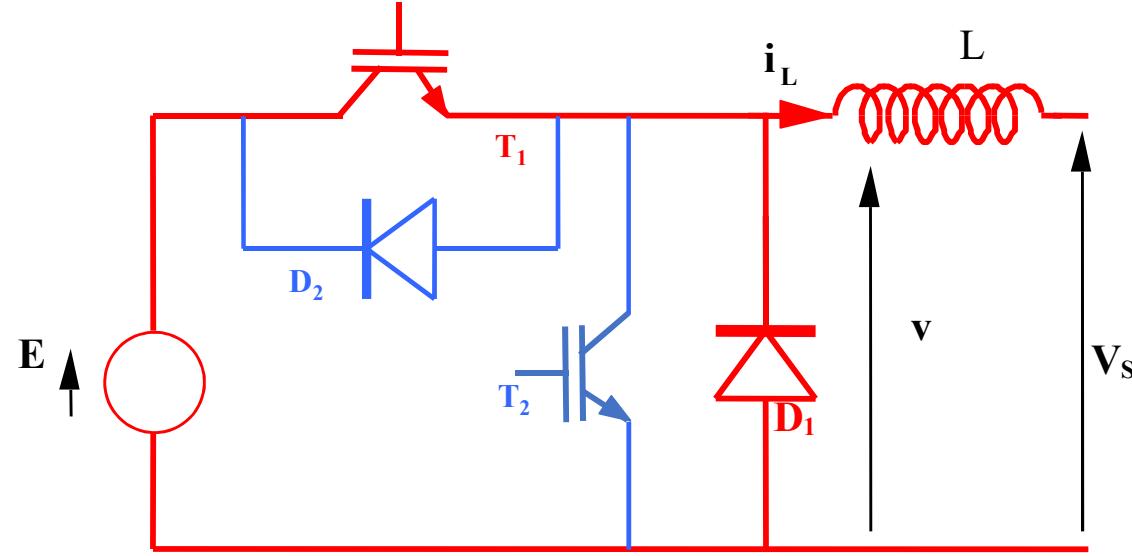

Buck chopper

Boost chopper

Introduction

Direct conversion

Reversible
choppers

2 quadrants chopper


4 quadrants chopper

Inverters

Closed loop
chopper control


Energy storage
based chopper

Two quadrants chopper: control

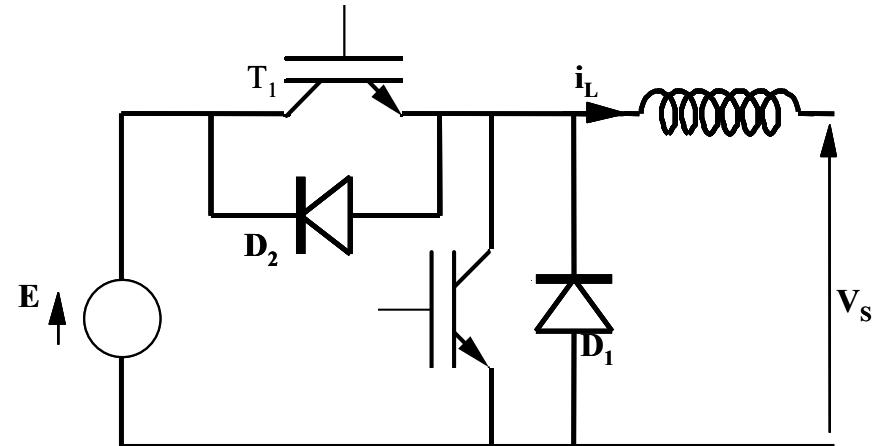

*2 switches => 2 duty cycles
Complementary control*

$$\alpha_1 + \alpha_2 = 1$$

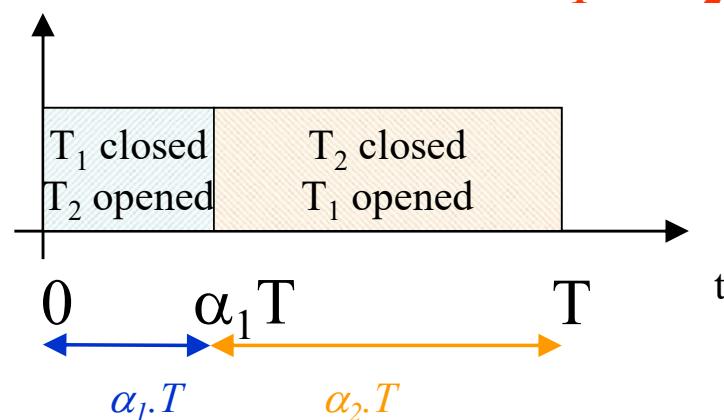

Introduction

Direct conversion

Reversible
choppers

2 quadrants chopper



4 quadrants chopper

Inverters

Closed loop
chopper control

Energy storage
based chopper

Two quadrants chopper: output voltage

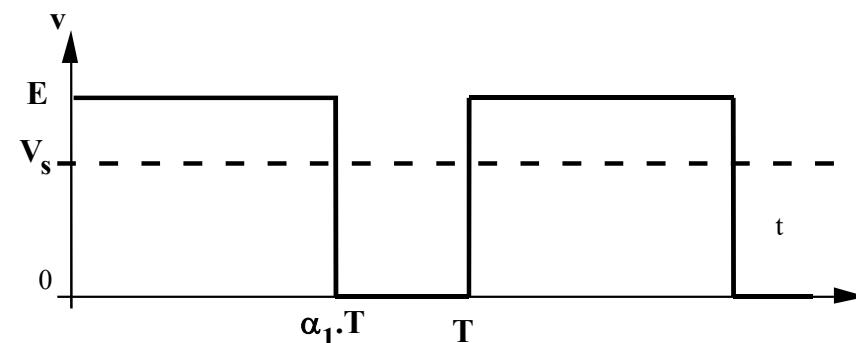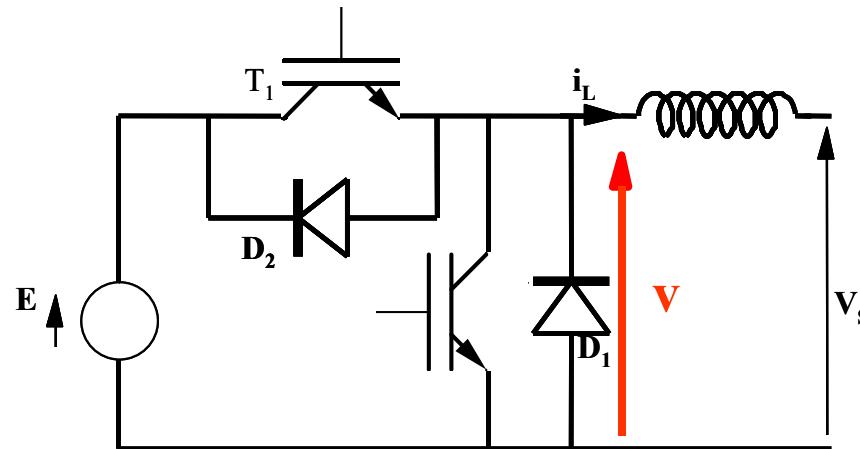

$$V_s = \alpha_1 \cdot E$$

Introduction

Direct conversion

Reversible
choppers





2 quadrants chopper
4 quadrants chopper

Inverters

Closed loop
chopper control

Energy storage
based chopper

Two quadrants chopper: output current

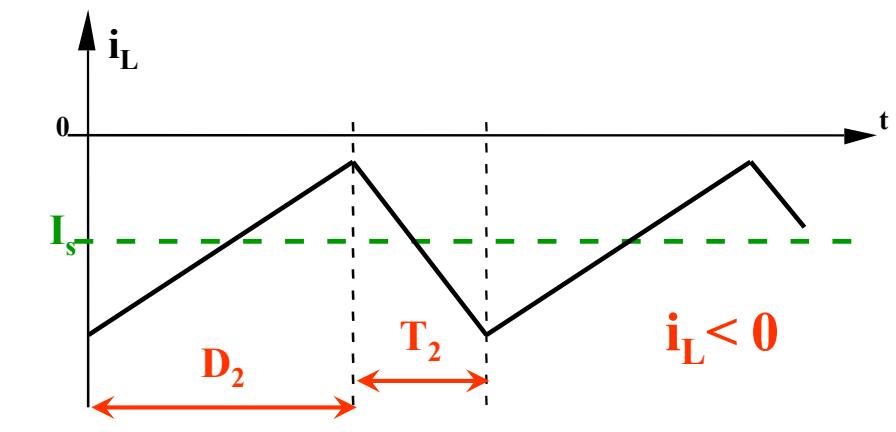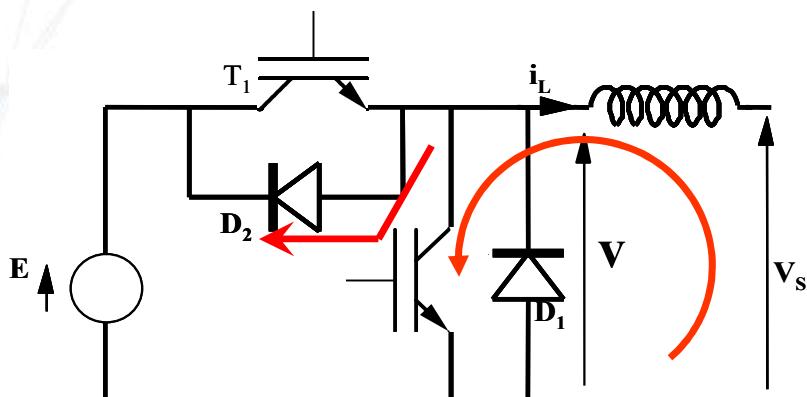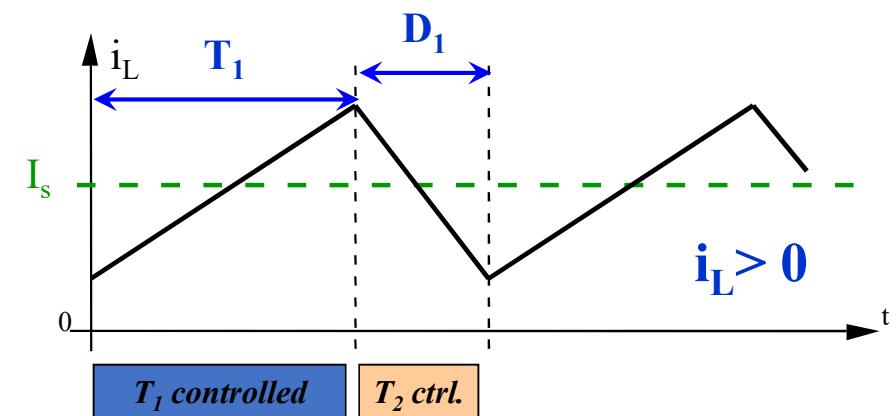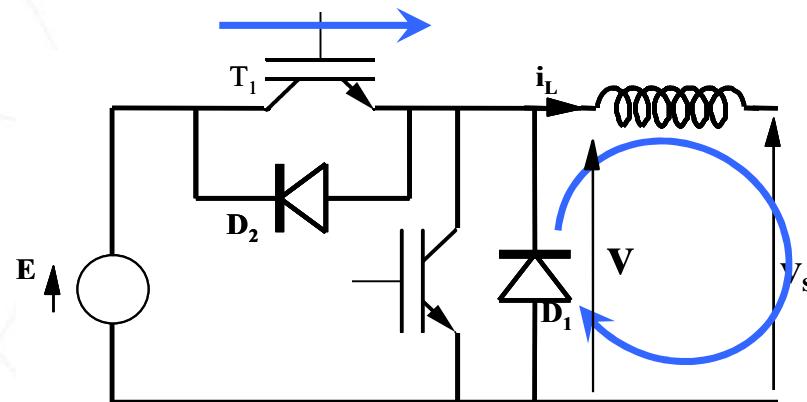

Introduction

Direct conversion

Reversible
choppers

2 quadrants chopper


4 quadrants chopper

Inverters

Closed loop
chopper control

Energy storage
based chopper

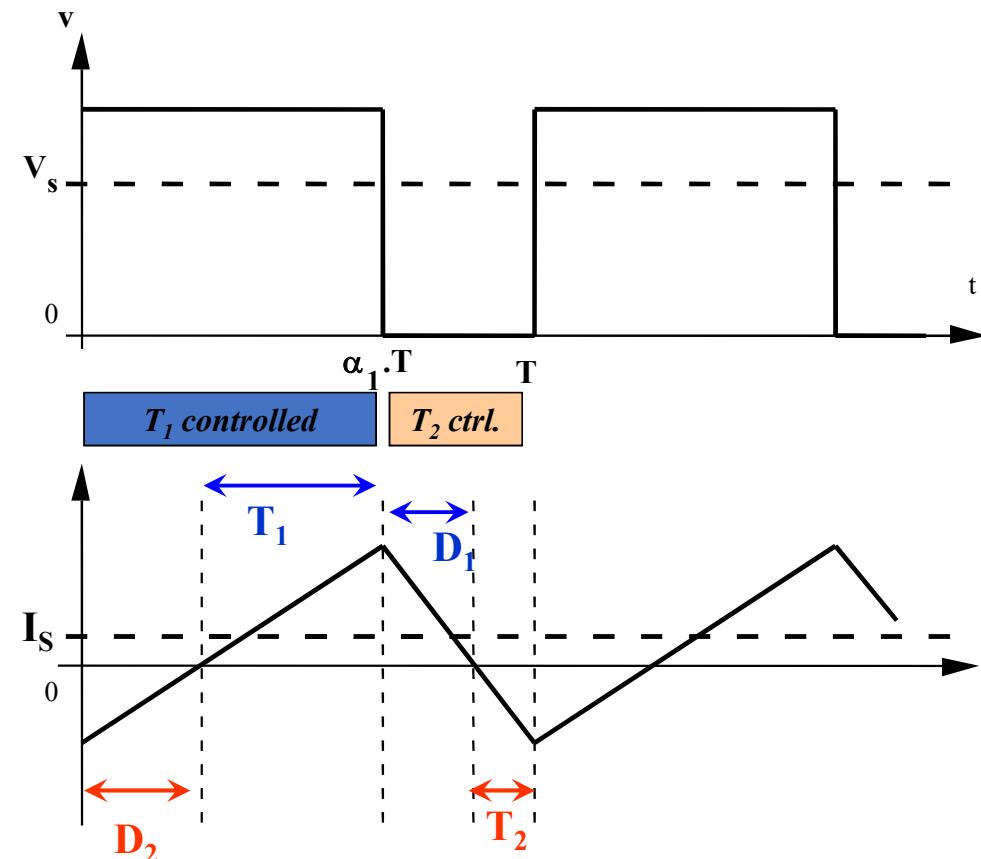Two quadrants chopper: Arbitrary output current



Introduction

Direct conversion

Reversible
choppers

2 quadrants chopper


4 quadrants chopper

Inverters

Closed loop
chopper control

Energy storage
based chopper

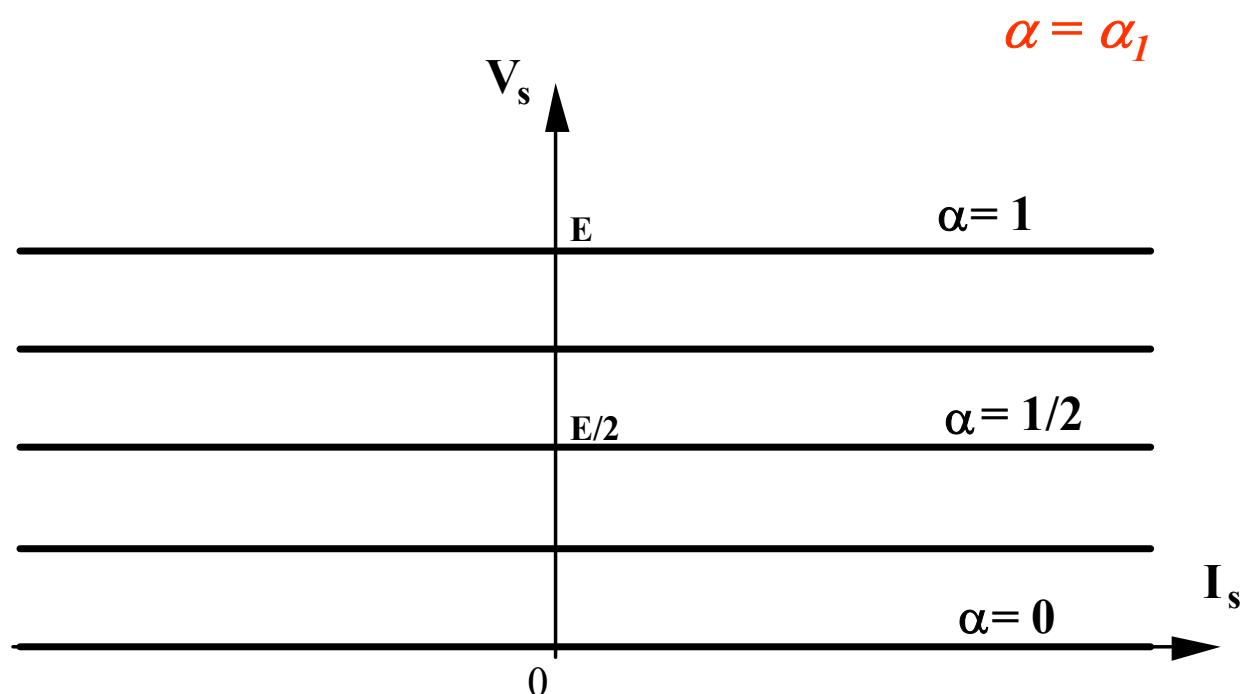Two quadrants chopper: Output characteristics grid



Introduction

Direct conversion

Reversible
choppers

2 quadrants chopper


4 quadrants chopper

Inverters

Closed loop
chopper control

Energy storage
based chopper

4 quadrants chopper

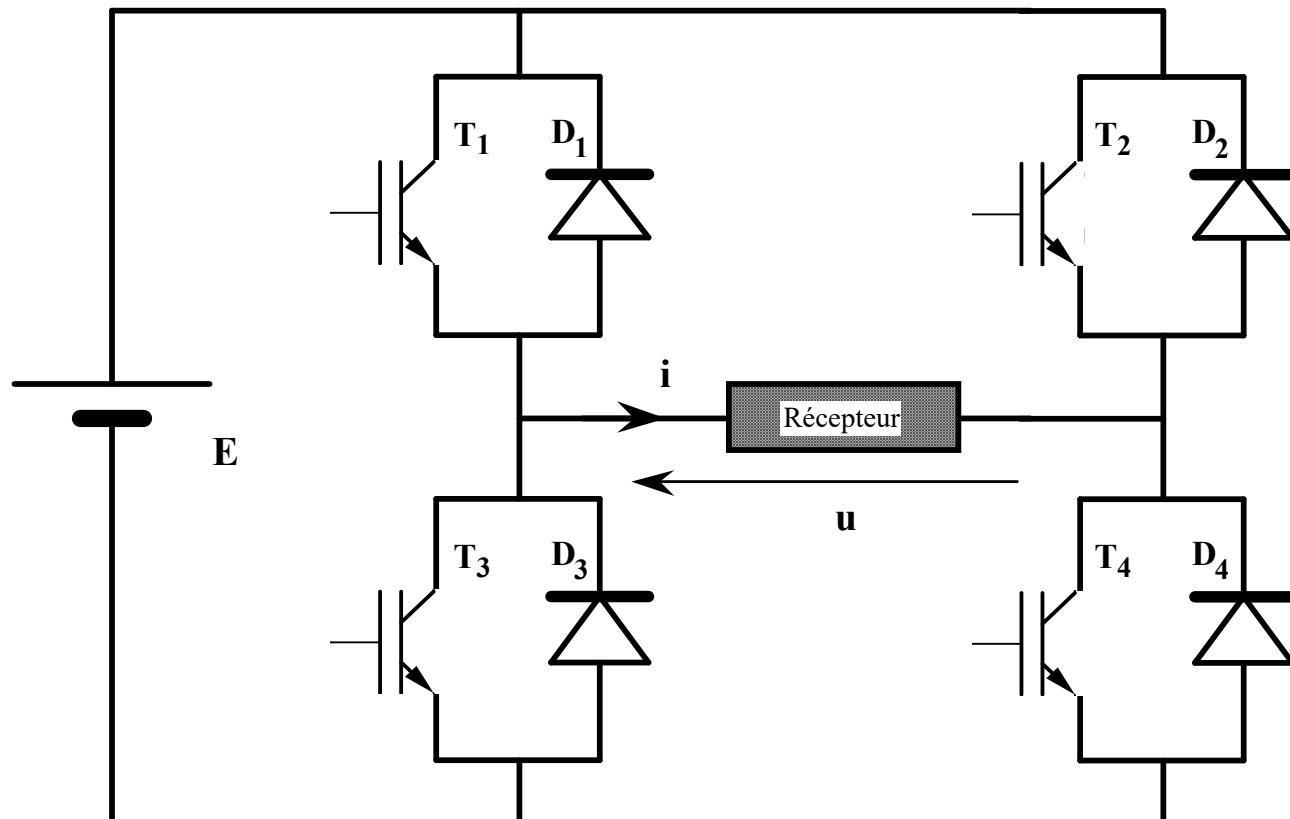

Introduction

Direct conversion

Reversible
choppers

2 quadrants chopper


4 quadrants chopper

Inverters

Closed loop
chopper control


Energy storage
based chopper

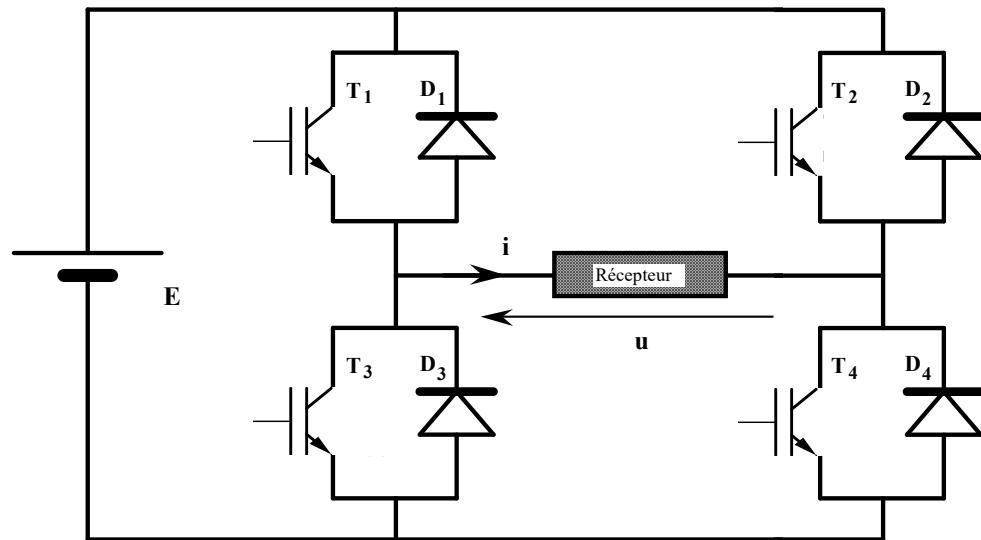4 quadrants chopper: Synchronous complementary control



$$\alpha_1 = \alpha_4 \quad \text{et} \quad \alpha_2 = \alpha_3$$

$$\alpha_2 = 1 - \alpha_1$$

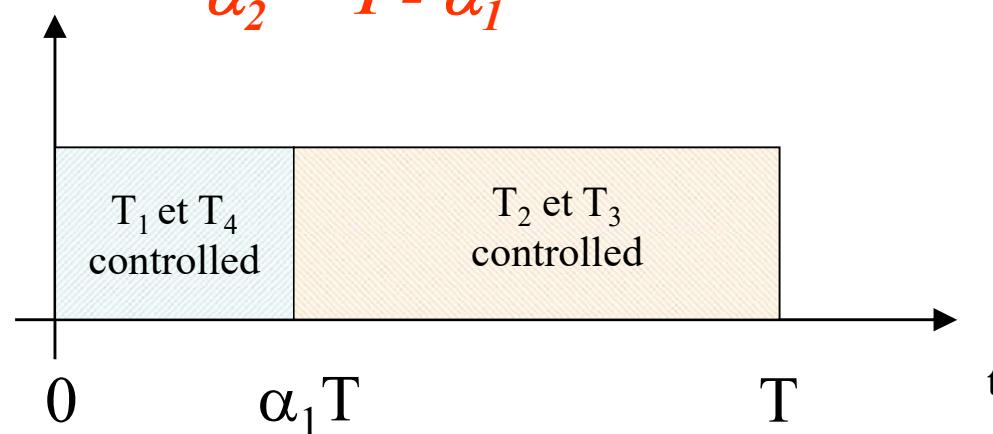

Introduction

Direct conversion

Reversible
choppers

2 quadrants chopper



4 quadrants chopper

Inverters

Closed loop
chopper control

Energy storage
based chopper

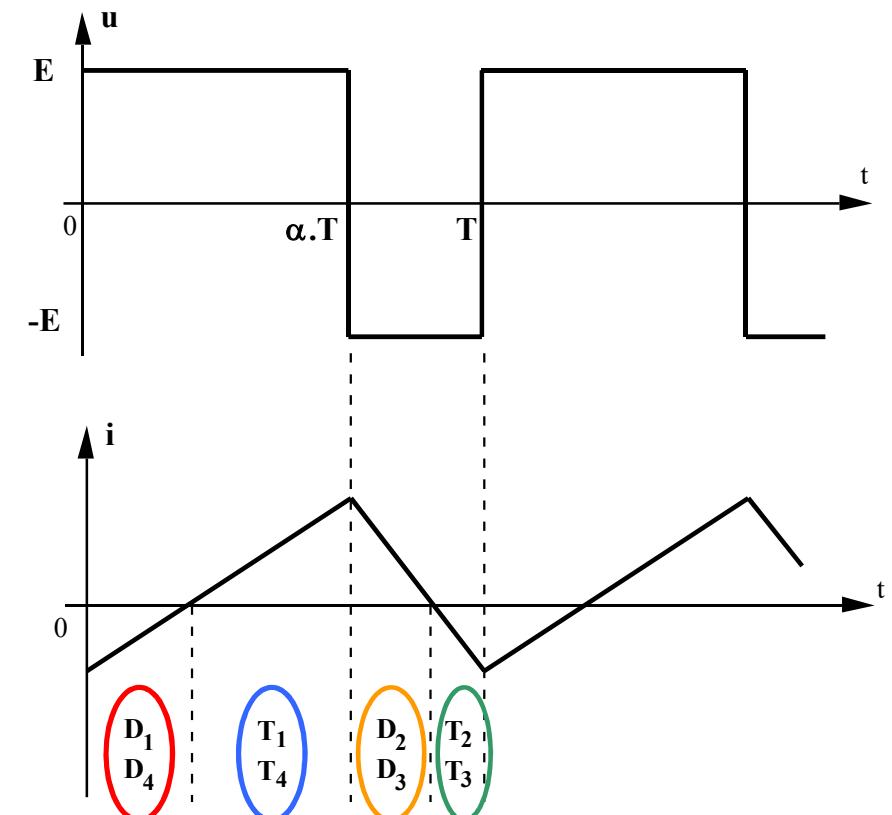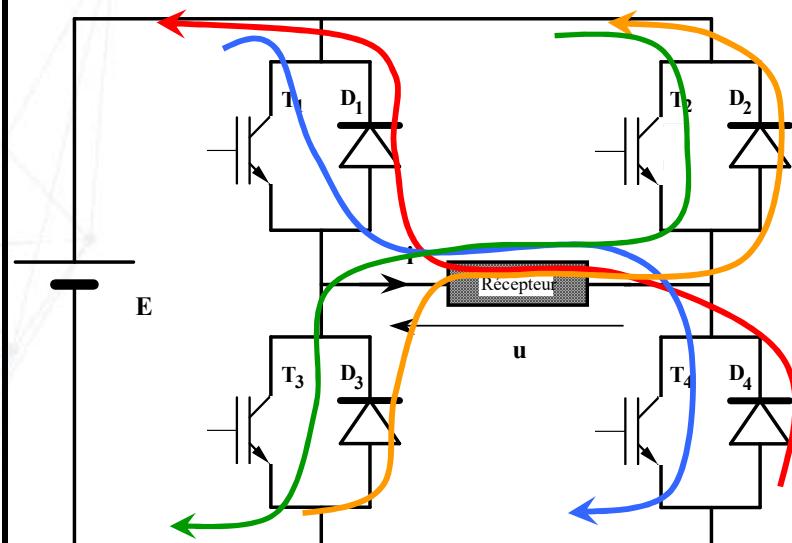4 quadrants chopper: Synchronous complementary control (chronograms)



Introduction

Direct conversion

Reversible choppers

2 quadrants chopper


4 quadrants chopper

Inverters


Closed loop
chopper control

Energy storage
based chopper

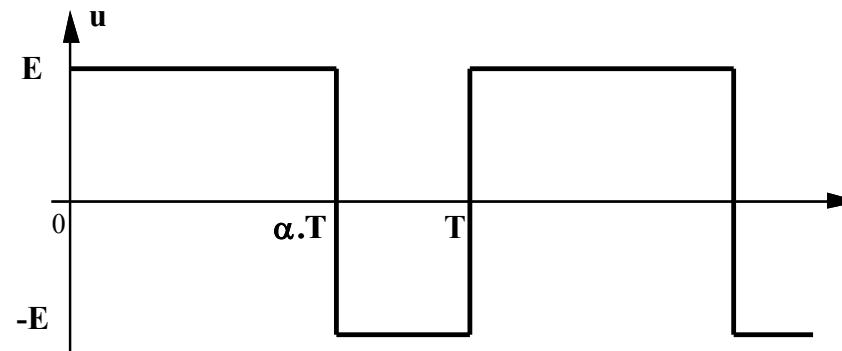4 quadrants chopper:
Synchronous complementary control (Average output voltage)


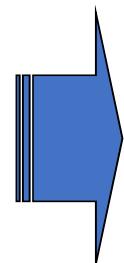
$$\langle u \rangle = (2\alpha - 1) \cdot E$$



*High voltage ripple: $2.E$
Low switching frequency*

Introduction

Direct conversion

Reversible
choppers

2 quadrants chopper


4 quadrants chopper

Inverters

Closed loop
chopper control

Energy storage
based chopper

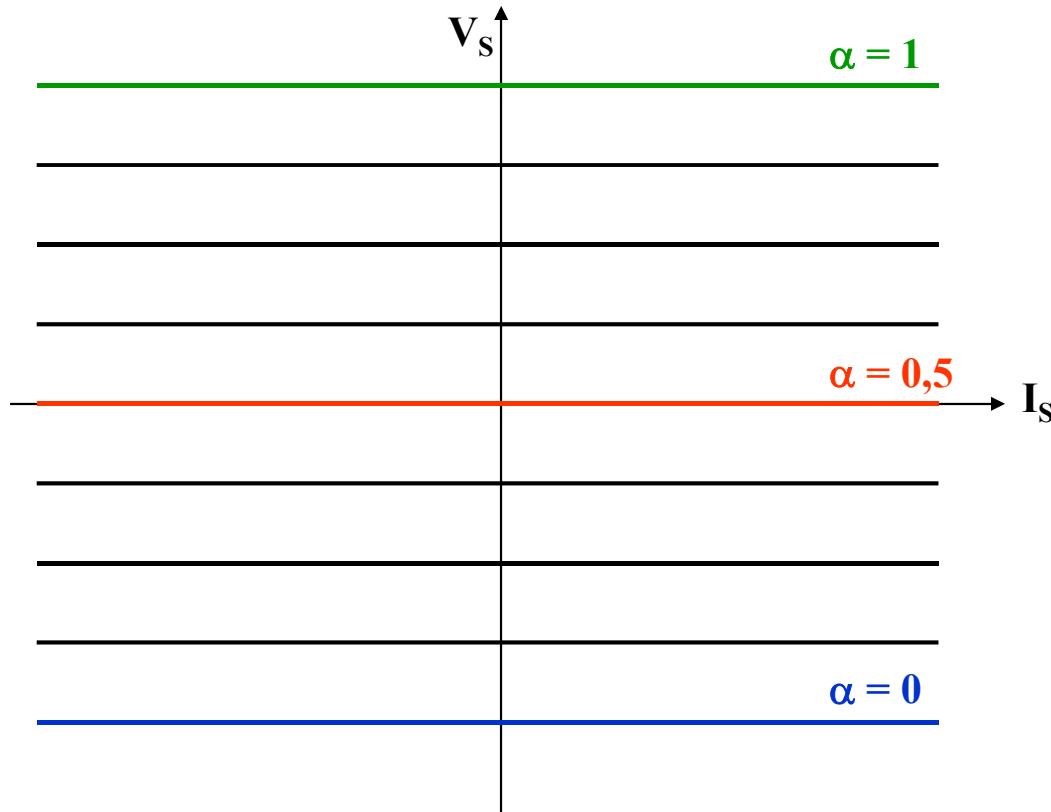4 quadrants chopper: Output characteristics



Introduction

Direct conversion

Reversible choppers

2 quadrants chopper


4 quadrants chopper

Inverters

Closed loop chopper control

Energy storage based chopper

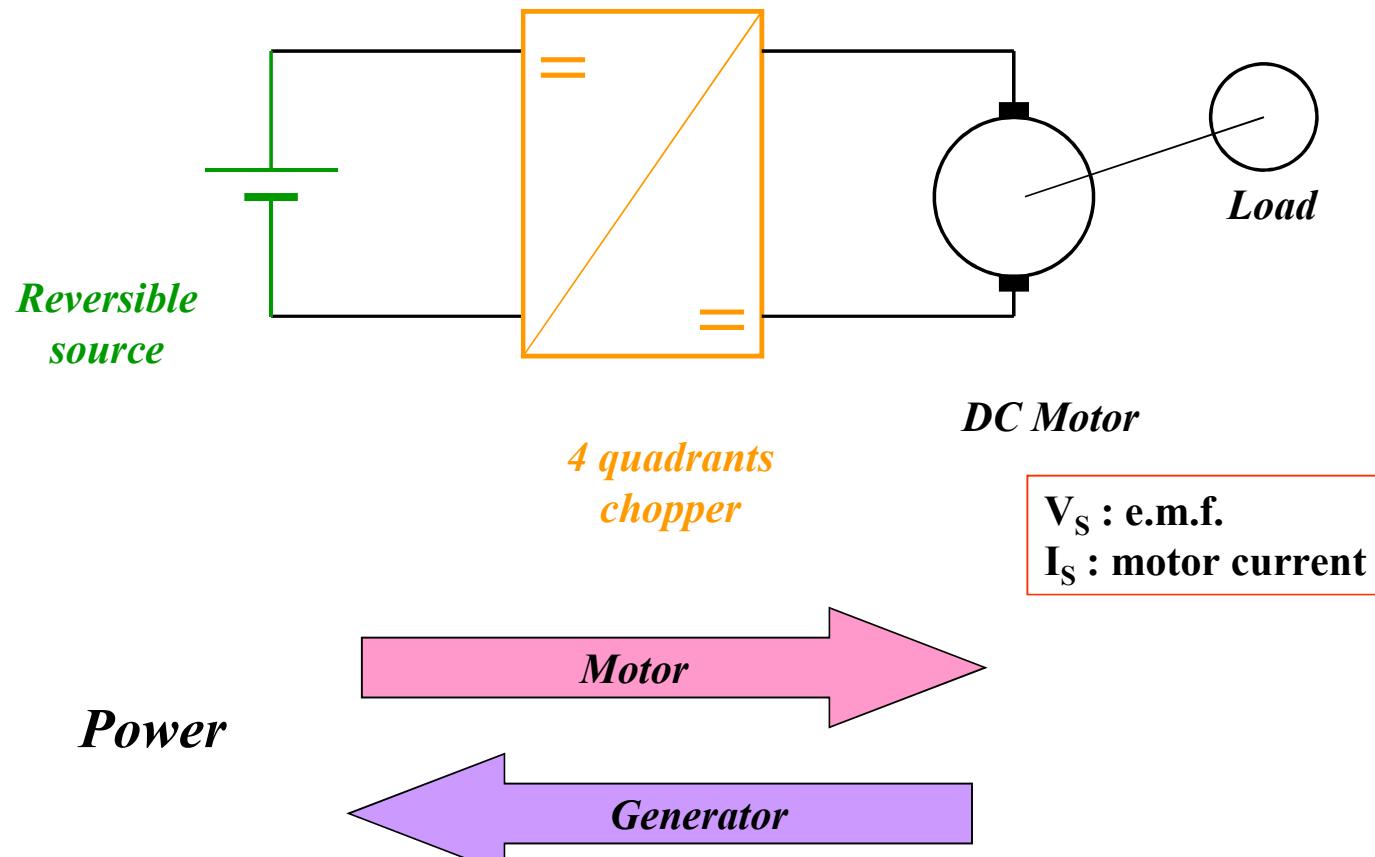4 quadrants chopper: control of a DC motor



Introduction

Direct conversion

Reversible
choppers


2 quadrants chopper
4 quadrants chopper

Inverters

Closed loop
chopper control

Energy storage
based chopper

4 quadrants chopper: working cycle

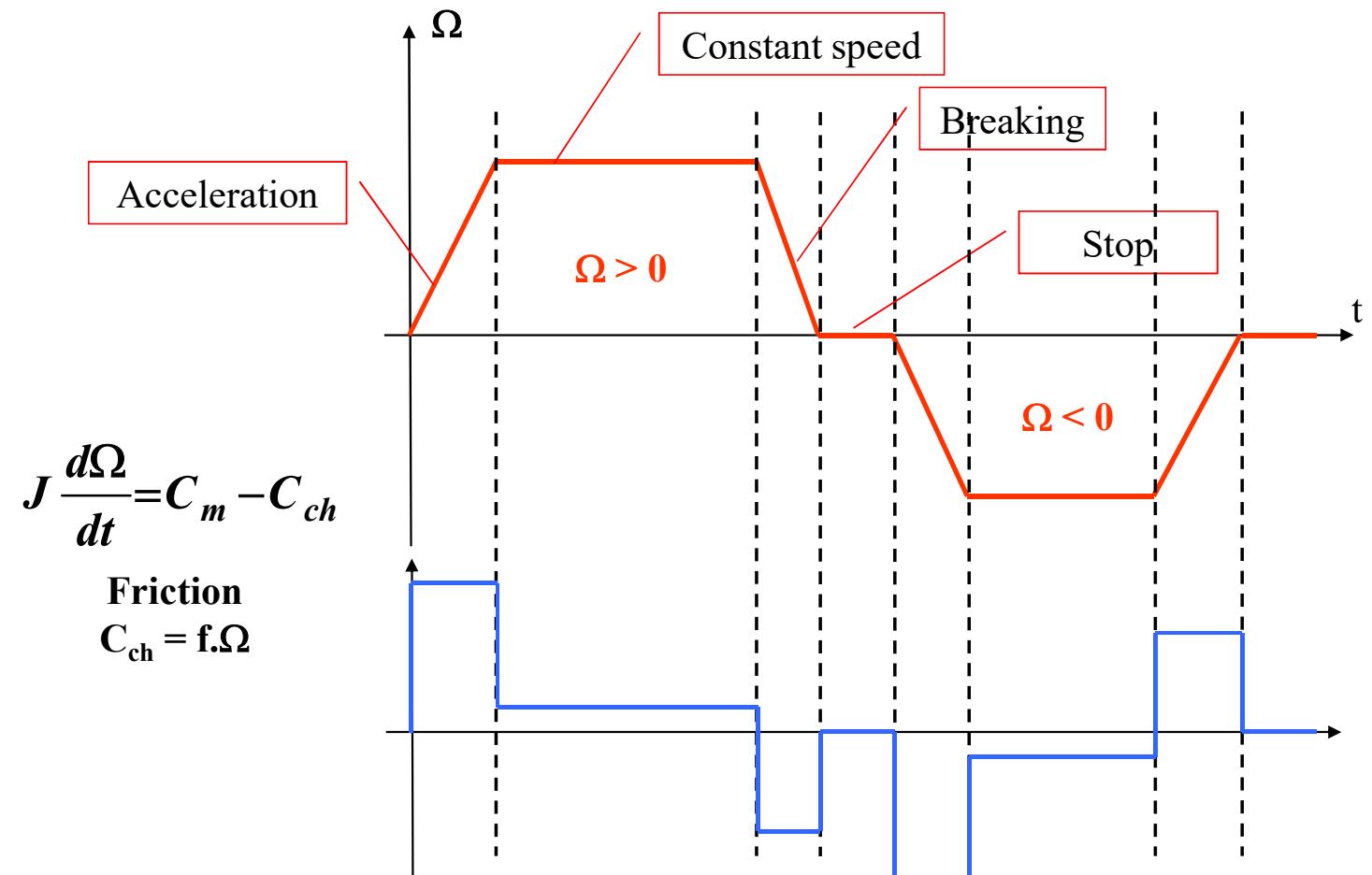

Introduction

Direct conversion

Reversible
choppers

2 quadrants chopper


4 quadrants chopper

Inverters

Closed loop
chopper control

Energy storage
based chopper

4 quadrants chopper: Operating point

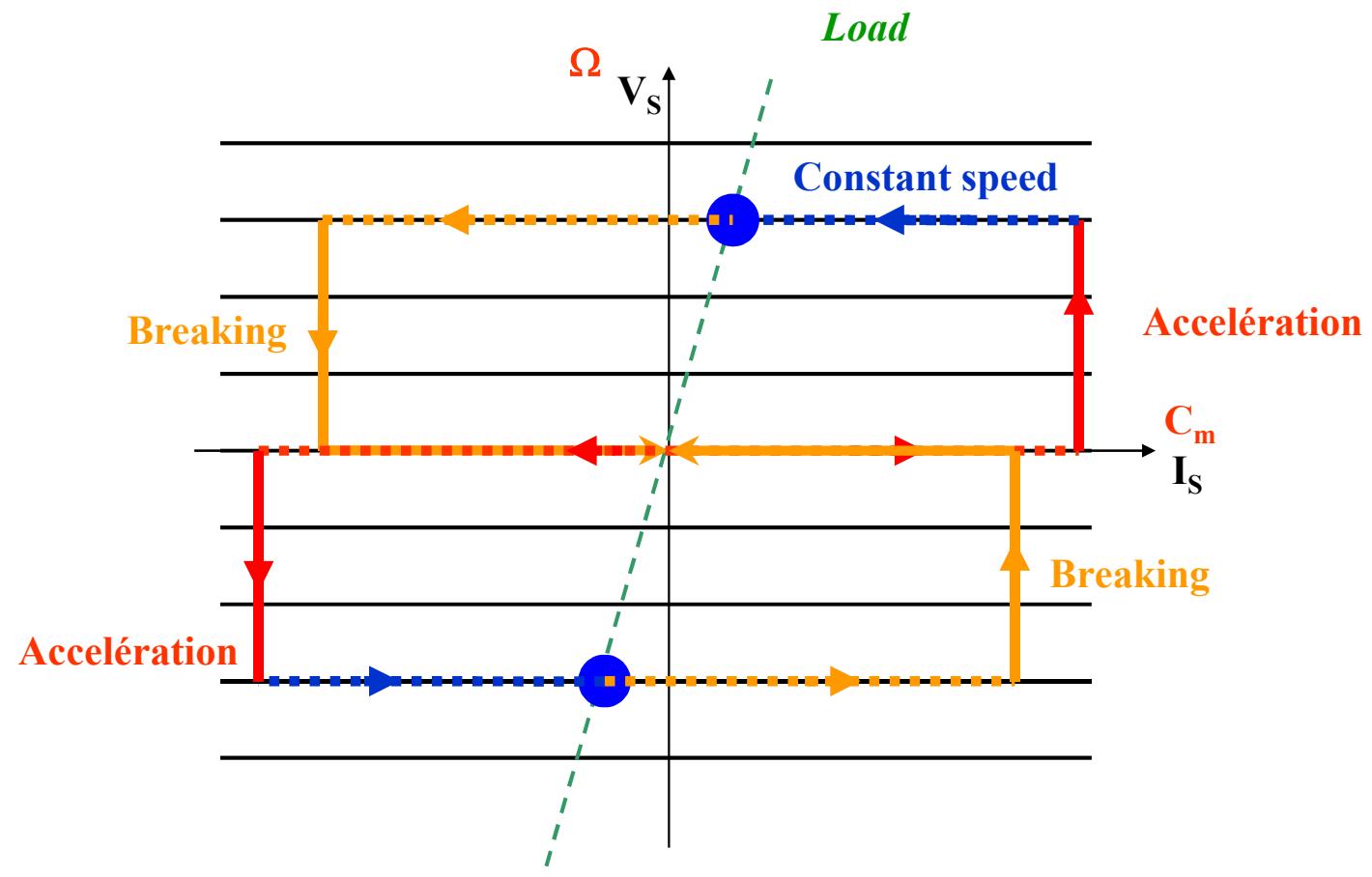

Introduction

Direct conversion

Reversible choppers

2 quadrants chopper


4 quadrants chopper

Inverters

Closed loop chopper control

Energy storage based chopper

4 quadrants chopper: additional control

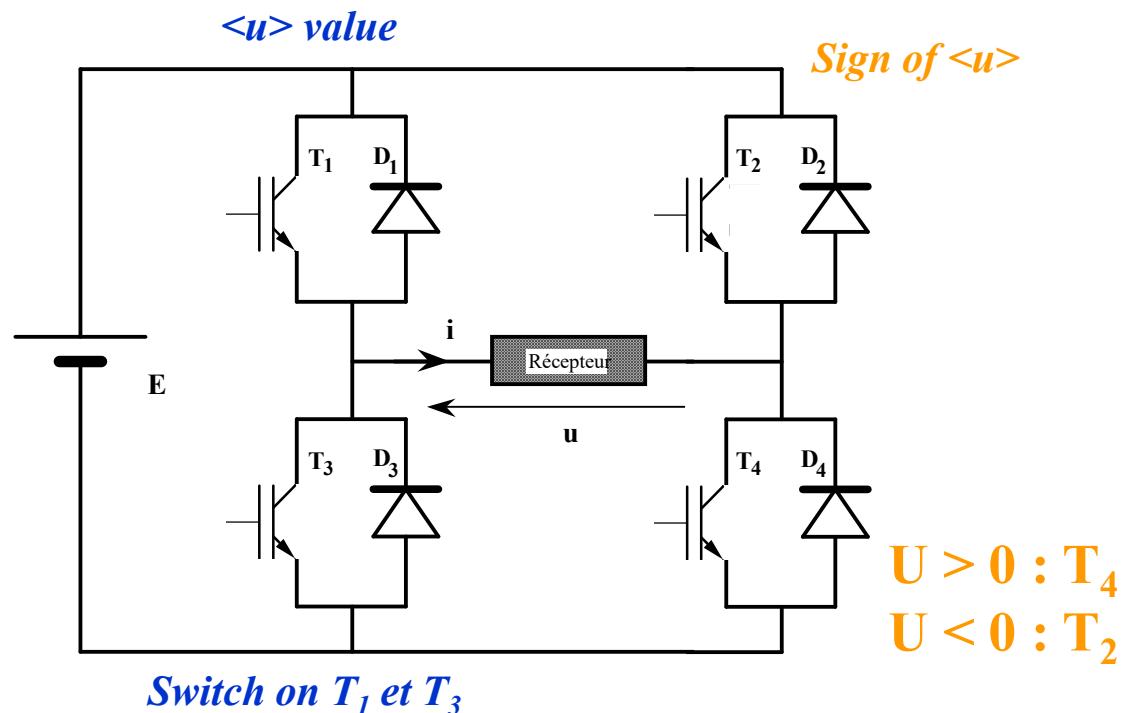

$U > 0 : T_4$
 $U < 0 : T_2$

Introduction

Direct conversion

Reversible choppers

2 quadrants chopper


4 quadrants chopper

Inverters

Closed loop chopper control

Energy storage based chopper

4 quadrants chopper: additional control

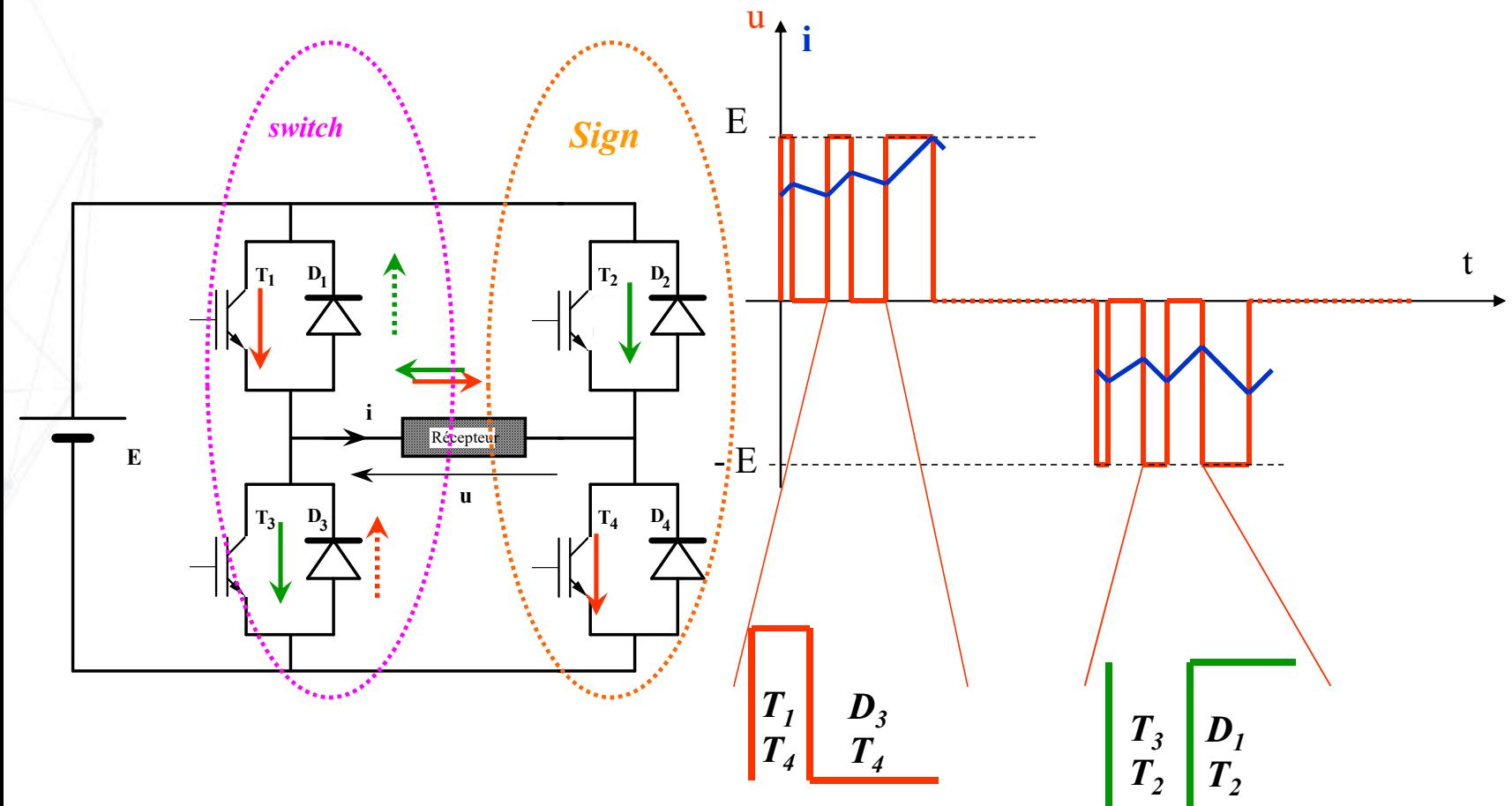

Introduction

Direct conversion

Reversible choppers

2 quadrants chopper


4 quadrants chopper

Inverters

Closed loop chopper control


Energy storage based chopper

4 quadrants chopper: additional control

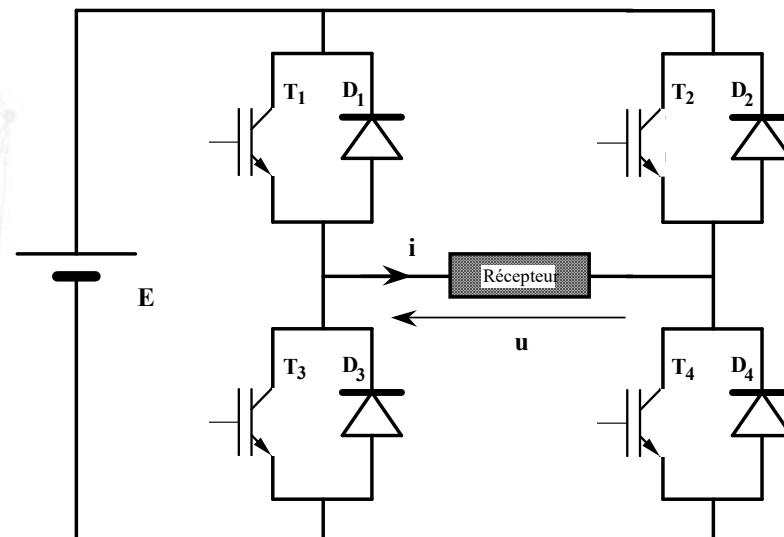

$$U = +/- \alpha \cdot E$$

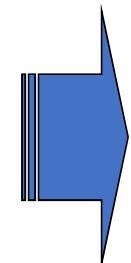Average value during
a switching time T_d



*Voltage ripple reduced: E
Switching only on T_1/T_3 : losses reduced
Instabilities around 0V ! !*

Introduction

Direct conversion

Reversible
choppers


2 quadrants chopper
4 quadrants chopper

Inverters

Closed loop
chopper control

Energy storage
based chopper

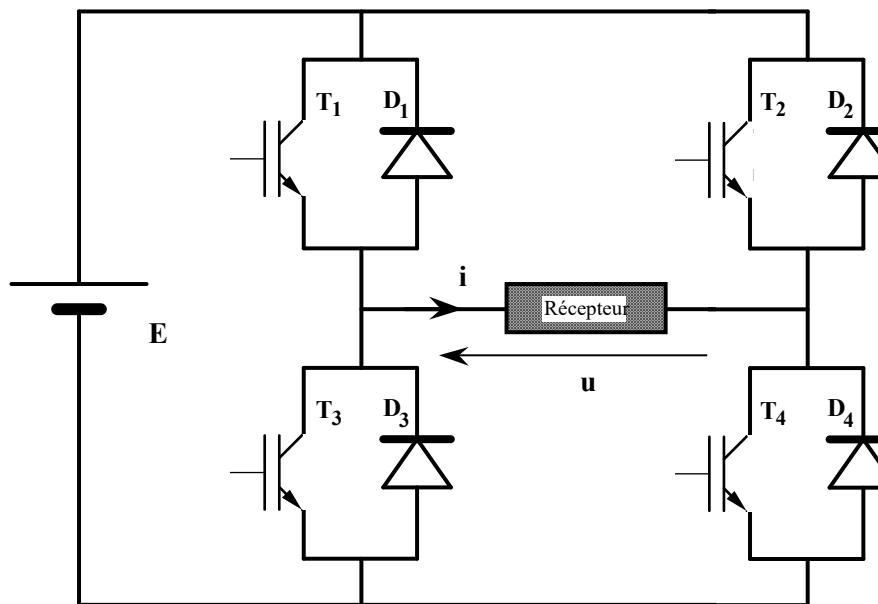4 quadrants chopper: Shifted complementary control



Switching on T_1 and T_3 at $t = 0$

Switching on T_2 and T_4 at $t = T/2$

$$\alpha_1 = \alpha_4$$

$$\alpha_2 = \alpha_3$$

$$\alpha_3 = 1 - \alpha_1$$

$$\alpha_4 = 1 - \alpha_2$$

Introduction

Direct conversion

Reversible
choppers

2 quadrants chopper



4 quadrants chopper

Inverters

Closed loop
chopper control

Energy storage
based chopper

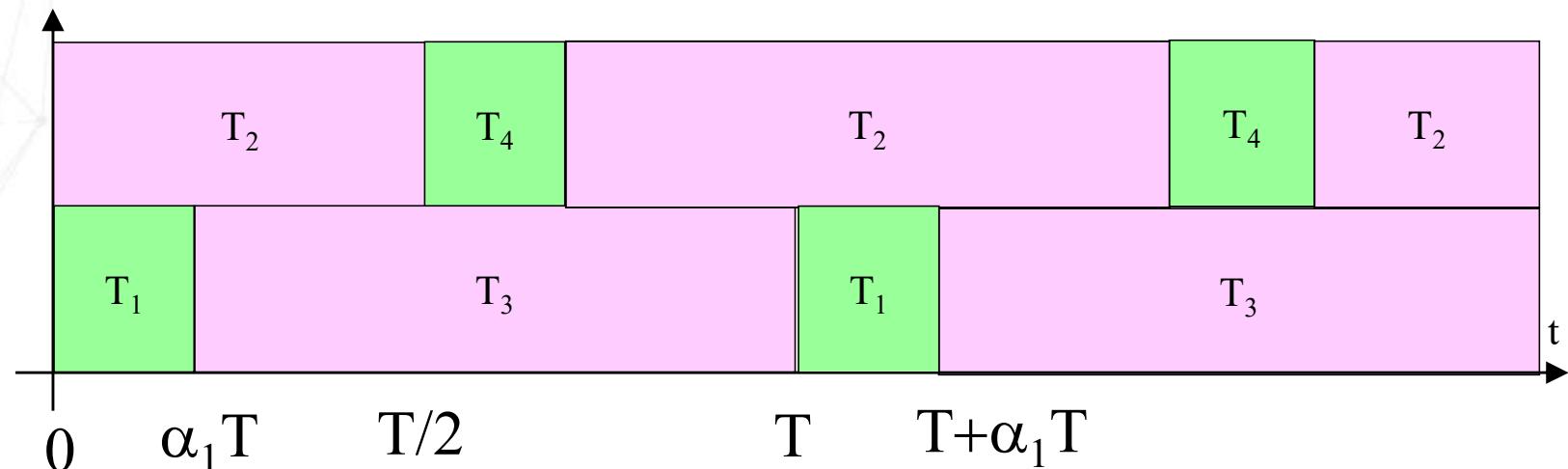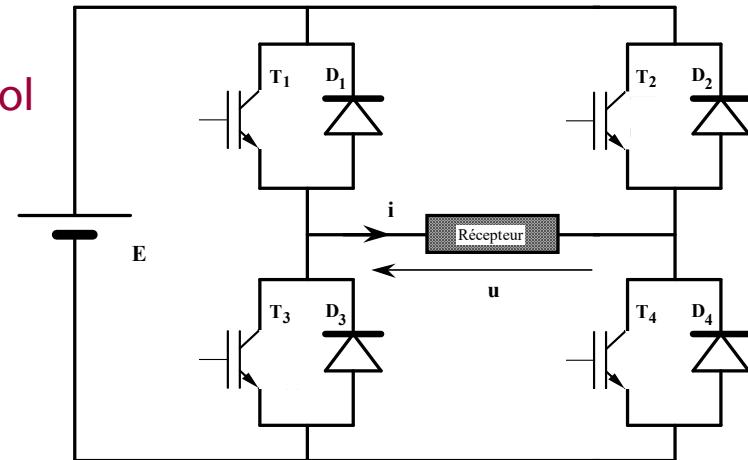4 quadrants chopper: Shifted complementary control



Introduction

Direct conversion

Reversible choppers

2 quadrants chopper



4 quadrants chopper

Inverters


Closed loop
chopper control

Energy storage
based chopper

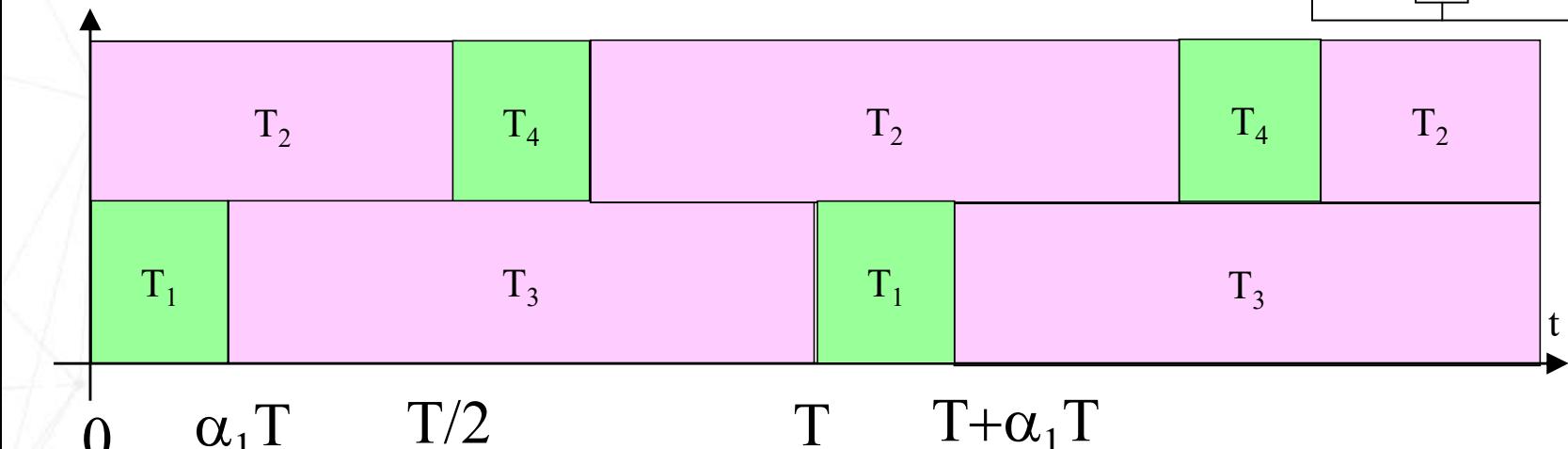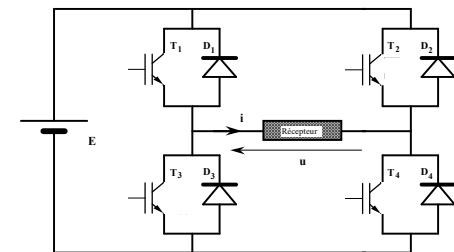4 quadrants chopper: Shifted complementary control



$$\alpha_1 < 0,5$$

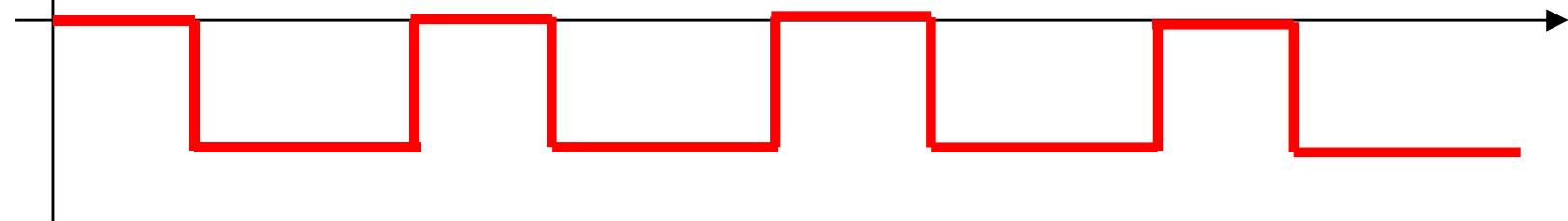

Introduction

Direct conversion

Reversible
choppers

2 quadrants chopper


4 quadrants chopper

Inverters


Closed loop
chopper control

Energy storage
based chopper

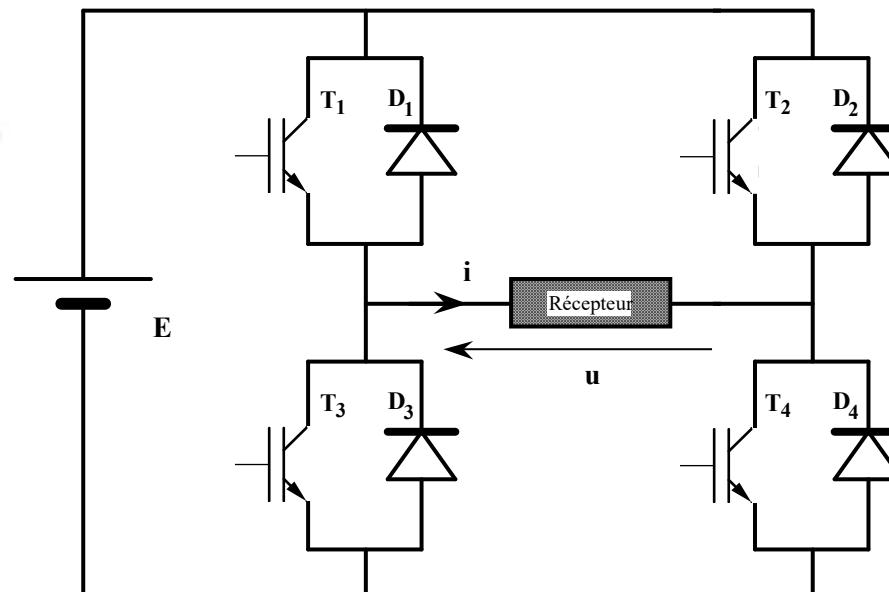4 quadrants chopper: Shifted complementary control



$$U = (2\alpha - 1) \cdot E$$

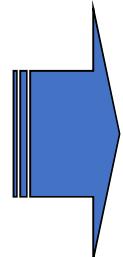

*Voltage ripple reduced: E
High switching frequency
=> PWM*

Introduction

Direct conversion

Reversible
choppers

2 quadrants chopper

4 quadrants chopper

Inverters

Closed loop
chopper control


Energy storage
based chopper

4 quadrants chopper: Stepper motor control

Operation principle: full step

For a clockwise rotation, the sequence is:

B1	B2
+I	0
0	+I
-I	0
0	-I

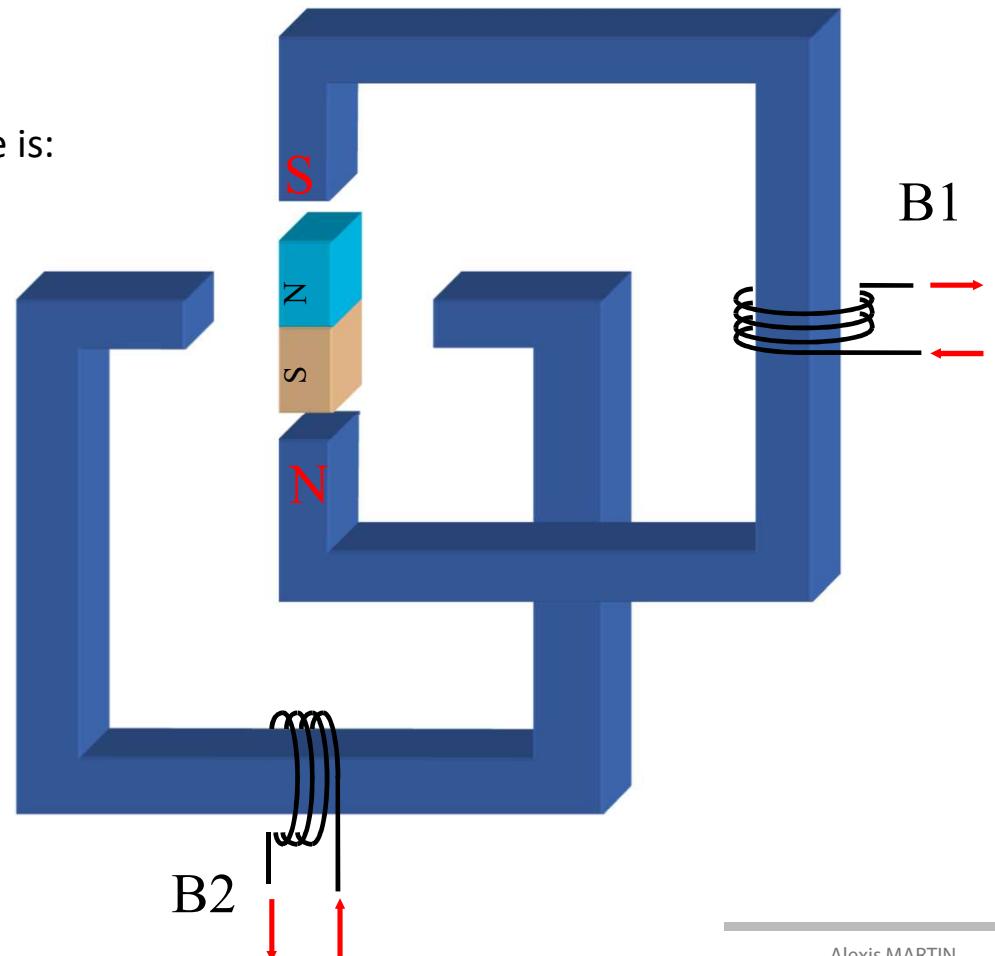

Introduction

Direct conversion

Reversible
choppers

2 quadrants chopper

4 quadrants chopper

Inverters

Closed loop
chopper control


Energy storage
based chopper

4 quadrants chopper: Stepper motor control

Operation principle: half step

For a clockwise rotation:

	B1	B2
I+	0	
I+	I+	
0	I+	
I-	I+	
I-	0	
I-	I-	
0	I-	
I+	I-	

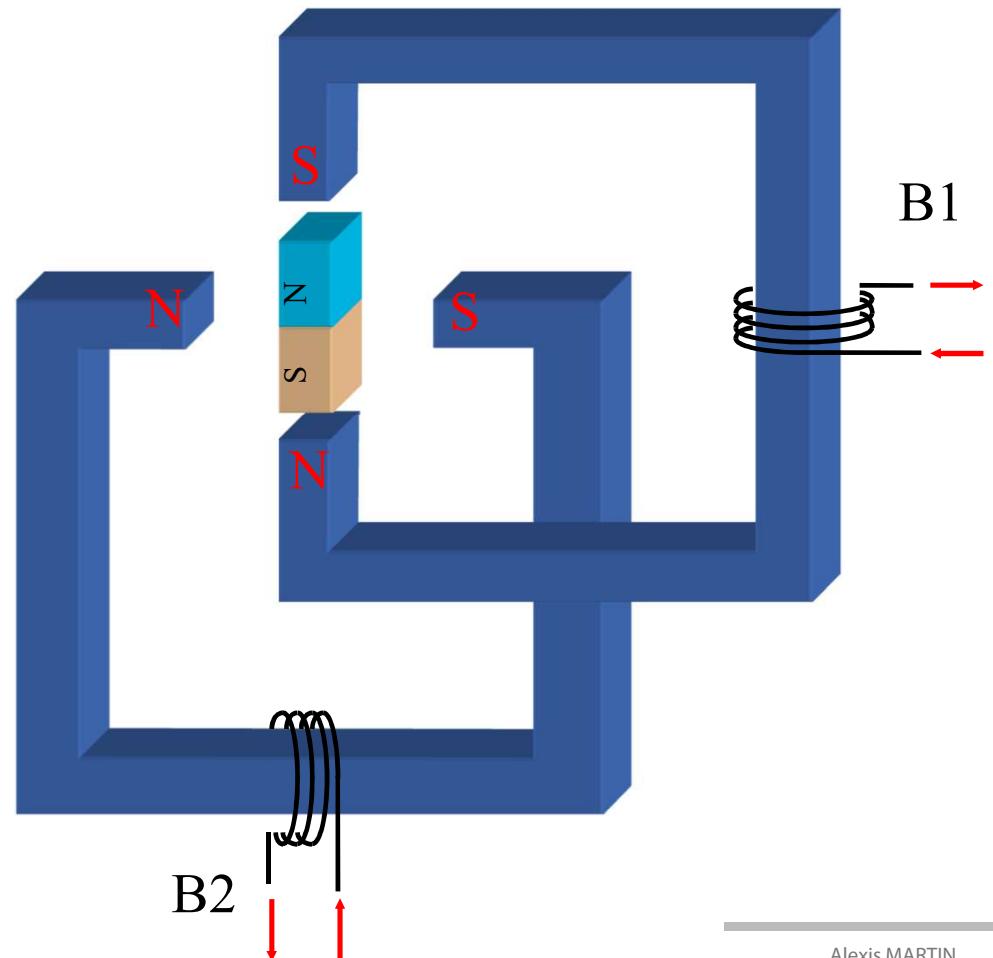

Introduction

Direct conversion

Reversible choppers

2 quadrants chopper



4 quadrants chopper

Inverters

Closed loop chopper control

Energy storage based chopper

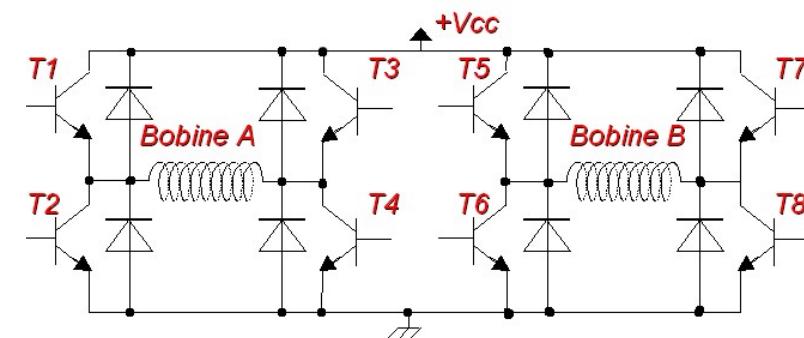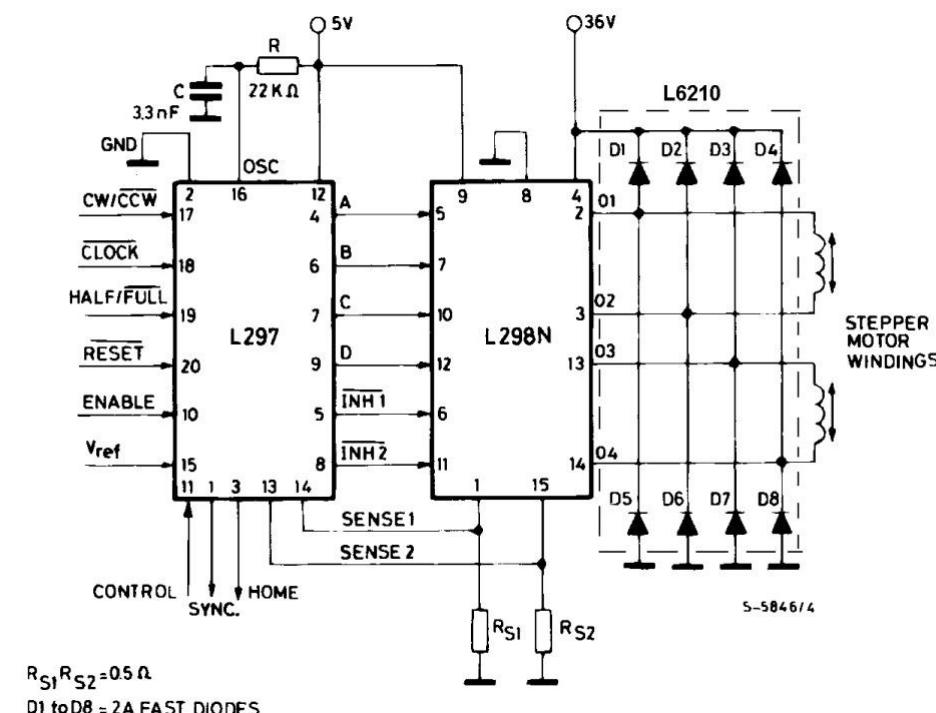4 quadrants chopper: Stepper motor control



Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Inverter

Introduction

Direct conversion

Reversible
choppers

Inverters

Single phase inverter

Three phase inverter

Three phase motor
control


Closed loop
chopper control

Energy storage
based chopper

ENSEA

Beyond Engineering

Single phase inverter

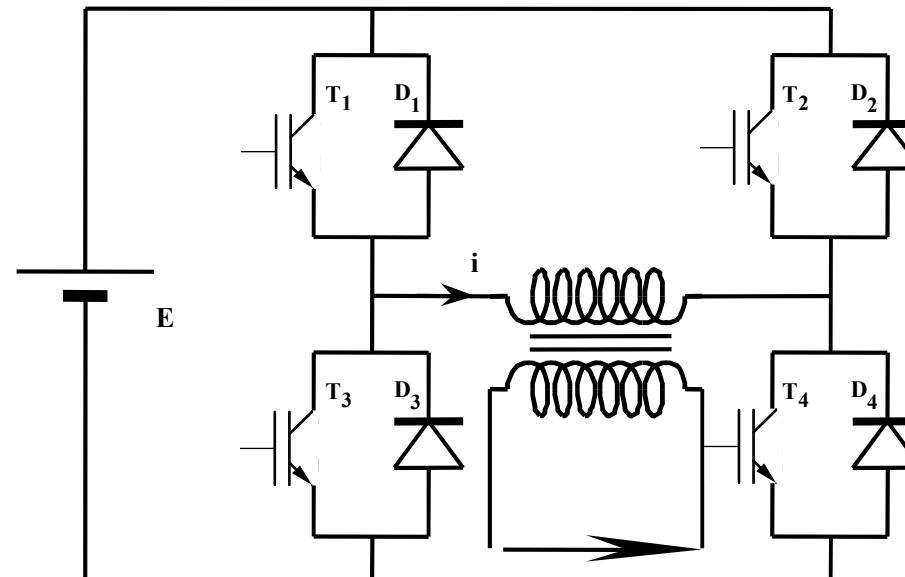

$$\alpha = \frac{1}{2} + \delta_\alpha \sin(\omega t)$$

Introduction

Direct conversion

Reversible
choppers

Inverters

Single phase inverter

Three phase inverter

Three phase motor
control


Closed loop
chopper control

Energy storage
based chopper

ENSEA

Beyond Engineering

Single phase inverter: PWM control

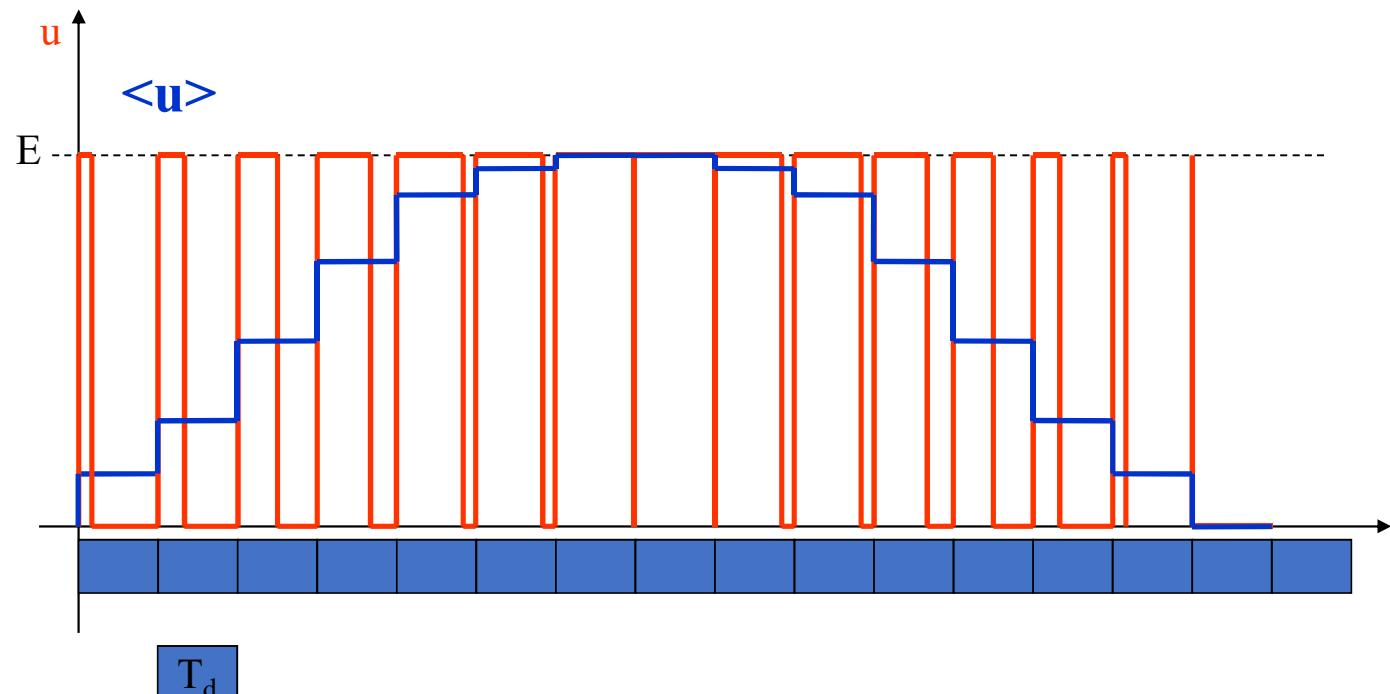

Introduction

Direct conversion

Reversible
choppers

Inverters

Single phase inverter

Three phase inverter

Three phase motor
control

Closed loop
chopper control


Energy storage
based chopper

ENSEA

Beyond Engineering

Three phase inverter
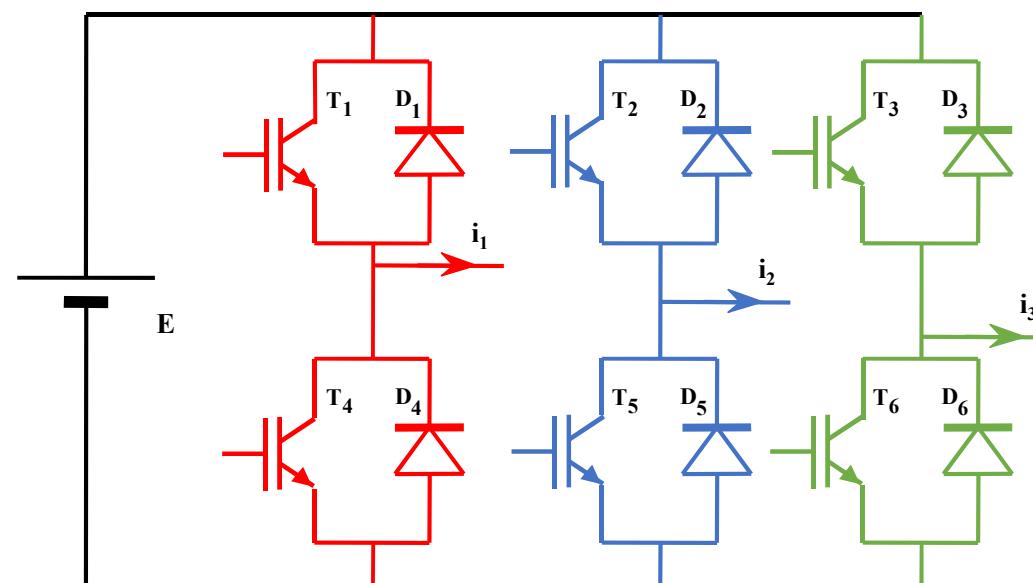
$$\alpha_2 = \frac{1}{2} + \delta_\alpha \sin(\omega t - \frac{2\pi}{3})$$



$$\alpha_1 = \frac{1}{2} + \delta_\alpha \sin(\omega t)$$

$$\alpha_3 = \frac{1}{2} + \delta_\alpha \sin(\omega t + \frac{2\pi}{3})$$

Introduction

Direct conversion

Reversible
choppers

Inverters

Single phase inverter
Three phase inverter


Three phase motor
control

Closed loop
chopper control

Energy storage
based chopper

ENSEA
Beyond Engineering

3 Phases motor control : BLDC

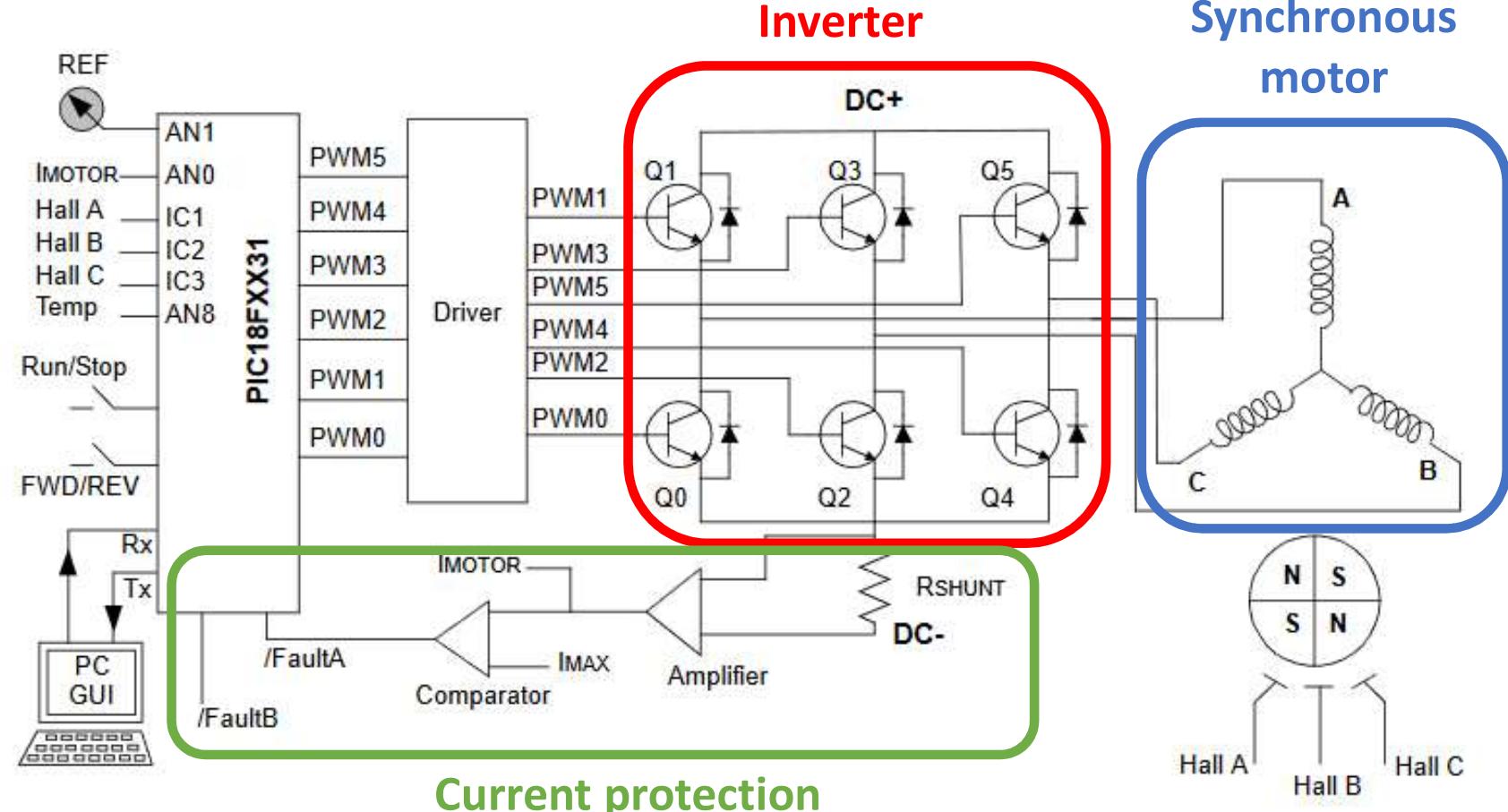

Current protection

AN899 (Microchip) : Brushless DC Motor Control Using PIC18FXX31 MCUs

Introduction

Direct conversion

Reversible
choppers

Inverters

Single phase inverter
Three phase inverter



Three phase motor
control

Closed loop
chopper control

Energy storage
based chopper

ENSEA
Beyond Engineering

3 Phases motor control : BLDC

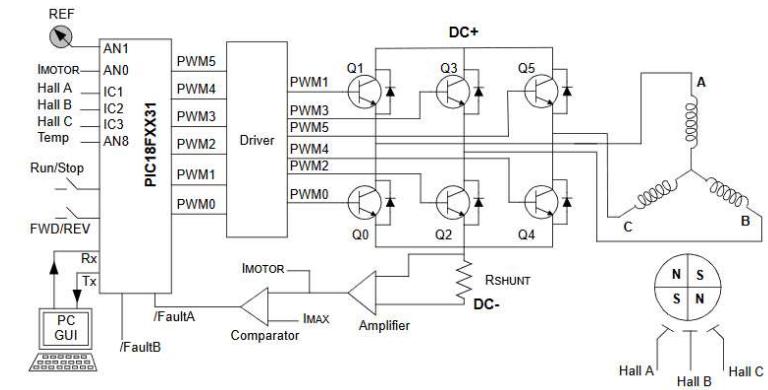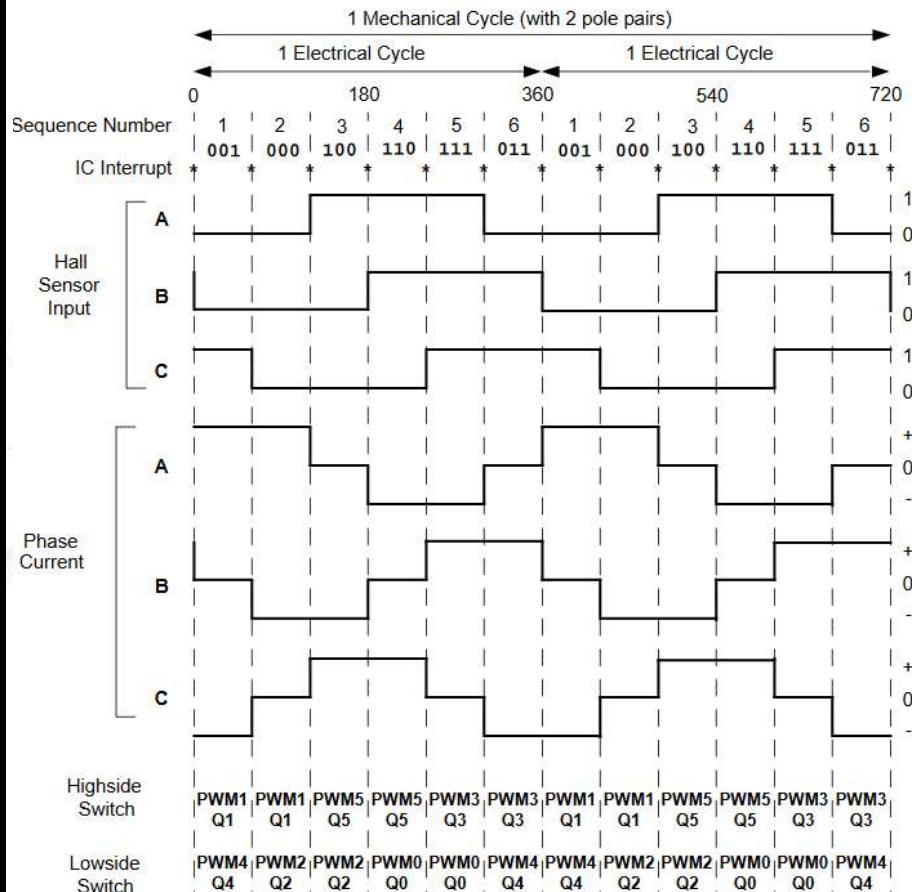

Sequence Number	Hall Sensor Input			Active PWMs		Phase Current			
	A	B	C	A	B	C	A	B	C
1	0	0	1	PWM1(Q1)	PWM4(Q4)	DC+	Off	DC-	
2	0	0	0	PWM1(Q1)	PWM2(Q2)	DC+	DC-	Off	
3	1	0	0	PWM5(Q5)	PWM2(Q2)	Off	DC-	DC+	
4	1	1	0	PWM5(Q5)	PWM0(Q0)	DC-	Off	DC+	
5	1	1	1	PWM3(Q3)	PWM0(Q0)	DC-	DC+	Off	
6	0	1	1	PWM3(Q3)	PWM4(Q4)	Off	DC+	DC-	

AN899 (Microchip) : Brushless DC Motor Control Using PIC18FXX31 MCUs

Introduction

Direct conversion

Reversible
choppers

Inverters

**Closed loop
chopper control**

Energy storage
based chopper



Closed loop chopper control

Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control

Models

Current control


Speed control

Energy storage
based chopper



Beyond Engineering

Closed loop chopper control

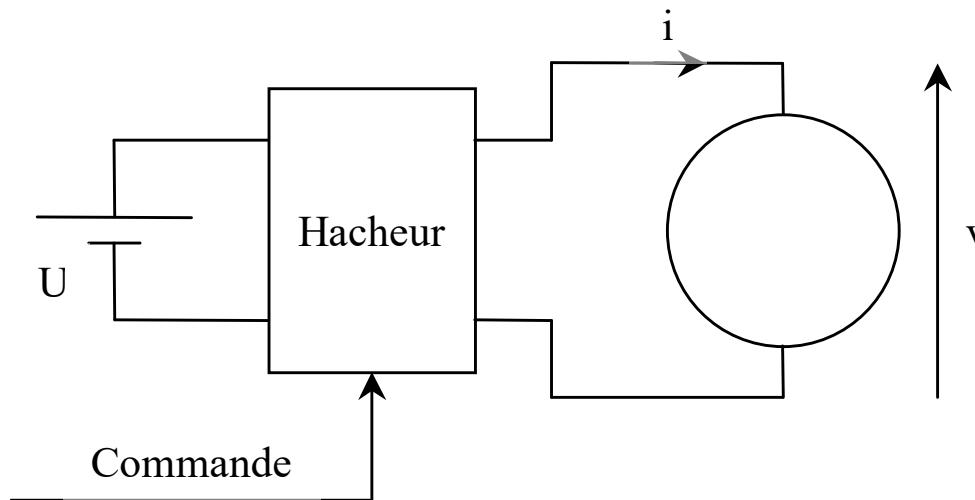

Possible control : speed / torque

Voltage / current

Introduction

Direct conversion

Reversible choppers

Inverters

Closed loop chopper control

Models

Current control

Speed control

Energy storage based chopper

ENSEA

Beyond Engineering

DC motor model

Electrical equation

$$u = e + r \cdot i + L \cdot \frac{di}{dt}$$

Mechanical equation

$$J \frac{d\Omega}{dt} + f\Omega = \gamma_m - \gamma_r$$

Coupling equations



$$e = k_\phi \cdot \Omega \quad \gamma_m = k_\phi \cdot i$$

$$\tau_{em} = \frac{J \cdot R}{k_\phi^2 + R \cdot f}$$

electromechanical time constant

$$\tau_e = \frac{L}{R}$$

electrical time constant

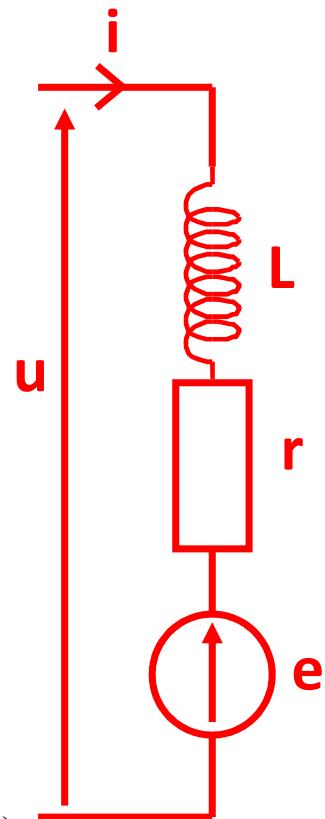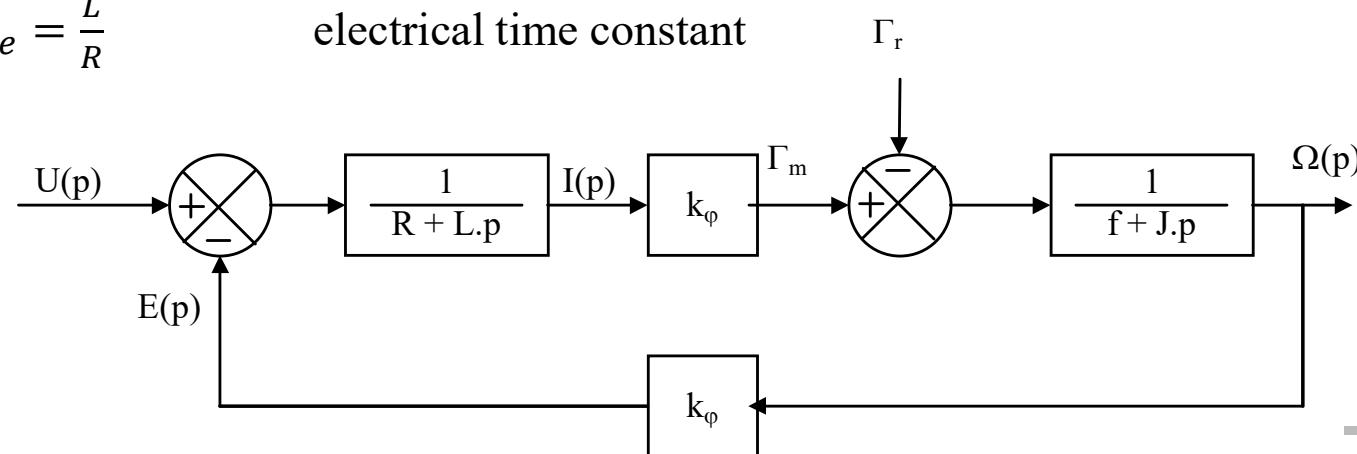

Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control

Models

Current control


Speed control

Energy storage
based chopper

ENSEA

Beyond Engineering

Reversible structure

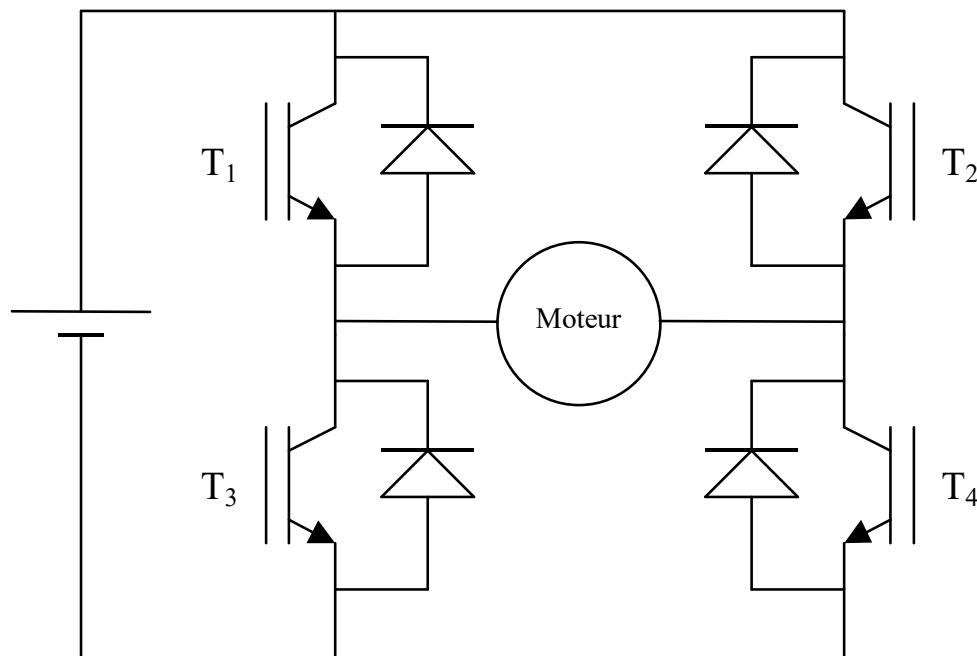

Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop chopper control

Models

Current control

Speed control

Energy storage
based chopper



Beyond Engineering

Chopper model

$$G_h(p) = \frac{U}{V_{dc}} \cdot e^{-\frac{T_d}{2} \cdot p}$$

(Average delay $T_d / 2$)

$$G_h(p) \approx \frac{G_0}{1 + \tau_h \cdot p} \quad \text{with} \quad \tau_h = \frac{T_d}{2} \quad \text{and} \quad G_0 = \frac{U}{V_{dc}}$$

(linearization)

Introduction

Direct conversion

Reversible
choppers

Inverters

**Closed loop
chopper control**

Models

Current control



Speed control

Energy storage
based chopper

ENSEA

Beyond Engineering

Current control

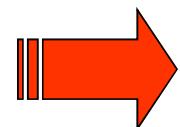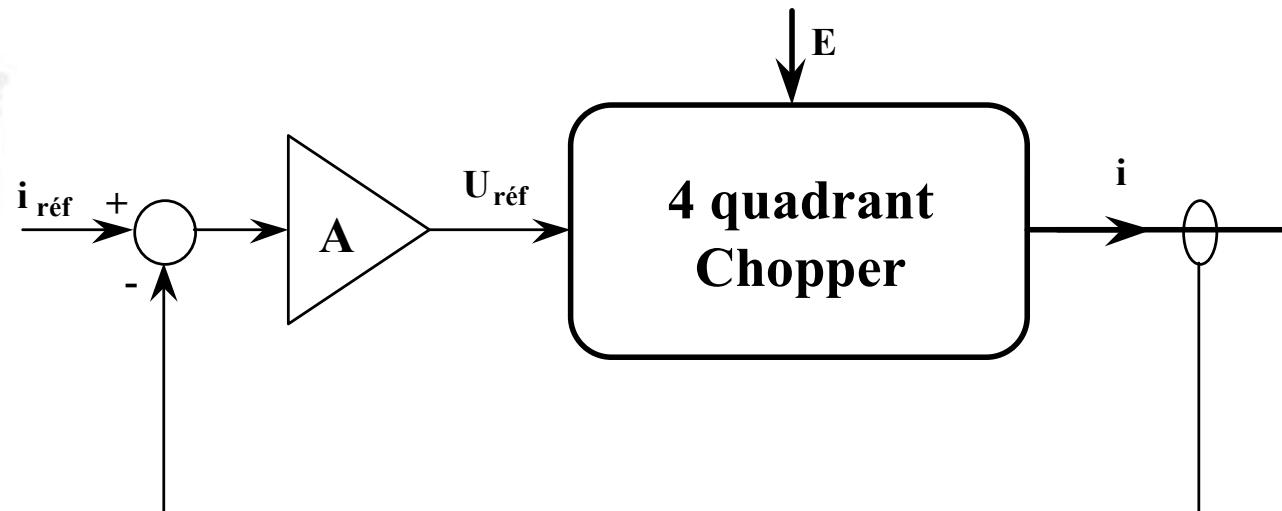

Torque control of a motor

Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control

Models

Current control

Speed control

Energy storage
based chopper



ENSEA

Beyond Engineering

Current loop

Armature current regulation

- *Current regulation*
- *Torque control ($G = k_\varphi \cdot I$)*
- *Better transient response*
- *Need a high performance sensor*
- *Simple Regulation (P.I.)*

Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control

Models

Current control


Speed control

Energy storage
based chopper




Current loop: Current sensor

Resistor = shunt

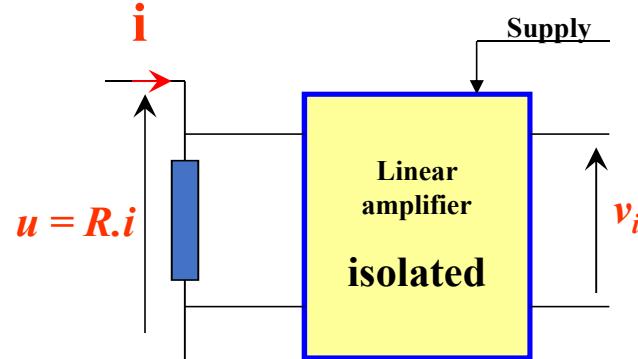

Hall effect sensor

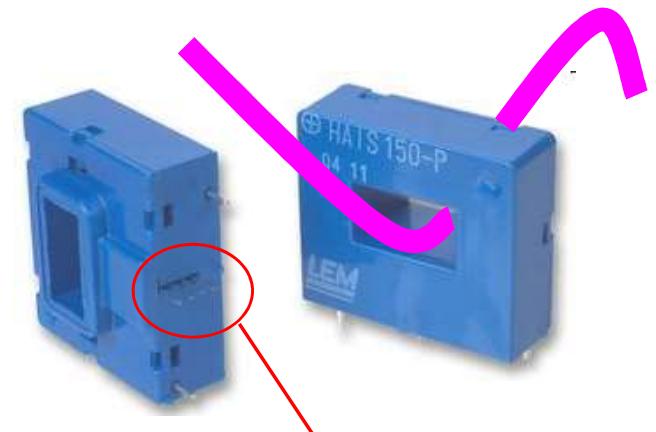

**Supply
Isolated measurement**

Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control

Models


Current control

Speed control

Energy storage
based chopper



DC motor: Current control

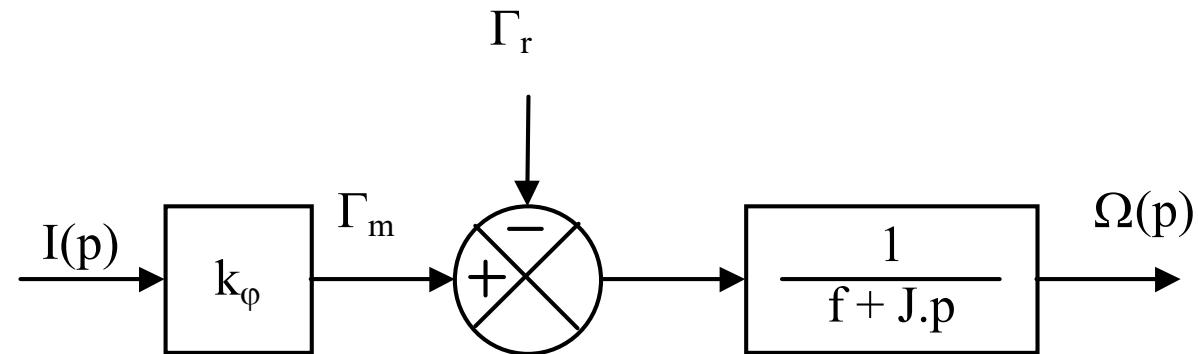

$$G_i(p) = \frac{\Omega(p)}{I(p)} = \frac{k_\phi}{f + J.p}$$

Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop chopper control

Models


Current control

Speed control

Energy storage
based chopper



Current loop

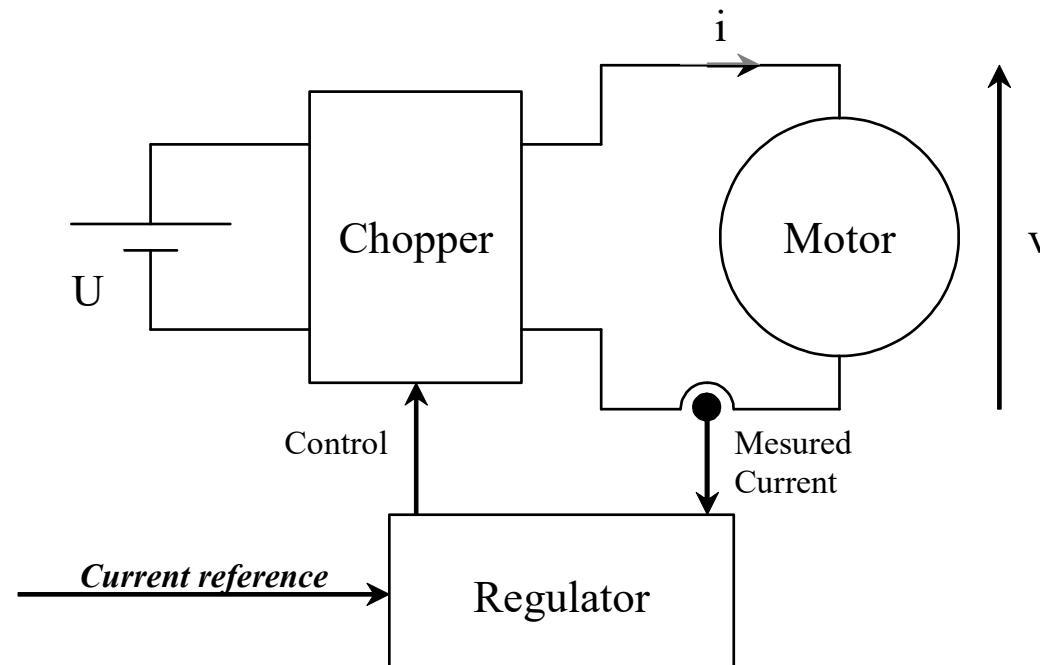

Introduction

Direct conversion

Reversible
choppers

Inverters

**Closed loop
chopper control**

Models

Current control

Speed control

Energy storage
based chopper



Control criteria

Accuracy : no static error

Speed : time response enhancement

Unconditional stability (high margin)

Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control

Models


Current control

Speed control

Energy storage
based chopper



Current Control

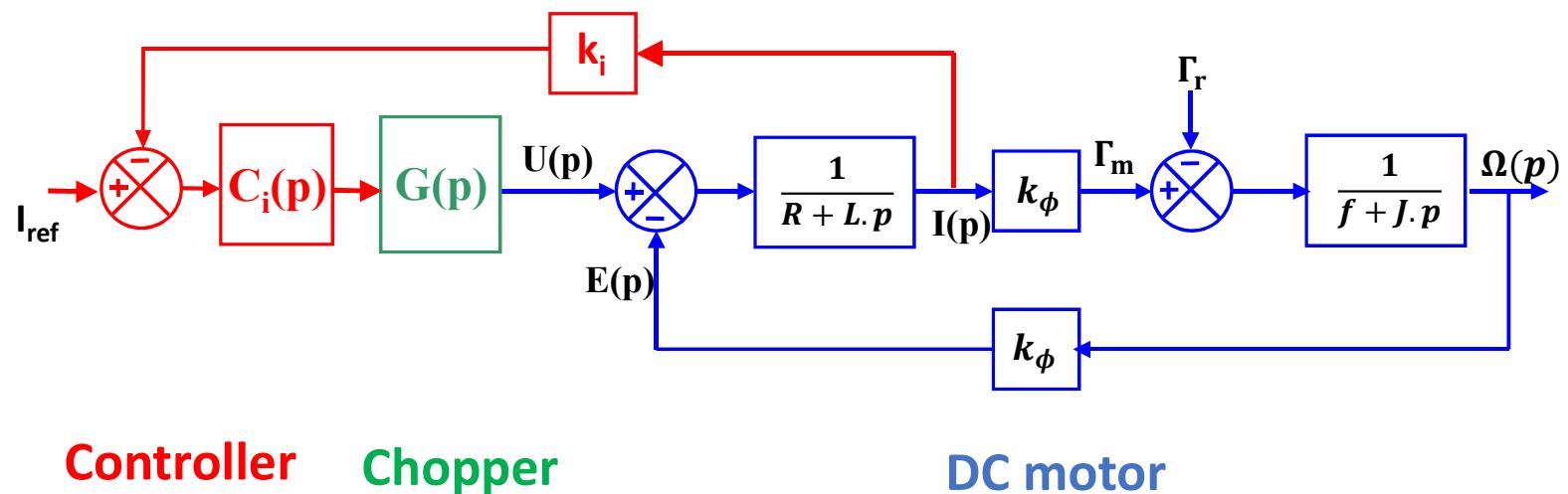

Controller

Chopper

DC motor

=> *Controller choice: $C_i(p)$*

Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control

Models


Current control

Speed control

Energy storage
based chopper



P.I. control: simplified chopper

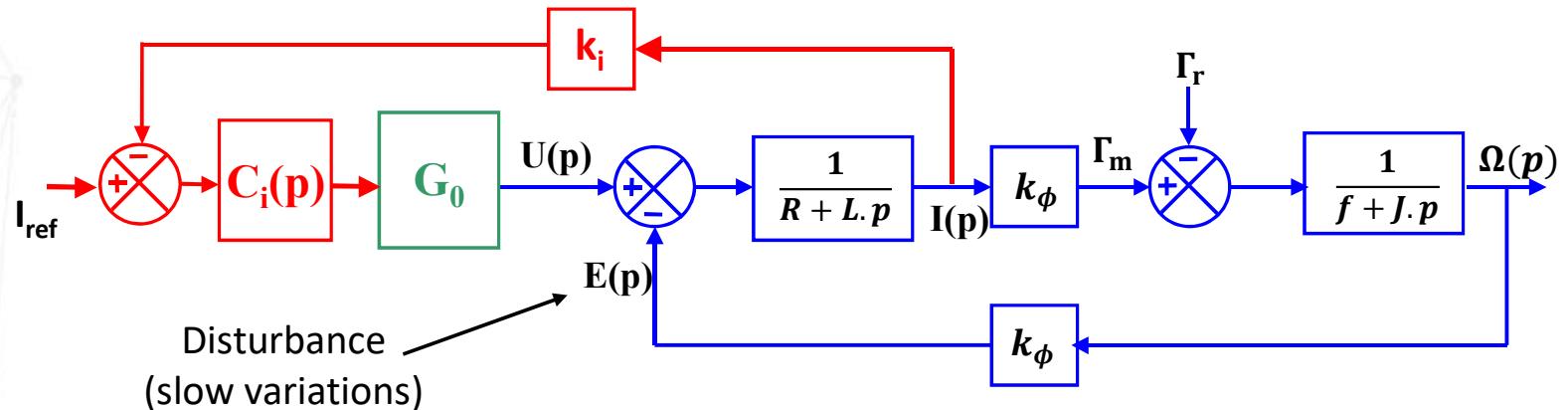

$$C_i(p) = k_i \cdot \frac{1 + \tau_i p}{\tau_i p}$$

$$H_{NCOL}(p) = \frac{G_0 / R}{1 + \tau_e p}$$

$$H_{OL}(p) = \frac{k_i \cdot (1 + \tau_i p) G_0 / R}{\tau_i p (1 + \tau_e p)}$$

$$\Rightarrow \tau_i = \tau_e$$

Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control

Models

Current control

Speed control

Energy storage
based chopper



P.I. control: simplified chopper

$$H_{CL}(p) = \frac{k_i \cdot G_0 / R}{k_i \cdot G_0 / R + \tau_e p} = \frac{1}{1 + \tau_{BF} p}$$

$$\tau_{BF} = \frac{\tau_e}{\frac{k_i G_0}{R}}$$

1st order without error, faster

Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control

Models


Current control

Speed control

Energy storage
based chopper



P.I. control: first order chopper

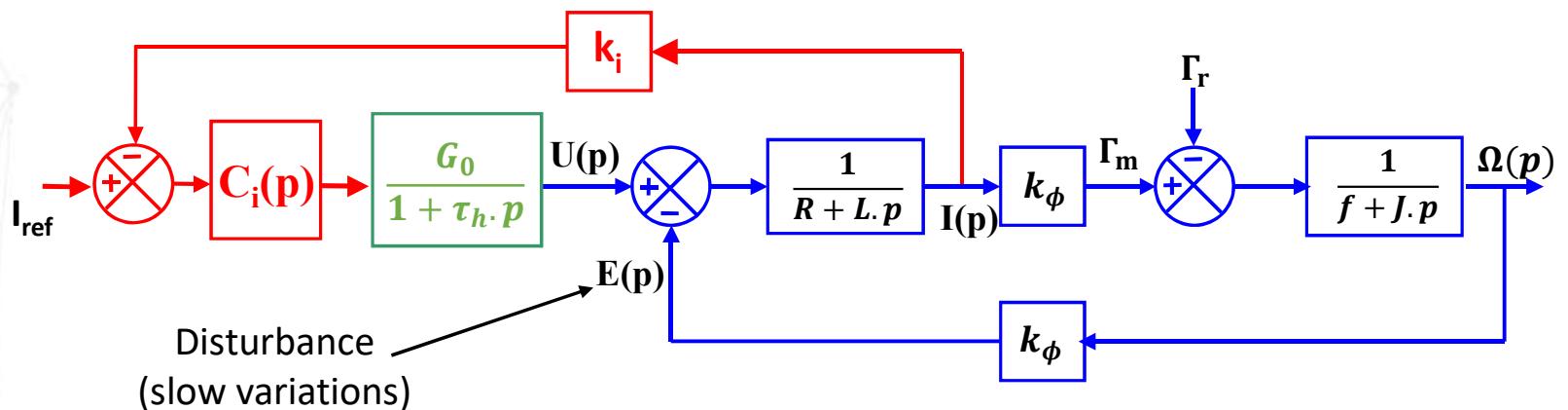

$$C_i(p) = k_i \cdot \frac{1 + \tau_i p}{\tau_i p}$$

$$H_{OL}(p) = \frac{G_0 / R}{(1 + \tau_h p) \cdot (1 + \tau_e p)}$$

$$H_{OL}(p) = \frac{k_i \cdot (1 + \tau_i p) G_0 / R}{\tau_i p (1 + \tau_h p) \cdot (1 + \tau_e p)}$$

$$\Rightarrow \tau_i = \max(\tau_h, \tau_e)$$

Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control

Models

Current control

Speed control

Energy storage
based chopper



Beyond Engineering

Closed loop

$$H_{OL}(p) = \frac{k_i G_0 / R}{\tau_{he} p (1 + \tau_{he})}$$

$$H_{CL}(p) = \frac{1}{1 + 2m \frac{p}{\omega_0} + \frac{p^2}{\omega_0^2}}$$

Second ordre without error

Choose of m : damping [0,7 .. 1]

Choose of ω_0 : bandwidth

Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control

Models

Current control


Speed control

Energy storage
based chopper



DC motor: Speed / voltage transfer function
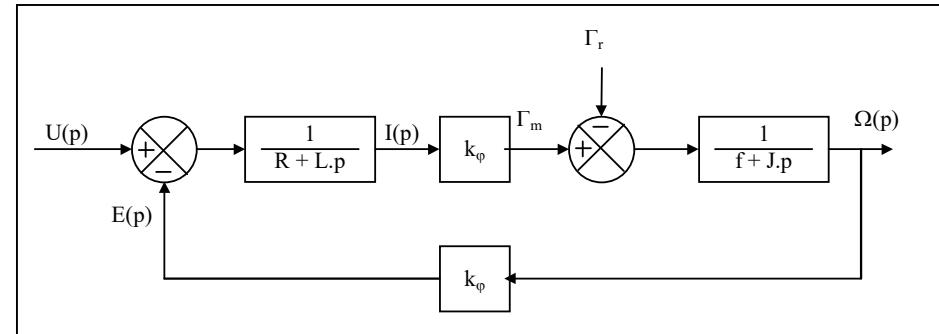
$$G'_u(p) = \frac{\Omega(p)}{U(p)} = \frac{k_\phi}{k_\phi^2 + (R + Lp)(f + Jp)}$$



$$G_u(p) = \frac{\Omega(p)}{U(p)} = \frac{k_\phi}{k_\phi^2 + Rf} \cdot \frac{1}{(1 + \tau_e p)(1 + \tau_{em} p)}$$

$$\tau_{em} = \frac{JR}{k_\phi^2 + Rf}$$
 electromechanical time constant

$$\tau_e = \frac{L}{R}$$
 electrical time constant

Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop chopper control

Models


Current control

Speed control

Energy storage
based chopper



Speed loop

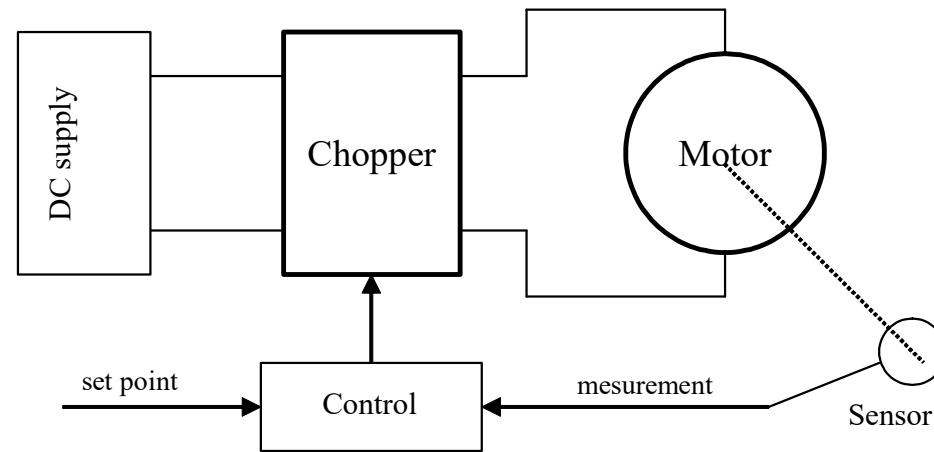

$$G_{hv}(p) = \frac{V_{\Omega mes}(p)}{V_{\Omega ref}(p)} = \frac{G_{0\Omega}}{1 + 2m \frac{p}{\omega_0} + \frac{p^2}{\omega_0^2}}$$

Introduction

Direct conversion

Reversible
choppers

Inverters


Closed loop
chopper control

Models
Current control
Speed control

Energy storage
based chopper



Nested loop

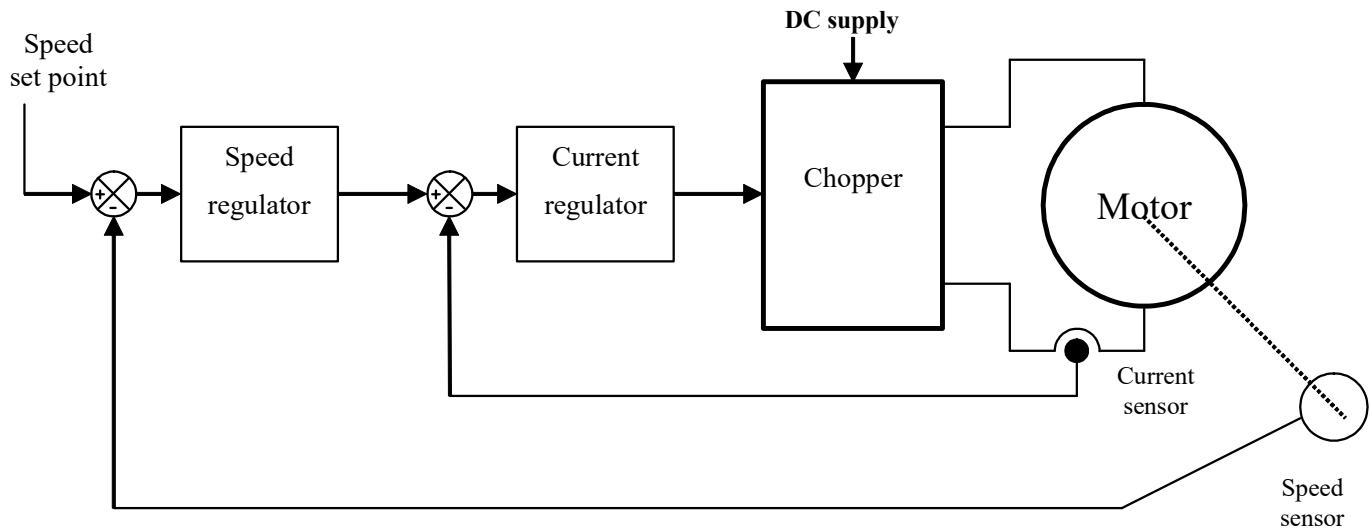

Internal loop faster than external loop

Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control

**Energy storage
based chopper**

Indirect Choppers

Introduction

Direct conversion


Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Indirect chopper: principle

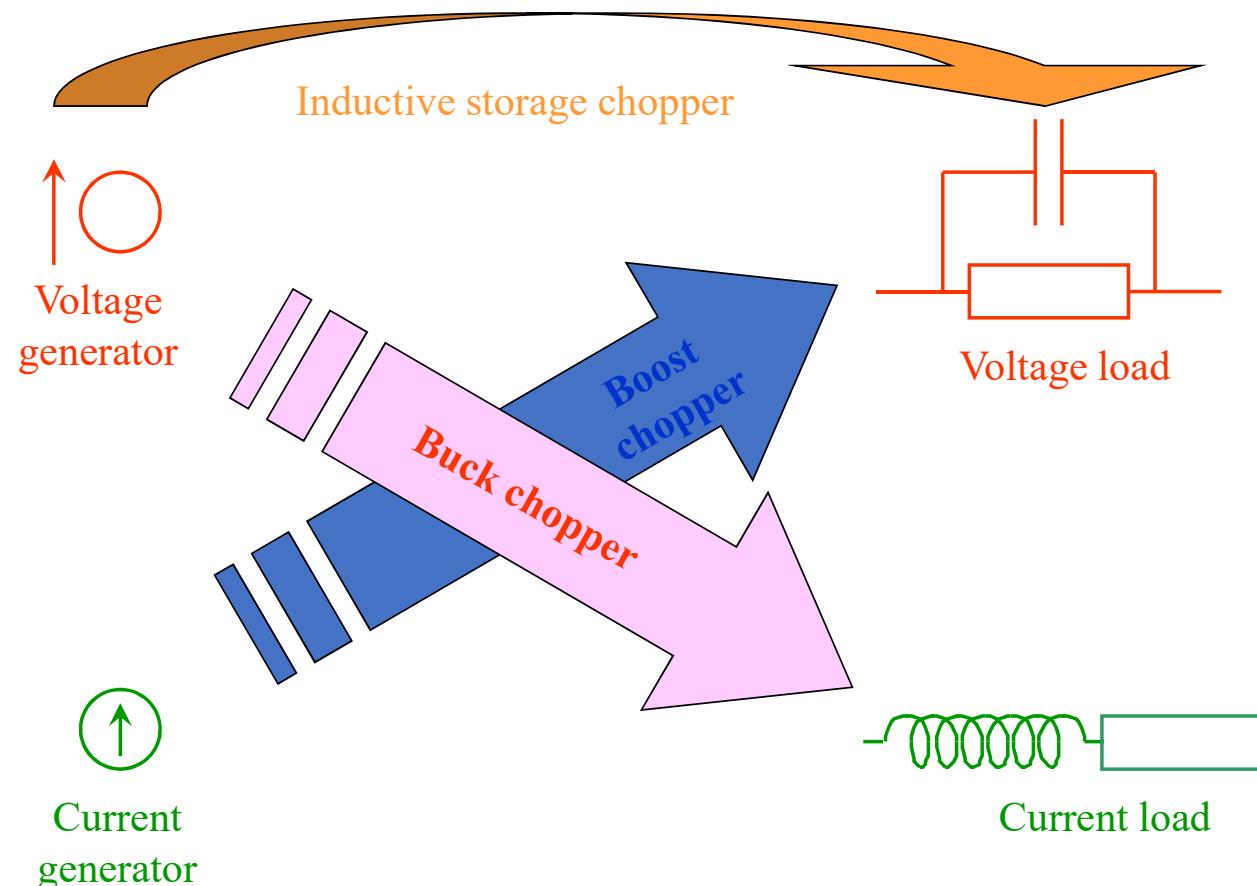

Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper


Buck-Boost

Cuk

SEPIC



Buck-Boost structure

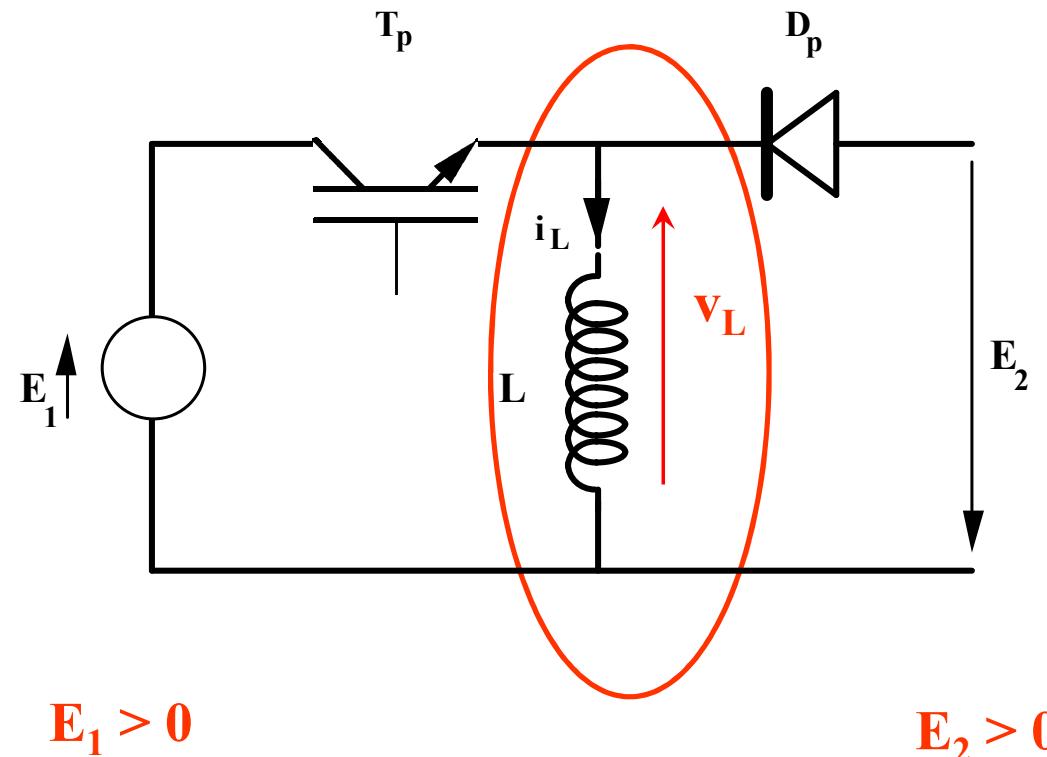

Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control


Energy storage
based chopper
Buck-Boost

Cuk

SEPIC




Buck-boost: Continuous mode ($i_L > 0$)

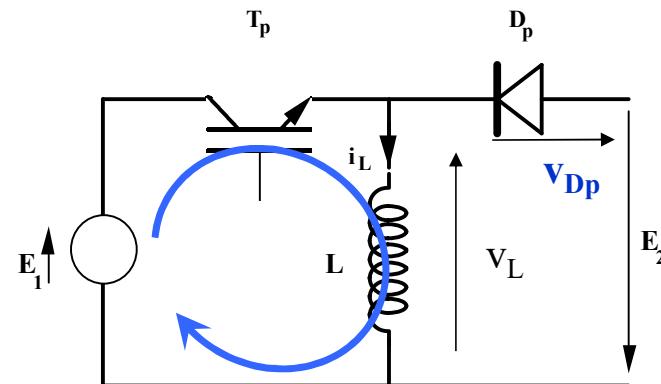

$0 < t < \alpha T : T_p$ closed

$v_{Dp} = -E_1 - E_2 \Rightarrow D_p$ reverse

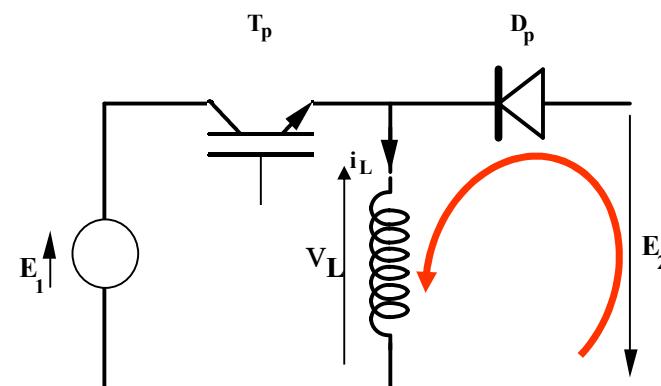$v_L = E_1 = L \cdot di_L/dt \Rightarrow i_L$ increasing > 0



$\alpha T < t < T : T_p$ opened

$i_L > 0 \Rightarrow D_p$ forward

$v_L = -E_2 = L \cdot di_L/dt \Rightarrow i_L$ decreasing

Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper


Buck-Boost

Cuk

SEPIC




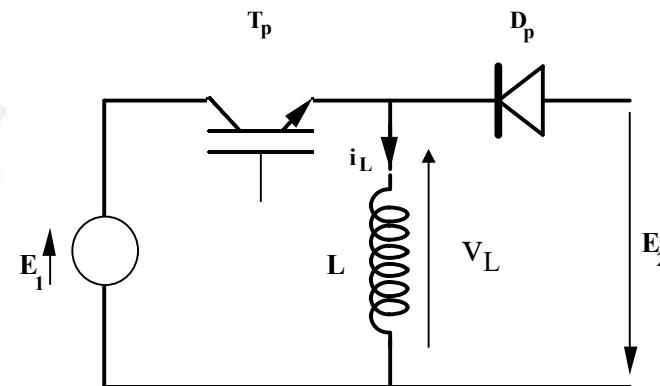Buck-boost: Continuous mode (chronograms)



$$\langle v_L \rangle = 0$$

Inductive storage chopper

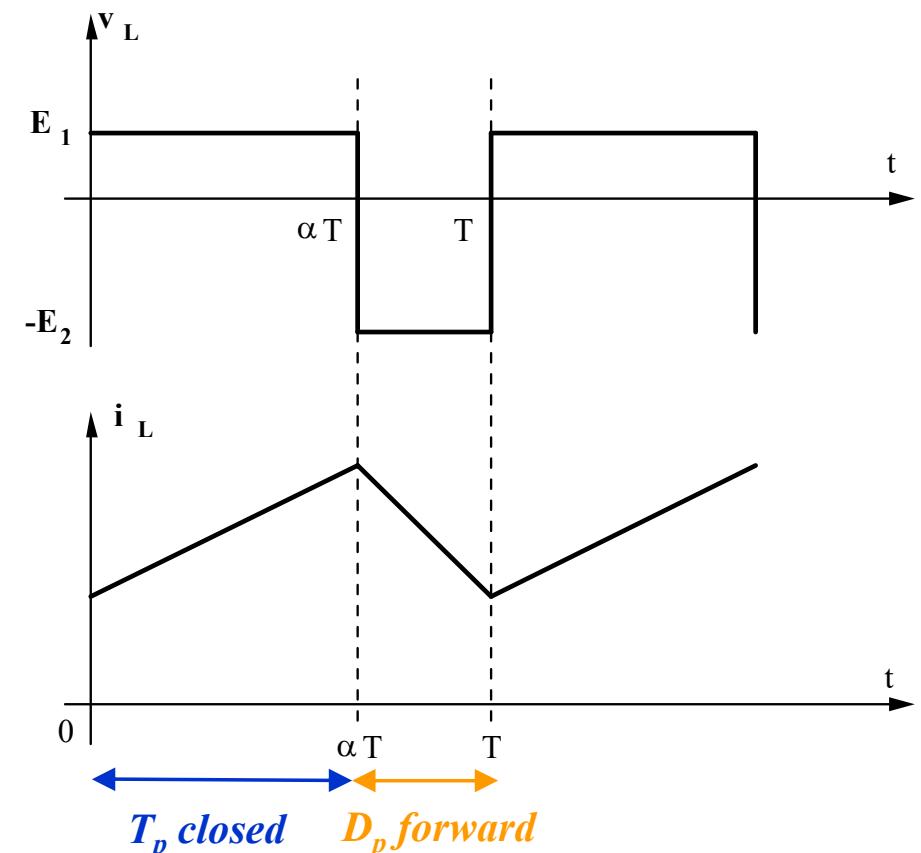

Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control


Energy storage
based chopper
Buck-Boost

Cuk


SEPIC



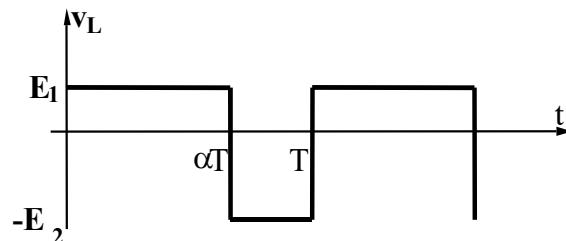Buck-boost: Continuous mode (Transfer characteristics)



$$\langle v_L \rangle = 0$$

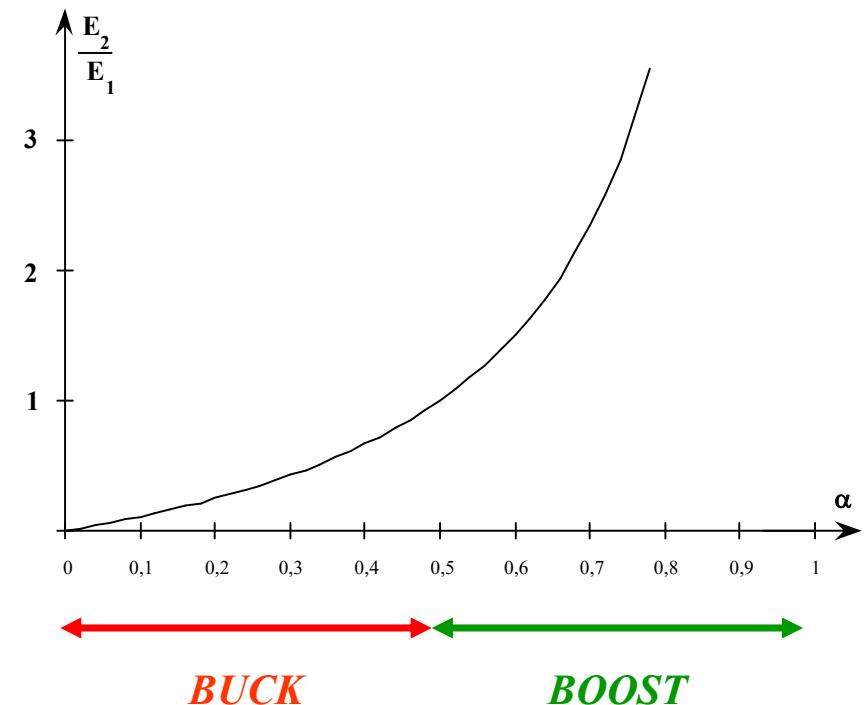

Introduction

Direct conversion

Reversible choppers

Inverters

Closed loop chopper control

Energy storage based chopper




Buck-Boost

Cuk

SEPIC



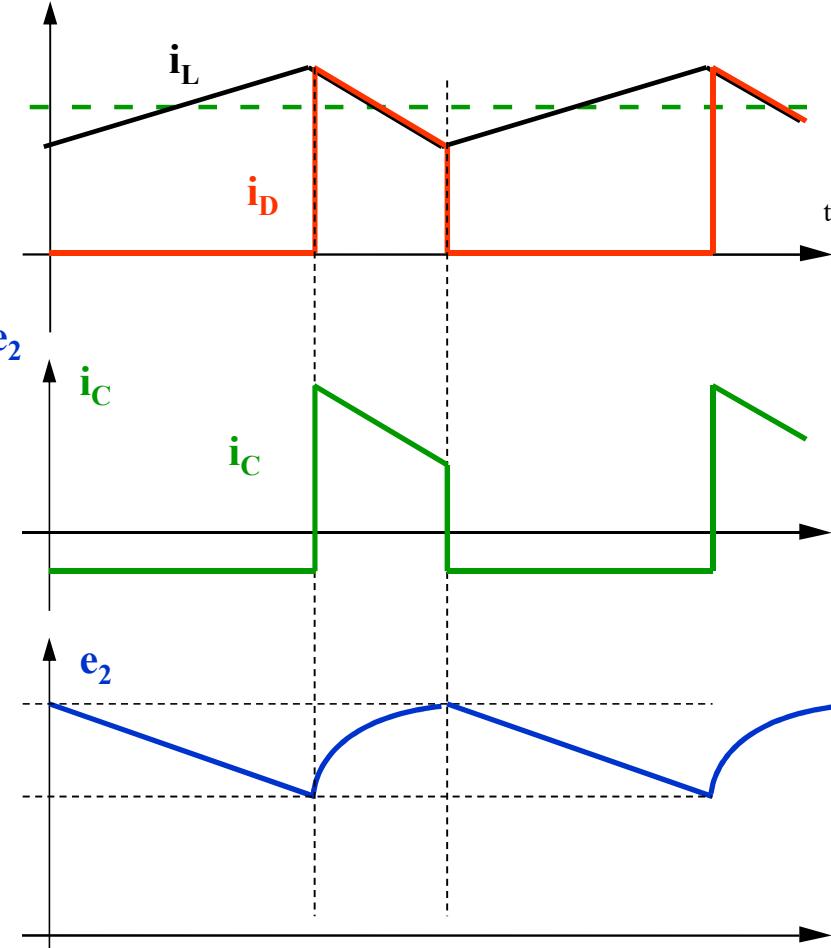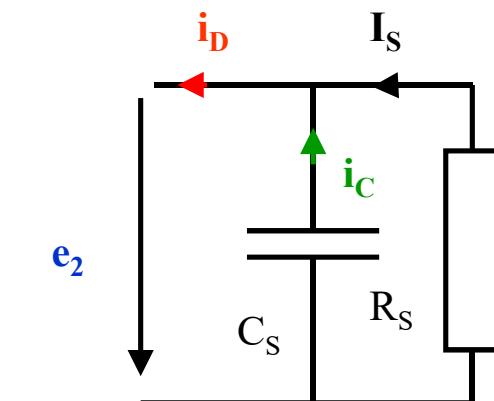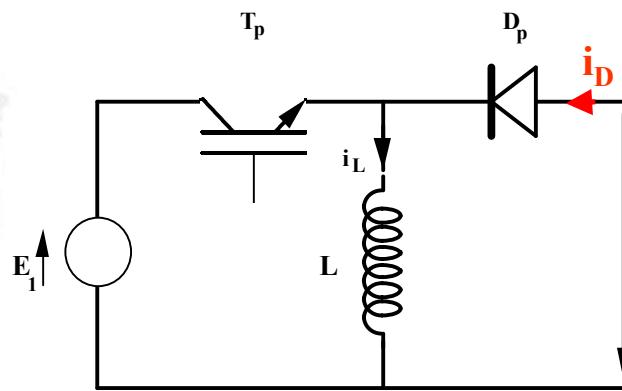Buck-boost: Continuous mode (output filtering)



Introduction

Direct conversion

Reversible choppers

Inverters

Closed loop chopper control

Energy storage based chopper

Buck-Boost

Cuk

SEPIC






Buck-boost: Continuous mode (Output filtering)

$$\Delta e_2 = \frac{1}{C_S} \cdot \int_0^{\alpha T} i_C(t) dt = \frac{I_S \cdot \alpha T}{C_S}$$

or $I_S = \frac{E_2}{R_S} = \frac{\alpha \cdot E_1}{(1-\alpha) R_S}$

$$\Delta e_2 = \frac{E_1 T}{R_S C_S} \cdot \frac{\alpha^2}{1-\alpha}$$

→ C_S

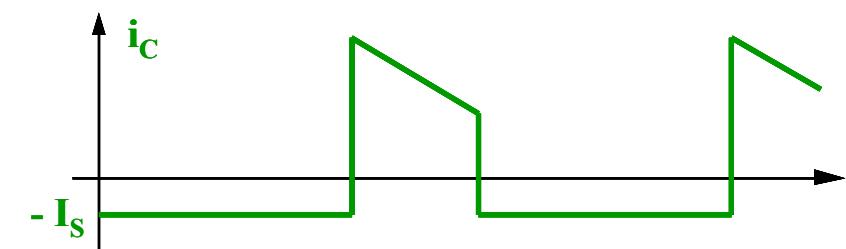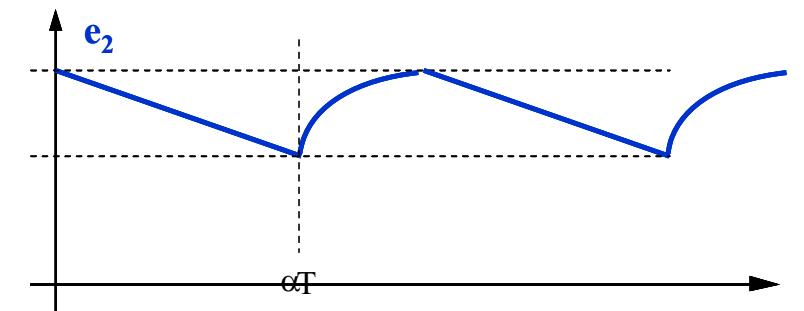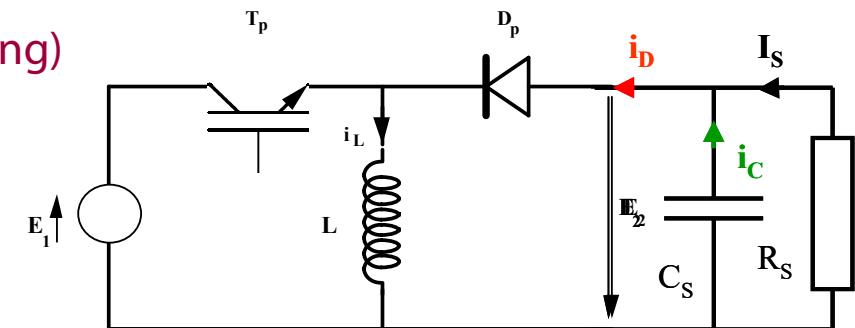

Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper


Buck-Boost

Cuk

SEPIC



Buck-boost: "decreasing" load

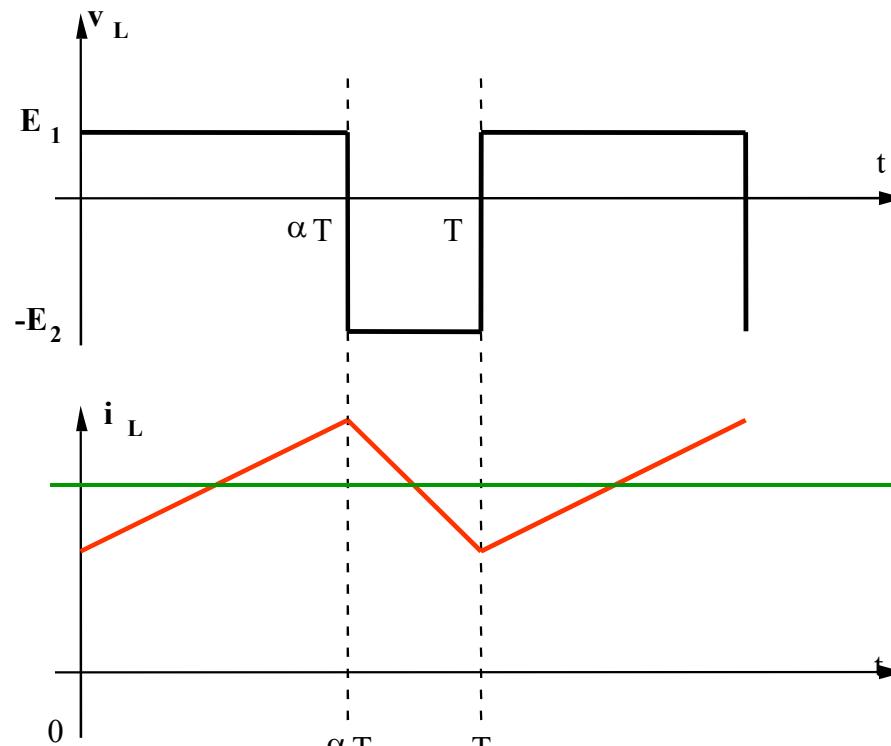

\Rightarrow Boundary mode

Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper



Buck-Boost

Cuk

SEPIC



Buck-boost: Boundary mode

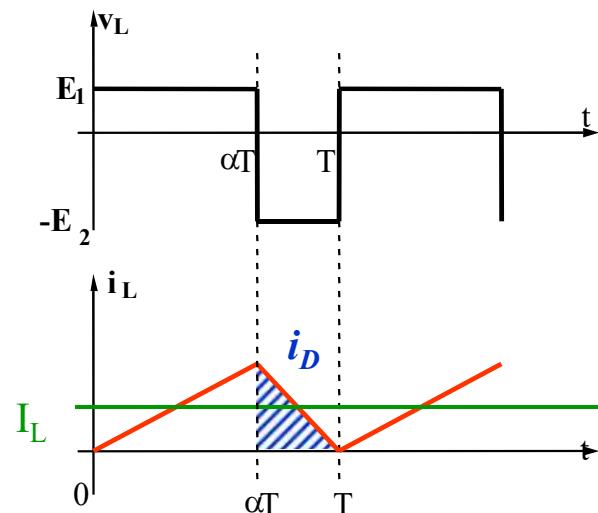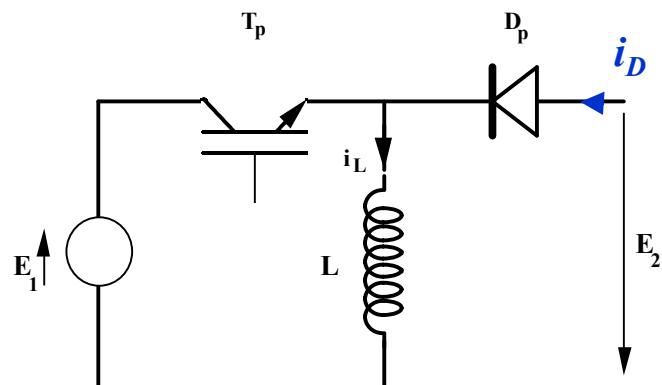

$$E_2 = E_1 \cdot \frac{\alpha}{1-\alpha} \Rightarrow \alpha = \frac{E_2}{E_1 + E_2}$$

$$I_{Lc} = \frac{E_1}{L} \frac{\alpha T}{2} = \frac{E_1 \cdot E_2}{E_1 + E_2} \cdot \frac{T}{2L} = \frac{I_{L\max}}{2}$$

Average boundary mode $I_S = \langle i_D \rangle$

$$I_S = \frac{I_{L\max}}{2} \cdot (1-\alpha) = \frac{E_1^2 \cdot E_2}{(E_1 + E_2)^2} \cdot \frac{T}{2L}.$$

$$\rightarrow E_2 = f(I_S)$$

Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper


Buck-Boost

Cuk

SEPIC



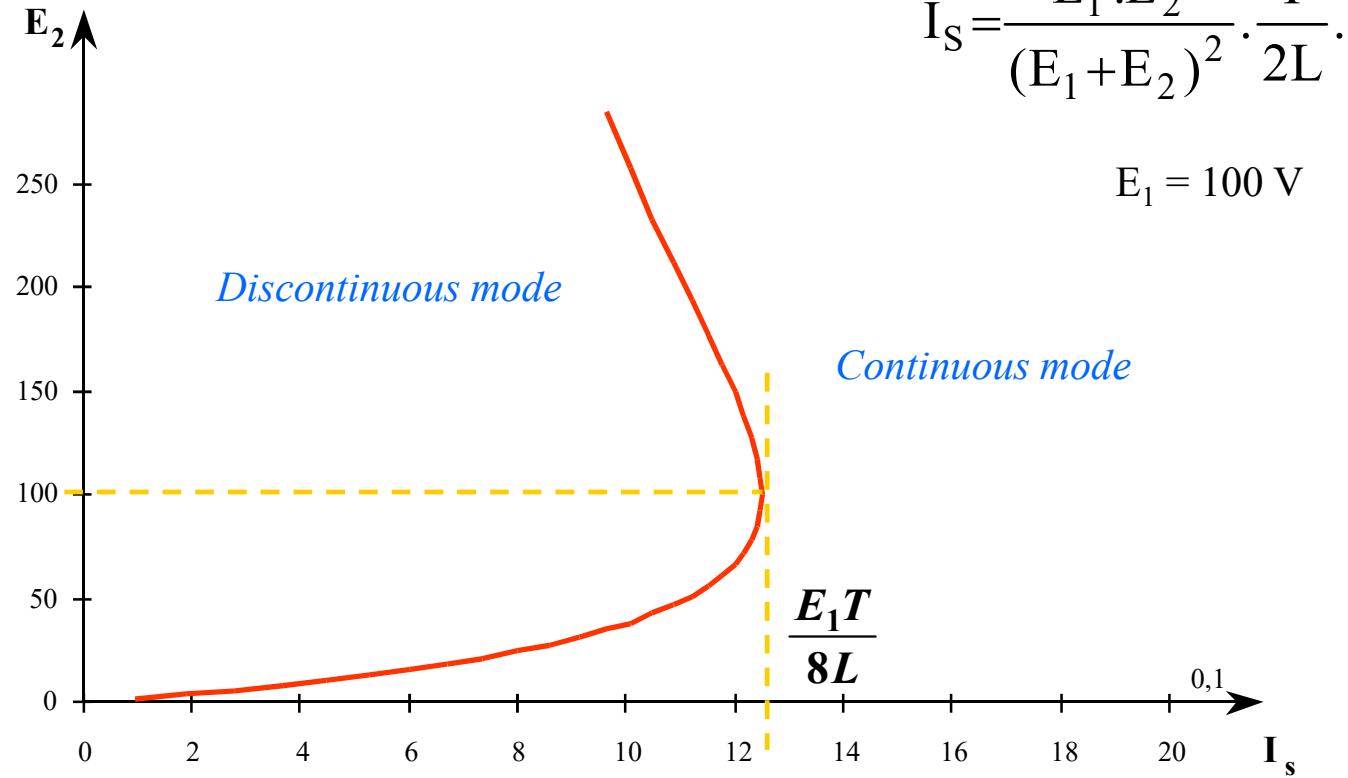Buck-boost: Boundary mode (characteristics)



Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper



Buck-Boost

Cuk

SEPIC



Buck-boost: Discontinuous mode

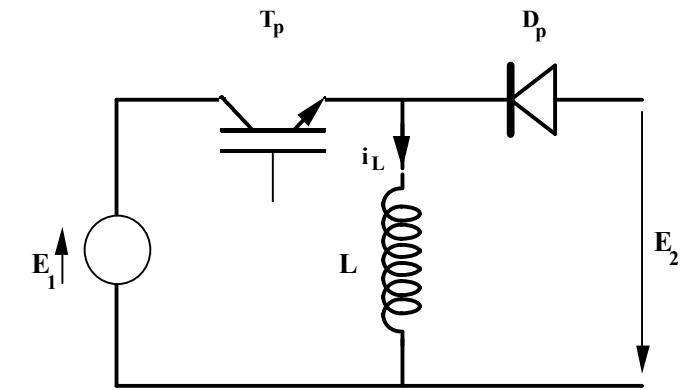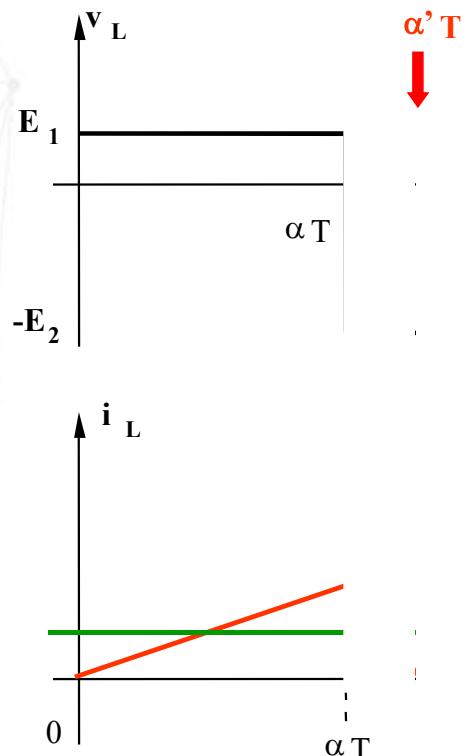

Full study: Switched-mode power supply

Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper


Buck-Boost

Cuk

SEPIC



Buck-boost: Discontinuous mode

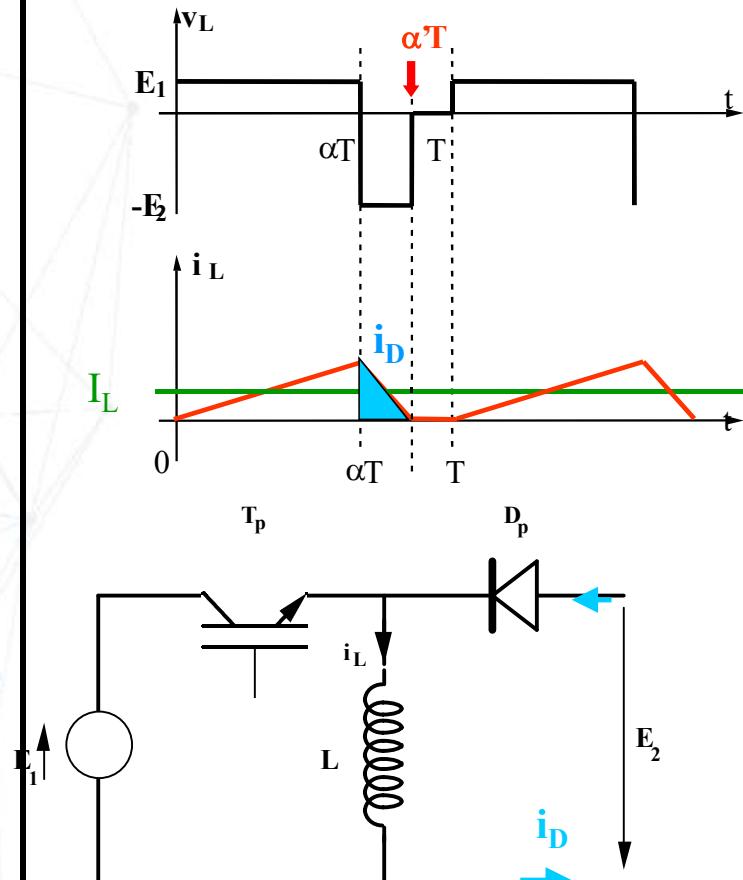

$$\langle v_L \rangle = 0 = \alpha E_1 - (\alpha' - \alpha) E_2 \Rightarrow \alpha' = \alpha + \frac{E_1 + E_2}{E_2}$$

$$I_S = \langle i_D \rangle = (\alpha' - \alpha) \cdot \frac{I_{L_{\max}}}{2} = (\alpha' - \alpha) \left(\alpha \frac{E_1 T}{2L} \right)$$

$$\rightarrow I_S = \frac{\alpha^2 \cdot E_1^2 \cdot T}{2L \cdot E_2}$$

Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper


Buck-Boost

Cuk

SEPIC



Buck-boost: Output characteristics

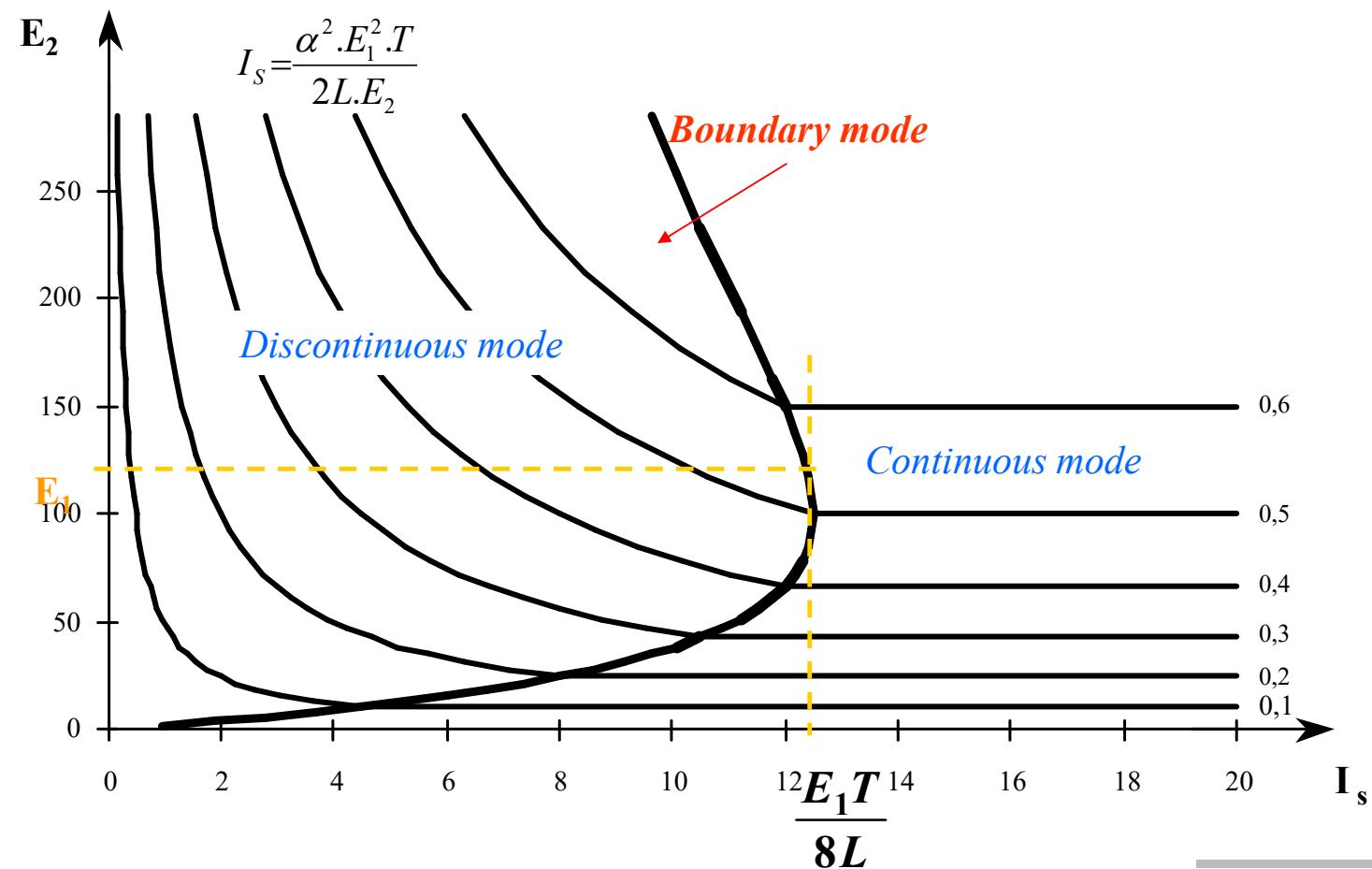

Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper


Buck-Boost

Cuk

SEPIC



Capacitive storage chopper

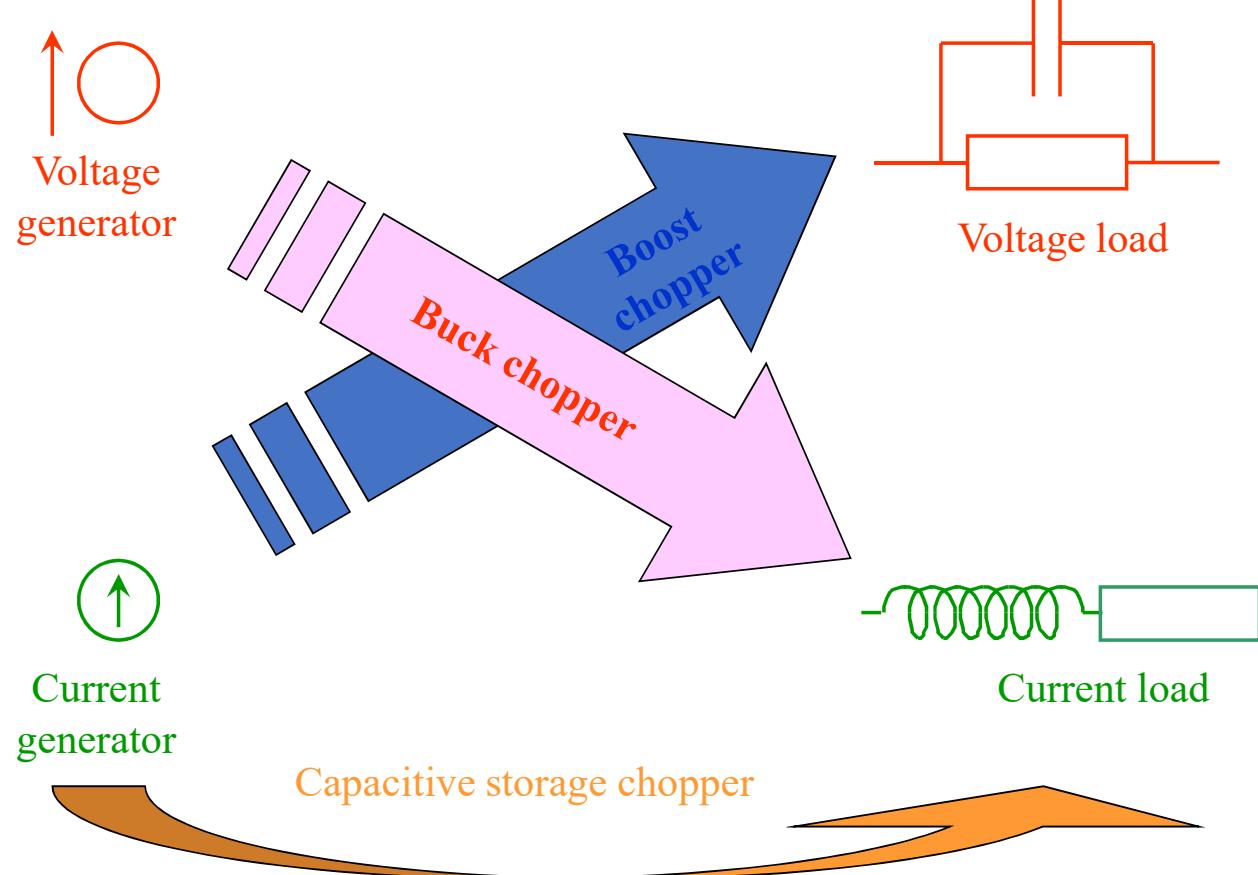

Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper


Buck-Boost

Cuk

SEPIC



CUK structure

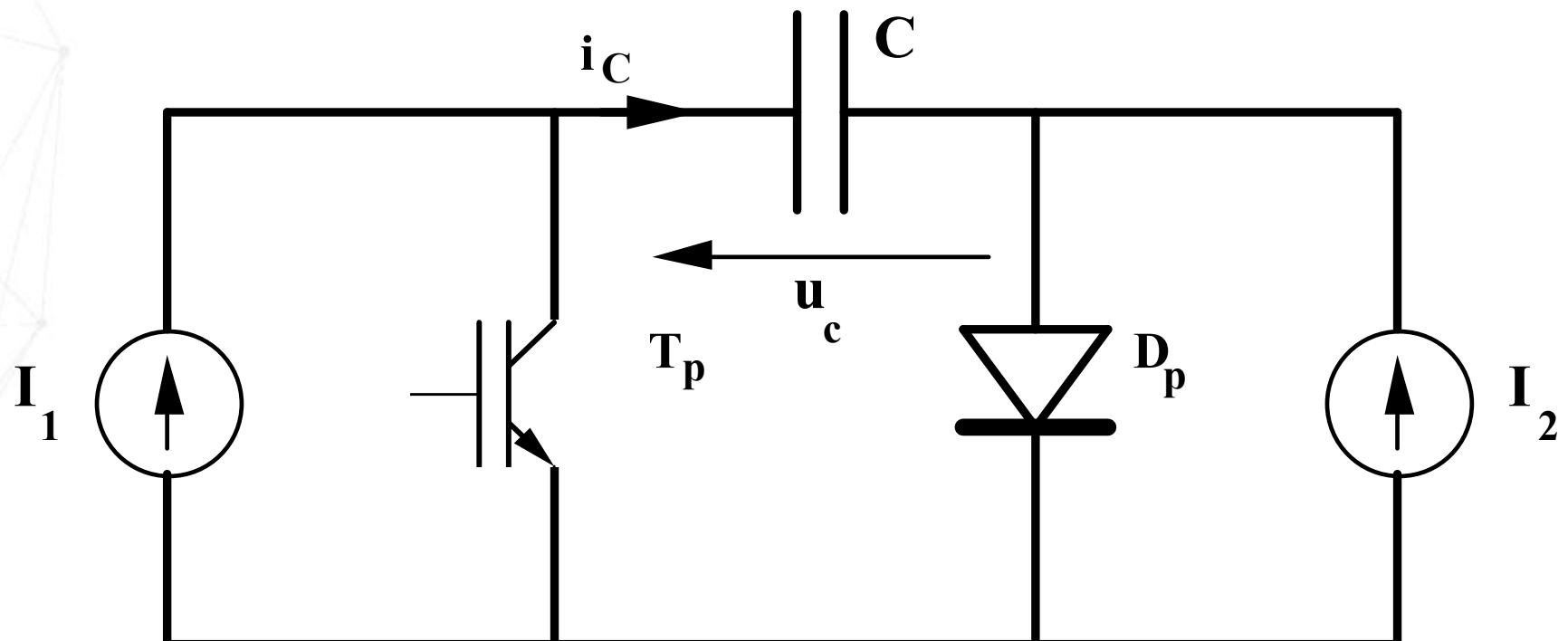

Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control


Energy storage
based chopper

Buck-Boost
Cuk

SEPIC



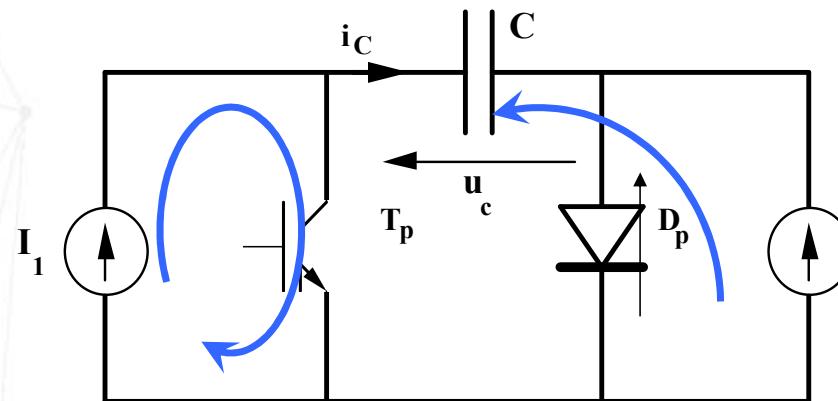
CUK structure: continuous mode ($u_c > 0$)



$0 < t < \alpha T : T_p$ closed

$v_{Dp} = -u_c \Rightarrow D_p$ reverse

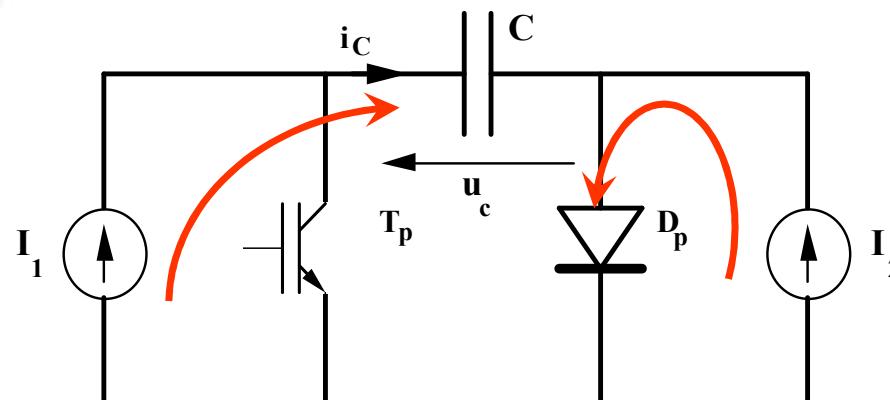$i_c = -I_2 = C \cdot du_c/dt \Rightarrow u_c$ decreases



$\alpha T < t < T : T_p$ opened

$i_c = I_1 = C \cdot du_c/dt \Rightarrow u_c$ increases

$i_D = I_1 + I_2 \Rightarrow D_p$ forward

Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Buck-Boost

Cuk


SEPIC



CUK structure: Chronograms

$$\langle i_C \rangle = 0$$
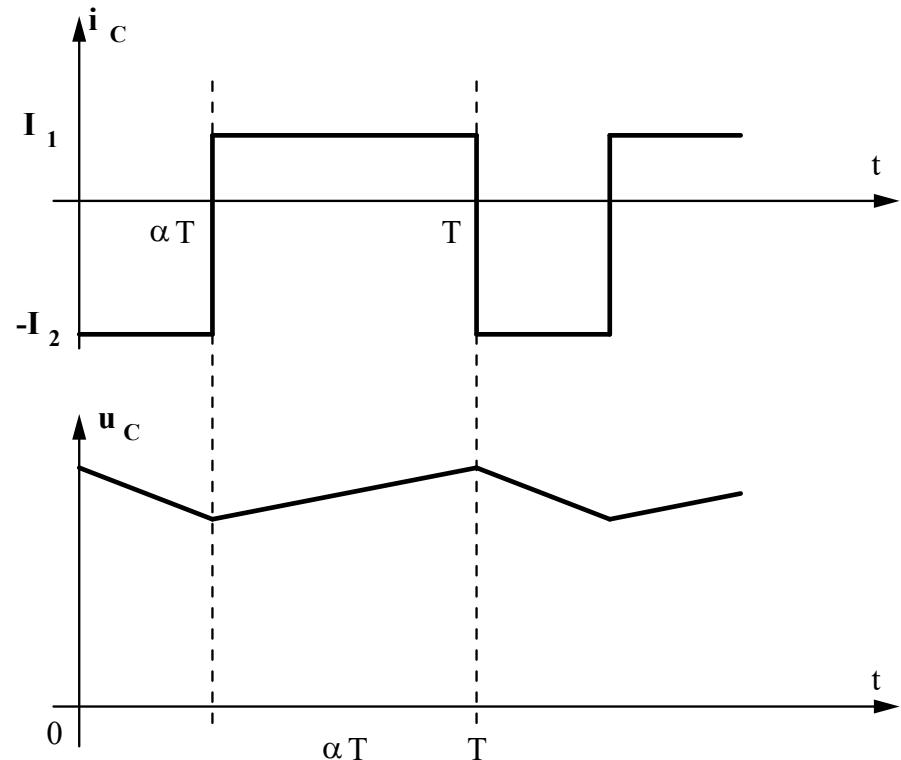
$$I_2 = I_1 \cdot \frac{1 - \alpha}{\alpha}$$



Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control

**Energy storage
based chopper**

Buck-Boost

Cuk


SEPIC



ENSEA

Beyond Engineering

CUK structure: Transfer characteristic

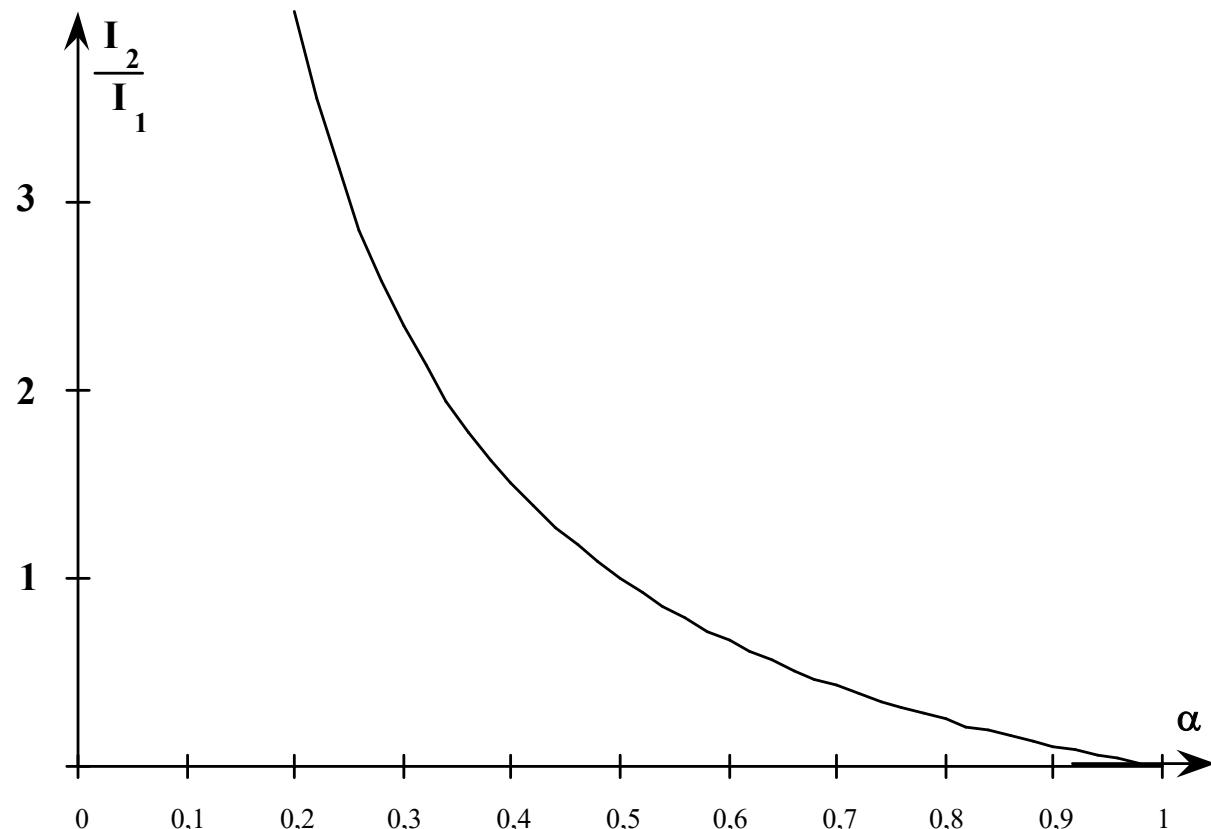

Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper


Buck-Boost

Cuk

SEPIC



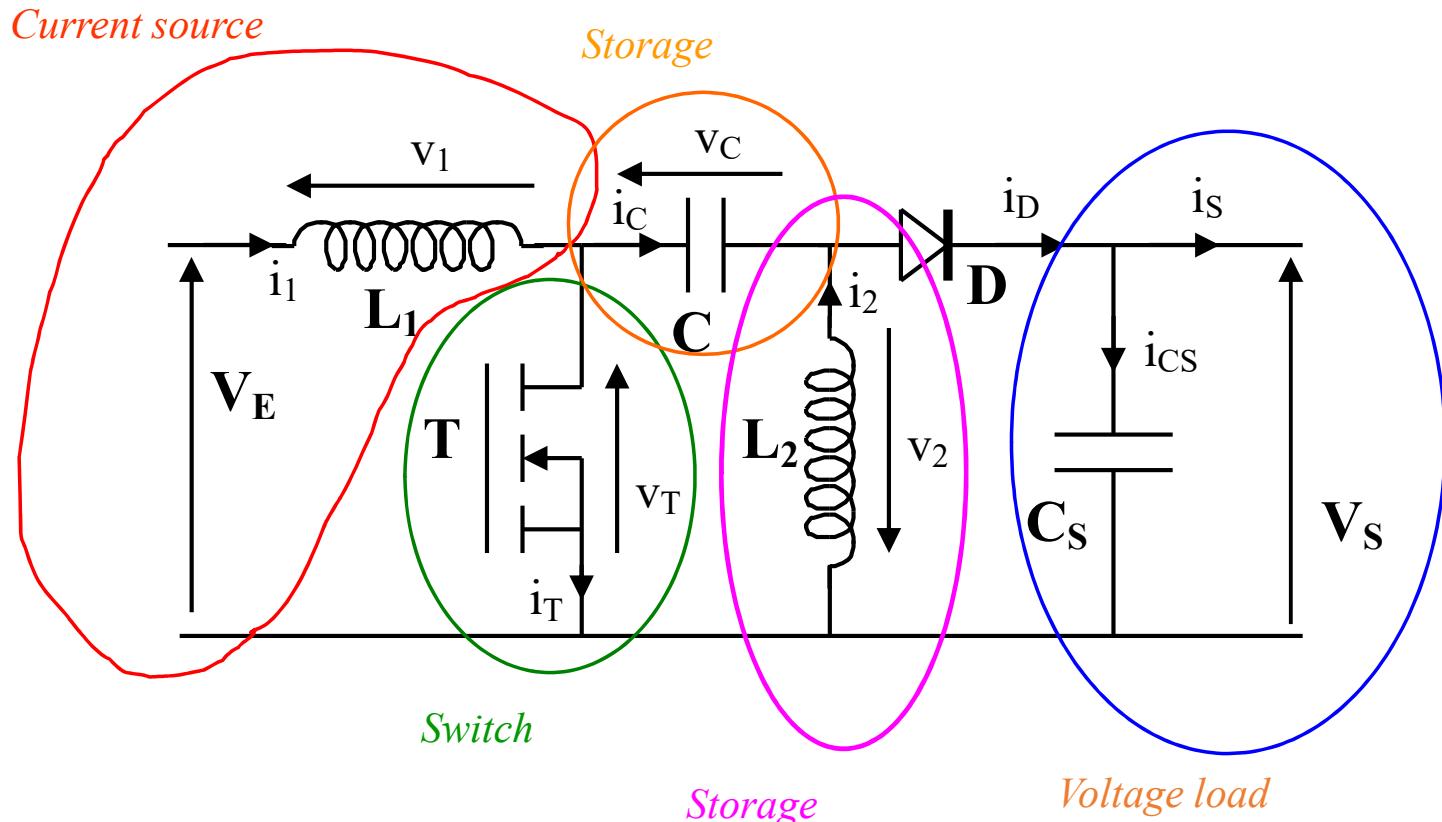SEPIC: Single Ended Primary Inductor Converter



Introduction

Direct conversion

Reversible choppers

Inverters

Closed loop chopper control

Energy storage based chopper



Buck-Boost

Cuk

SEPIC



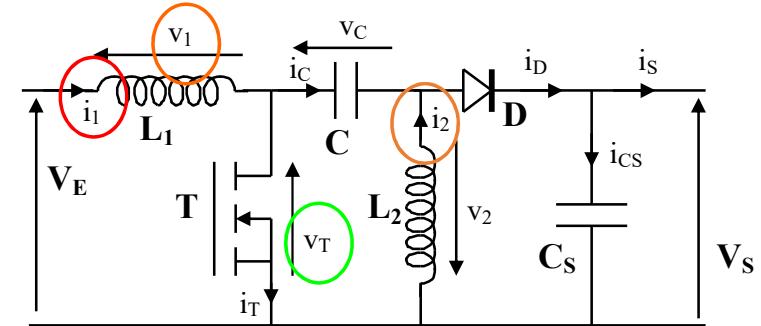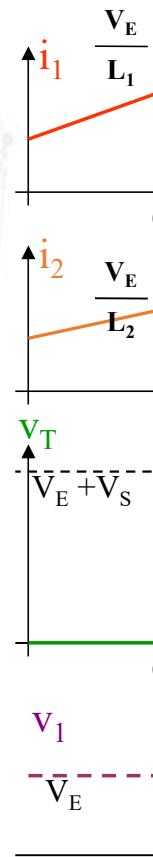SEPIC: Continuous mode (voltage transfer)



$$\langle v_1 \rangle = 0 \text{ et } \langle v_2 \rangle = 0 \Rightarrow \langle v_C \rangle = V_E = \text{Constant}$$

$$V_S = V_E \cdot \frac{\alpha}{1-\alpha}$$

Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper



Buck-Boost

Cuk

SEPIC



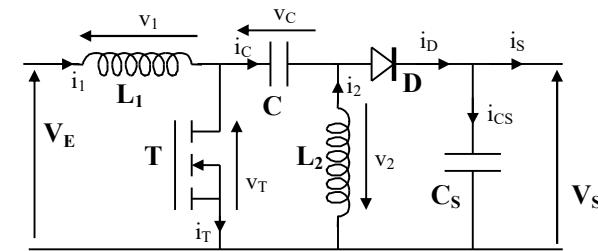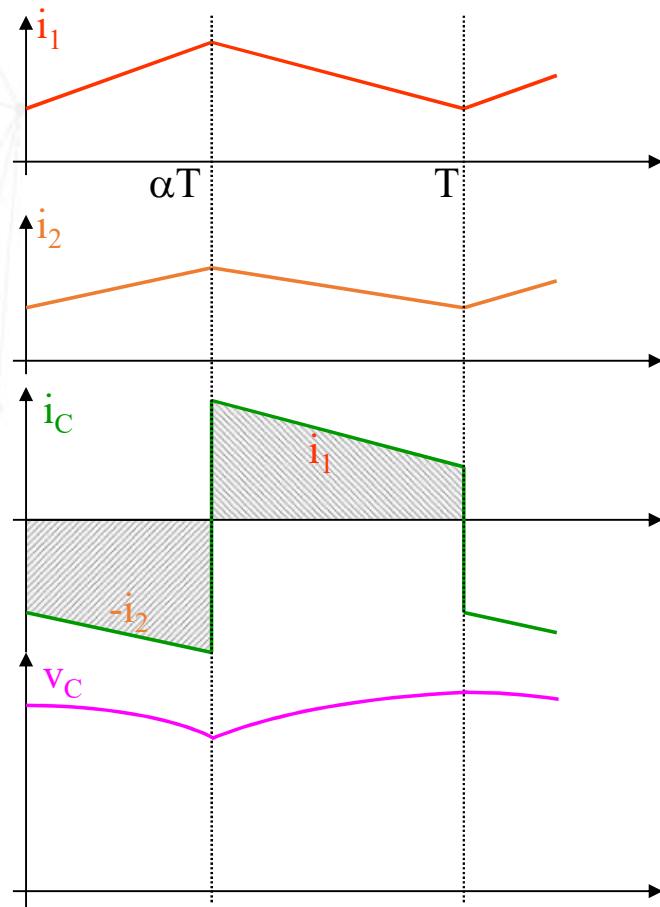SEPIC: Continuous mode (coupling capacitor)



$$I_2 = I_S \quad I_S = I_E \cdot \frac{1-\alpha}{\alpha}$$

$$\Delta V_C = \frac{\alpha \cdot I_S}{C \cdot f}$$

$$I_{C_{eff}} = I_S \cdot \sqrt{\frac{\alpha}{1-\alpha}}$$

Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Buck-Boost


Cuk

SEPIC



SEPIC: circuit example

TPS 61170 – Texas Instrument

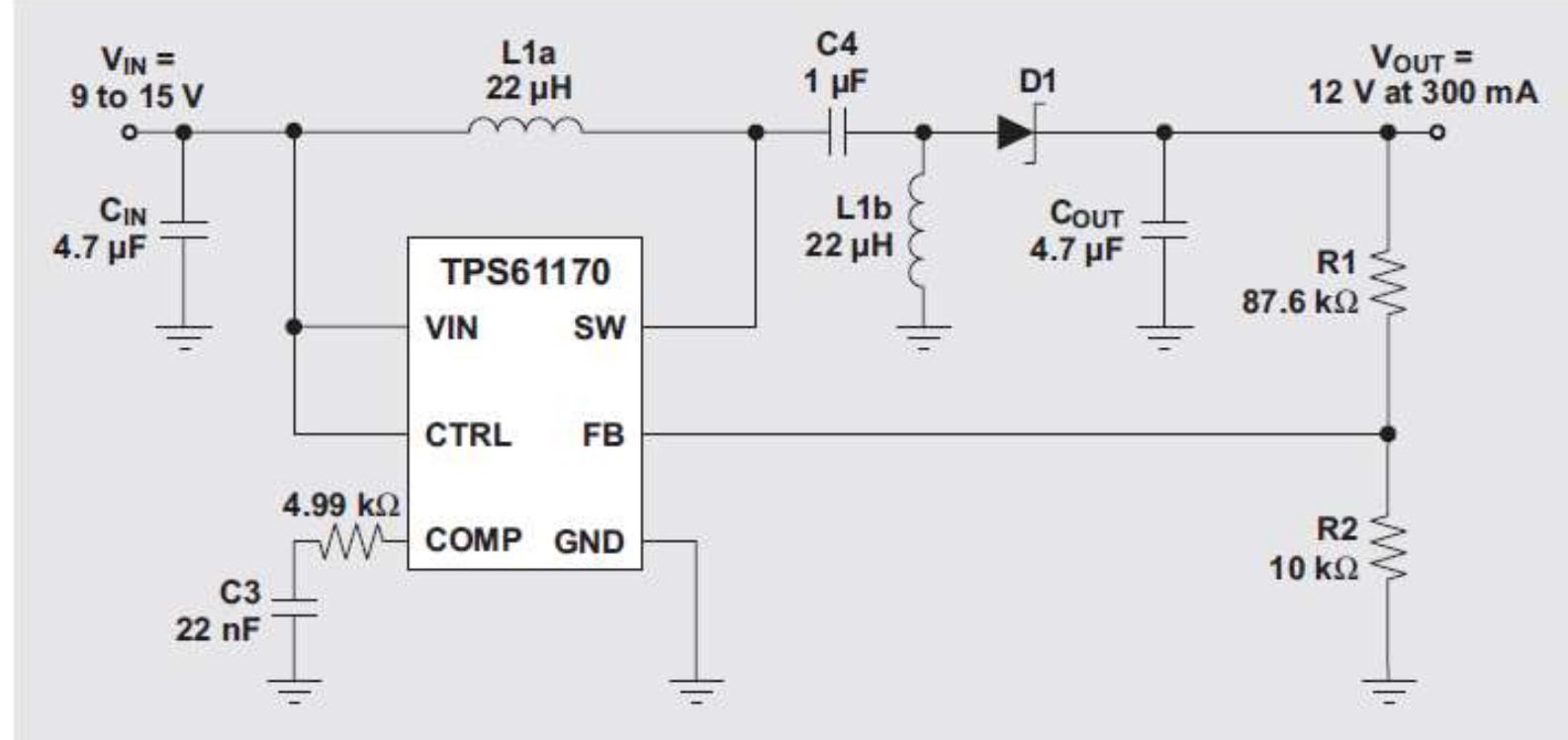

Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper




Buck-Boost

Cuk

SEPIC



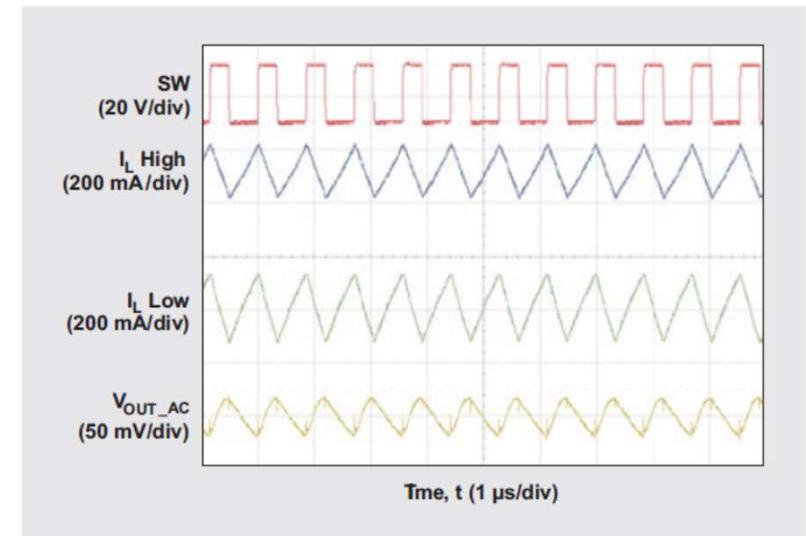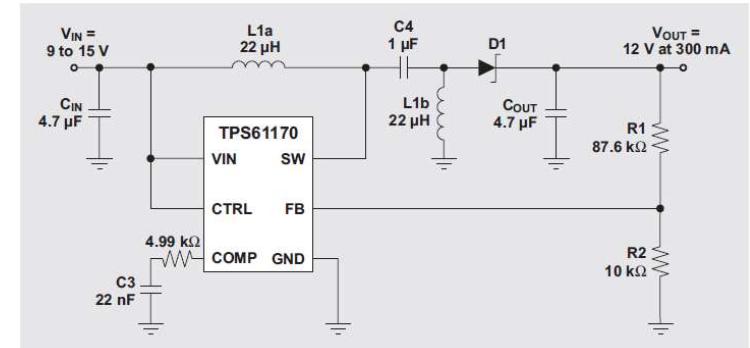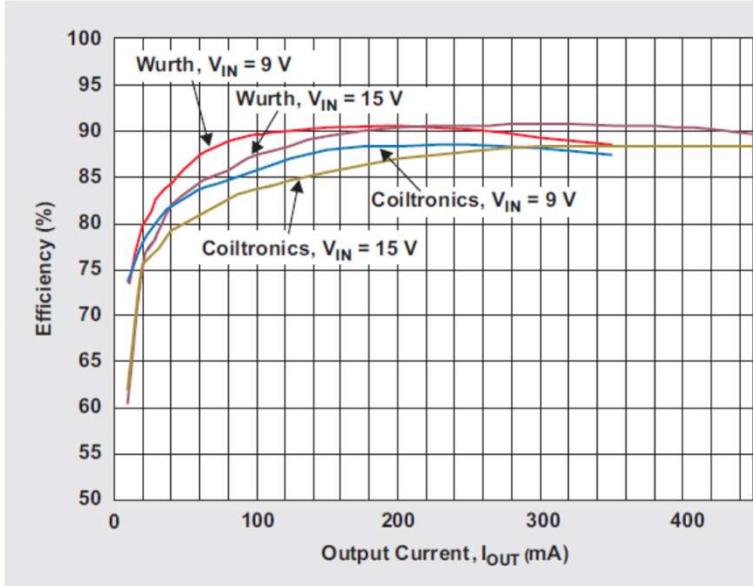SEPIC: circuit example TPS 61170 – Texas Instrument



Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper


Buck-Boost

Cuk

SEPIC



LM3481

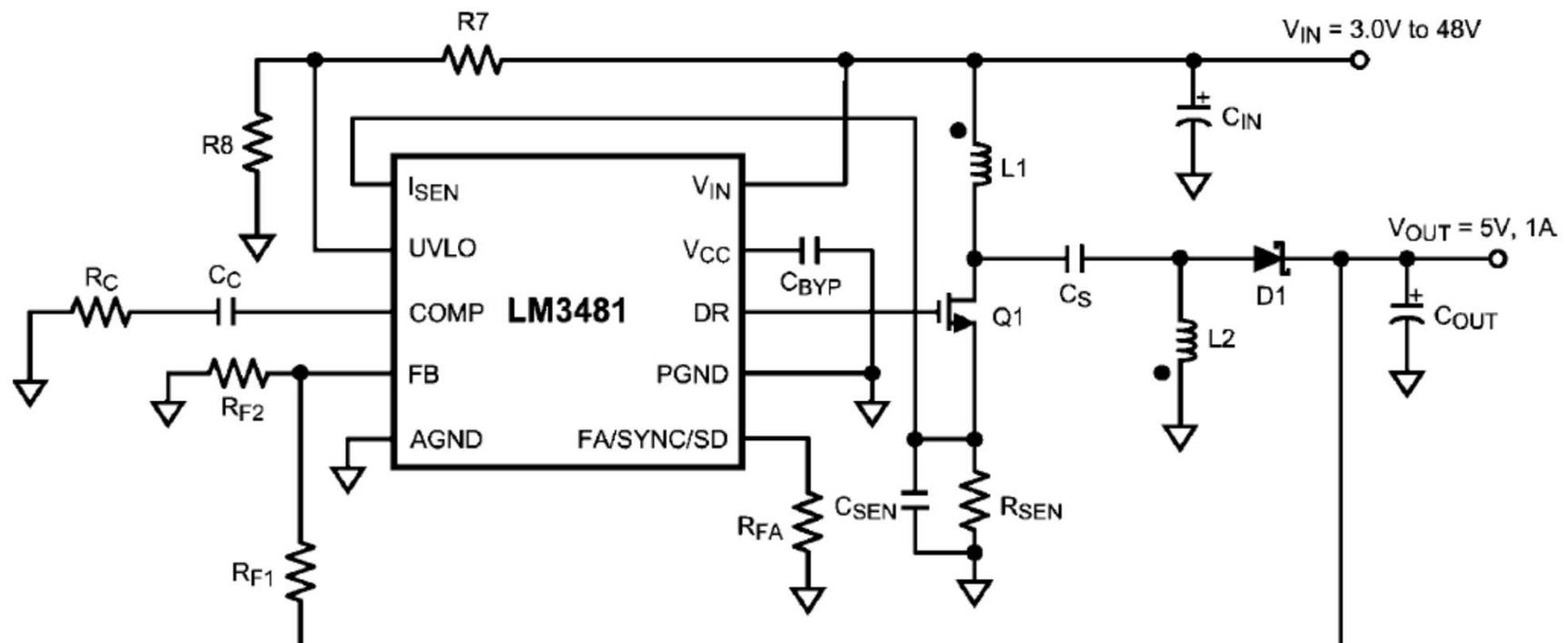

Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Buck-Boost



Cuk

SEPIC



LM3481

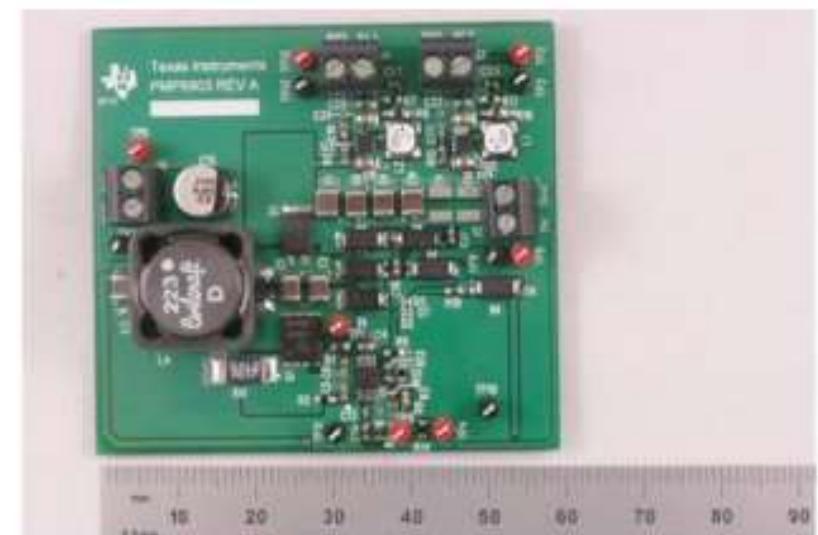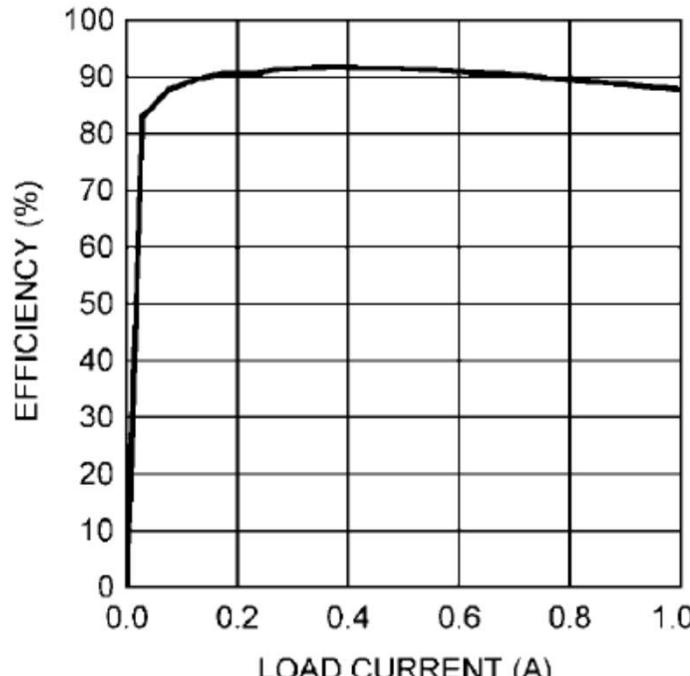Efficiency vs. Load Current ($3.3V_{IN}$ and $12V_{OUT}$)



Introduction

Direct conversion

Reversible
choppers

Inverters

Closed loop
chopper control

Energy storage
based chopper

Buck-Boost

Cuk

SEPIC



LM3481: internal schematic

